

Contents

Preface vii

To the Instructor ix

1	A Basic Electric Circuit	1	7	Series-Parallel Circuits	44
1.1	Getting Started	1	7.1	Basic Circuit Forms	44
1.2	A Simple Circuit	2	7.2	Series-parallel Circuits: First Form	44
1.3	Basic Particles	3	7.3	Series-parallel Circuits: Second Form	46
1.4	Atoms and Molecules	4	7.4	Mental Approximations	47
1.5	Representing Fields of Force	5	8	Magnetism	51
2	Current and Voltage	9	8.1	The Magnetic Field	51
2.1	Electric Current	9	8.2	Magnetism of a Coil	52
2.2	The Coulomb	12	8.3	Permeability of Materials	54
2.3	Velocity of Current	12	8.4	Temporary and Permanent Magnets	55
2.4	Electric Pressure or Voltage	13	8.5	Magnetic Attraction and Repulsion	56
3	Resistance and Conductance	17	9	Alternating Current	61
3.1	Electron Sources in Series	17	9.1	Direct Current	61
3.2	Resistance Decreases Current	19	9.2	Alternating Current	62
3.3	Resistance and Wires	20	9.3	Inducing Emf	63
3.4	Conductors and Ionization	21	9.4	Generating an A-c	64
4	Ohm's Law in Series Circuits	25	9.5	Frequency of A-c	66
4.1	Current Form of Ohm's Law	25	9.6	Peak, Rms, and Average Values	67
4.2	Solving for Voltage	26	10	Inductance and Transformers	70
4.3	Solving for Resistance	28	10.1	Developing Counter-emf	70
4.4	The Ohm's Law Triangle	29	10.2	Inductance	72
5	Energy and Power	31	10.3	The Shorted-turn Effect	73
5.1	Electrical Energy	31	10.4	Transformers	74
5.2	Electrical Power	32	10.5	Power and Current Ratios in Transformers	75
5.3	Combining Power and Ohm's Law Formulas	33	11	Series RL Circuits	80
5.4	Substituting E/R in the Power Formula	34	11.1	Resistance-inductance Time Effects	80
5.5	Practical Energy Formulas	34	11.2	Current Lags Voltage	83
6	Parallel Circuits	34	11.3	Inductive Reactance	85
6.1	Review of Series Circuits	34	11.4	Impedance	86
6.2	Conductance and Resistance	38	12	Capacitance	91
6.3	Parallel Circuits	39	12.1	The Capacitor	91
6.4	Leaning-ladder Graphs	41	12.2	The Farad	91
6.5	Kirchhoff's Current Law	41	12.3	Types of Capacitors	93
			12.4	Dielectric Strength and Constant	96
			12.5	Capacitors in Parallel	97
			12.6	Capacitors in Series	97

13	RC Circuits	101	19.7	Balanced-bridge Measuring Devices	166
13.1	Resistance-capacitance Time Effects	101	19.8	A D-c Vacuum-tube Voltmeter Bridge	167
13.2	Phase Angle	103	19.9	Electrostatic Voltmeters	169
13.3	Capacitive Reactance	104	19.10	Digital Voltmeters	170
13.4	Impedance in Capacitive Circuits	105	19.11	D-c Wattmeters	171
14	Series LCR Circuits	109	19.12	Ampere-hour Meters	172
14.1	Series LC Circuits	109	20	A-c Meters	175
14.2	Series Resonance	110	20.1	A-c Components with D-c Meters	175
14.3	Series L, C, and R	111	20.2	Rectifier-type A-c Meters	177
14.4	The Q of a Series Circuit	113	20.3	Peak-reading and dB Meters	179
15	Parallel LCR Circuits	117	20.4	Electrodynamometers	181
15.1	Parallel-reactance Circuits	117	20.5	Repulsion-type Meters	182
15.2	Parallel LC Circuits	118	20.6	A-c Wattmeters	184
15.3	Antiresonance	119	20.7	Watthour Meters	184
15.4	The Oscillating LC Tank Circuit	120	20.8	Thermocouple Ammeters	185
15.5	Parallel R, L, and C	122	20.9	Frequency Meters	186
15.6	Current Vectoring a Parallel LCR Circuit	123	20.10	Grid-dip Meters	188
16	Tuning Circuits	127	21	Alternators	192
16.1	Tuning Circuits	127	21.1	Rotating-coil Alternators	192
16.2	Double-tuned Transformers	128	21.2	Rotating-field Alternators	194
16.3	Low-pass Filters	130	21.3	Inductor Alternators	195
16.4	High-pass Filters	131	21.4	The Efficiency of Machines	196
16.5	Bandstop Filters	132	21.5	Adding an Alternator to a Line	196
17	Vacuum Tubes and Transistors	135	21.6	Polphase Alternators	198
17.1	The Diode Vacuum Tube	135	21.7	Delta-connected Alternators	199
17.2	The Triode	137	21.8	Y-connected Alternators	200
17.3	Solid-state Diodes	141	21.9	Transporting Electrical Power	202
17.4	Transistors	142	21.10	3- ϕ Transformer Configurations	202
18	D-c Ammeters	147	22	D-c Generators	207
18.1	Meter Accuracy	147	22.1	Externally Excited D-c Generators	207
18.2	The Moving-coil Meter	148	22.2	Voltage Regulation	208
18.3	Changing Ammeter Ranges	151	22.3	The Effect of More Commutator Segments	209
18.4	Multirange Ammeters	153	22.4	Commutators and Brushes	210
18.5	Meter Damping	155	22.5	Shunt Generators	212
18.6	Linear and Nonlinear Meter Scales	156	22.6	Series Generators	212
19	Other D-c Meters	159	22.7	Compound Generators	213
19.1	D-c Voltmeters	159	22.8	Armature Reaction	214
19.2	Moving-coil Voltmeters	159	22.9	Four-pole Generators	215
19.3	Voltmeter Loading of a Circuit	160	22.10	Machine Maintenance	215
19.4	High-voltage Voltmeters	162	23	Motors	218
19.5	Ohmmeters	163	23.1	Electric Motors	218
19.6	Decade Boxes	164	23.2	Series Motors	219

23.3	Shunt Motors	220	27.3	Ferromagnetism	274
23.4	Exciting a D-c Motor with A-c	222	27.4	Permeability Curves	275
23.5	A Thyatron Motor Control	223	27.5	Hysteresis Loops	276
23.6	Reversing Motors	224	27.6	Magnetizing and Demagnetizing	278
23.7	Motor Generators and Dynamotors	225	27.7	Magnetostriction	278
23.8	Synchronous A-c Motors	226	27.8	Magnetic Transducers	279
23.9	Squirrel-cage A-c Motors	227	27.9	Relays	279
23.10	Three-phase Motors	229	27.10	Determining Polarity with a Compass	281
24	Batteries	234	27.11	English and Cgs Magnetic Units	282
24.1	Electrochemical Actions	234	28	The Sine Wave	286
24.2	Electroplating	235	28.1	Frequencies of Alternating Current	286
24.3	The Development of the Cell	236	28.2	Harmonics	287
24.4	The Leclanché Cell	236	28.3	The Sine Wave	289
24.5	Other Primary Cells	238	28.4	Determining Instantaneous Values	290
24.6	Lead-acid Cells	239	28.5	Adding Two Sine Waves	292
24.7	Specific Gravity of a Lead-acid Cell	241	28.6	Radians and Angular Velocity	294
24.8	The Capacity of a Cell	242	28.7	Period and Wavelength	295
24.9	Charging Batteries	242	29	Resistors and Inductors	299
24.10	Maintaining Lead-acid Cells	243	29.1	Wire-wound Resistors	299
24.11	Alkaline Secondary Cells	244	29.2	Carbon Resistors	301
24.12	Nonchemical Cells	245	29.3	Color Codes	302
25	Kirchhoff Loops in Circuits	251	29.4	Miniature Inductors	303
25.1	The Kirchhoff Laws	251	29.5	Radio-frequency Chokes	305
25.2	Applying Direction to Current and Voltage	251	29.6	Iron-core Chokes	305
25.3	Parallel Sources with a Common Load	253	29.7	Energy in Inductors	307
25.4	A Battery-charging Circuit	254	29.8	Inductance in Series	309
25.5	Two-wire Distribution Systems	255	29.9	Coefficient of Coupling	311
26	Superposition and Thévenin Systems	259	29.10	Determining Inductance	311
26.1	Solving Networks by Superimposing	259	30	Capacitors	316
26.2	Superposition with More Complex Circuits	260	30.1	Capacitors	316
26.3	The Thévenin Voltage	262	30.2	Energy in Capacitors	317
26.4	Solving Complex Circuits by the Thévenin Method	263	30.3	Dielectric Breakdown	317
26.5	Computing an Unbalanced Bridge	264	30.4	Capacitor Specifications	319
26.6	Thévenin's Theorem	267	30.5	Solving for Transient Values	319
26.7	Solving a Black-box Circuit	267	30.6	Capacitor Color Codes	321
27	Magnetic Circuits	271	31	Series A-c Circuits	325
27.1	Magnetic Circuits	271	31.1	Series LCR Circuits	325
27.2	Magnetic Terms	272	31.2	The Pythagorean Theorem	325
			31.3	Series Circuits with X_L and X_C	326
			31.4	The Sine Ratio	329
			31.5	The Cosine and Tangent Ratios	330
			31.6	Solving RL and RC A-c Circuits	332

32	Parallel and Complex A-c Circuits	335			
32.1	Solving Parallel A-c Circuits	335			
32.2	The Pythagorean Theorem in Parallel Circuits	336			
32.3	Solving for Parallel Impedances	338			
32.4	Equivalent Circuits	338			
32.5	Graphing Equivalent Circuits	342			
32.6	Computing Series-parallel A-c Circuits	343			
32.7	Solving for Individual Circuit Parameters	345			
33	The j-Operator	352			
33.1	Real and Imaginary Numbers	352			
33.2	The j-Operator	353			
33.3	Adding Real and Imaginary Numbers	354			
33.4	Real and Imaginary Voltage Values	355			
33.5	Rectangular and Polar Forms	357			
33.6	Converting from Polar to Rectangular Form	358			
33.7	The j-Operator in a Parallel Circuit	359			
33.8	The j-Operator in Series-parallel Circuits	360			
34	Power Transformers	365			
34.1	The Basic Transformer	365			
34.2	Loading the Secondary	366			
34.3	Effect of Resistance in the Windings	368			
34.4	Transformer Losses	369			
34.5	Phase Relationships	370			
34.6	Transformer Cores	372			
34.7	Transformer Ratings	374			
34.8	Cooling Transformers	375			
34.9	Transformer Windings	376			
34.10	Efficiency and Regulation	377			
34.11	Impedance Matching	378			
34.12	Autotransformers	380			
35	Resonant Circuits	385			
35.1	Resonance	385			
35.2	The Resonance Curve	387			
35.3	Bandwidth	389			
35.4	Reactance Curves Near Resonance	390			
35.5	The L/C Ratio	391			
35.6	Logarithms and Decibels	393			
36	Antiresonant Circuits	398			
36.1	The Antiresonant Circuit	398			
36.2	Loaded Antiresonant Circuits	400			
36.3	Bandwidth and Q	402			
36.4	Coupled and Tuned Circuits	405			
36.5	The Four Conditions of Coupling	407			
36.6	LC Oscillators	409			
36.7	Wavetraps	410			
37	Filters	414			
37.1	A Basic RC Low-pass Filter	414			
37.2	A Basic RL High-pass Filter	415			
37.3	Series Reactive Elements	416			
37.4	Low-pass and High-pass Constant-k	417			
37.5	Two-section Filters	420			
37.6	Bandpass and Bandstop Constant-k Filters	420			
37.7	m-Derived Filters	424			
37.8	Low-pass and High-pass m-Derived Filters	424			
37.9	Bandpass m-Derived Filters	426			
37.10	Coupling Filter Sections Together	427			
37.11	Balanced Filters	428			
37.12	Crystal Filters	429			
37.13	Mechanical Filters	430			
37.14	Crossover Networks	430			
37.15	Power-supply Filters	431			
	Appendixes	437			
A	Electrical Symbols	438			
B	Standard American Wire Gage in Metric and U.S. Customary Values	439			
C	Powers of Ten	441			
D	Table of Squares and Square Roots	443			
E	Table of Natural Trigonometric Functions	448			
F	Table of Common Logarithms (Four-place Mantissas)	452			
G	Table of Natural Logarithms, 0.01 to 1.0	454			
H	Greek Alphabet	454			
I	Multiples, Prefixes, and Symbols Adopted by the International Committee on Weights and Measures	455			
J	Units and Equivalents	456			
K	LCXf Nomograph	457			
	Index	461			
	Answers to Tests	473			