

CONTENTS OF VOLUME 2, PART A

CONTRIBUTORS TO VOLUME 2, PART A	xiii
FOREWORD	xv
CONTENTS OF VOLUME 2, PART B	xvii
CONTRIBUTORS TO VOLUME 2, PART B	xix

1. Passive Linear Circuit Elements and Networks

by R. M. Scarlett

1.1. Basic Principles and Terminology	1
1.1.1. The Lumped Elements R, L, C	1
1.1.2. Mutual Inductance; Transformers	2
1.1.3. Voltage and Current Sources	3
1.1.4. Kirchhoff's Laws	3
1.1.5. Complex Notation; Zeros and Poles	3
1.1.6. Relations between Time and Frequency Response	4
1.1.7. Impedance and Admittance; Series and Parallel Components	6
1.1.8. Power Relationships	7
1.1.9. DC Circuits	7
1.2. Network Theory	7
1.2.1. Network Topology	7
1.2.2. Loop Analysis	8
1.2.3. Node Analysis	9
1.2.4. The Superposition Principle	10
1.2.5. Reciprocity	10
1.2.6. Thevenin's and Norton's Theorems	10
1.2.7. Power Transfer and Impedance Matching	11
1.2.8. Simple Resonant Circuits; Duality	11
1.2.9. Simple Transients	14

1.3. Two-Terminal-Pair Networks; Filters	17
1.3.1. Network Parameters	17
1.3.2. Specific Structures	21
1.3.3. Filters	23
1.4. Distributed Constant Networks	29
1.4.1. Transmission Lines	29
1.4.2. Electromechanical Devices	32
1.5. Components	33
1.5.1. General Standards; Tolerance and Preferred Values	34
1.5.2. Resistors	34
1.5.3. Capacitors	36
1.5.4. Inductors and Transformers	38
1.6. Construction Techniques	39
1.6.1. Shielding; Skin Effect	39
1.6.2. Grounding Considerations	41
1.6.3. Component Mounting	42
1.6.4. Temperature Considerations	43
2. Semiconductor Circuit Elements	
by I. A. LESK	
2.1. Introduction	45
2.2. Discrete Semiconductor Devices	47
2.2.1. Devices Employing Bulk Semiconductor Properties	48
2.2.2. <i>P-N</i> Junction and Barrier Diodes	51
2.2.3. Transistors	67
2.2.4. Multiregion Devices	92
2.2.5. Device Symbols	99
2.2.6. Some Examples of Discrete Devices	100
2.3. Integrated Circuits (ICs)	103
2.3.1. Introduction	103
2.3.2. Monolithic Integrated Circuits	105
2.3.3. Hybrid Integrated Circuits	142

3. Vacuum Tubes

by EDWARD J. CRAIG

3.1. Thermionic Emission	147
3.1.1. The Richardson–Dushman Equation—The Schottky Effect	147
3.1.2. Types of Cathodes	148
3.1.3. Types, Operation, Physical Shapes of Cathodes	151
3.2. Diodes	152
3.2.1. General Diode Characteristics	152
3.2.2. Transit-Time Effects	154
3.3. Triodes	155
3.3.1. Description of Triodes	155
3.3.2. Characteristics of Triodes	155
3.3.3. Equivalent Circuits of Triodes	155
3.4. Multielement Tubes	158
3.4.1. Tetrodes, Pentodes, Beam Tubes	158
3.4.2. Mixers and Converters—Hexode, Heptode, Pentagrid	160
3.4.3. Secondary Electron Tubes	161
3.5. Selection of Tubes	161
3.5.1. Vacuum Tubes and Solid State	161
3.5.2. Microwave Triodes and Tetrodes	163

4. Gas Tubes

by WILLIAM J. KEARNS

4.1. Gaseous Electronic Devices	165
4.2. Gas Tube Phenomena	165
4.3. Corona Devices	167
4.3.1. Corona High-Voltage Regulator Tubes	167
4.4. Glow Devices	169
4.4.1. Voltage Regulator Tubes	169
4.4.2. Voltage Reference Tubes	171
4.4.3. Glow Indicator and Counting Tubes	172

4.5. Arc Devices	172
4.5.1. Gas Rectifiers	173
4.5.2. Thyratrons	174
4.5.3. Hydrogen Thyratrons	176
4.5.4. Ignitrons	180
4.5.5. Spark Gaps	183
4.5.6. Triggered Spark Gaps	184
4.5.7. Triggered Vacuum Gaps	184
4.6. Microwave Gas Tubes	186
4.7. Tube and Spark Gap Ratings: Definitions	186
4.7.1. Maximum Peak Inverse Voltage	186
4.7.2. Maximum Peak Forward Voltage	187
4.7.3. Maximum Average Current	187
4.7.4. Maximum Peak Anode Current	187
4.7.5. Maximum Surge Anode Current	187
4.7.6. Arc Drop or Anode Voltage Drop	188
4.7.7. Commutation Factor	188
4.7.8. Ionization Time	188
4.7.9. De-Ionization Time	188
4.7.10. Jitter	188
4.7.11. Anode Dissipation Factor	188
5. Rectifier Circuits and Power Supplies	
5.1. Rectifier Circuits	189
by ROBERT P. FEATHERSTONE	
5.1.1. Rectifiers, General	189
5.1.2. Half-Wave Circuits	193
5.1.3. Full-Wave Rectifiers with Capacitive Load	197
5.1.4. Full-Wave and Polyphase Rectifiers with Inductive Load	202
5.1.5. Voltage-Multiplying Rectifiers	207
5.1.6. DC to DC Converters	211
5.1.7. Additional Filtering of Rectifier Output	214
5.1.8. Selecting a Rectifying Device	216
5.1.9. Ratings of Rectifier Components	220

5.2. Controlled Rectifier Circuits	224
by ALLAN I. BENNETT and WILLIAM J. KEARNS	
5.2.1. Device Properties	225
5.2.2. Control Circuit Principles	228
5.2.3. Typical Controlled-Rectifier Applications	230
5.3. Regulated Power Supplies	242
by E. F. BUCKLEY	
5.3.1. Ac Voltage and Current Regulators	242
5.3.2. Dc Voltage and Current Regulators	243

6. Amplifiers

by F. H. SCHLERETH and R. J. MCFADYEN

6.1. Specification	246
6.1.1. Signal Specification	247
6.1.2. Noise Specification	250
6.1.3. Amplifier Specification	252
6.2. Basic Amplifier Stages	253
6.2.1. Single-Stage Amplifiers	253
6.2.2. Transistor Bias Circuits	256
6.2.3. Vacuum Tube and Field-Effect Transistor Bias Circuits	261
6.2.4. Equivalent Circuits	267
6.2.5. Single-Stage Transistor Amplifier Limitations	272
6.2.6. Extension to Multistage Connections; Coupling Methods	282
6.2.7. Computer-Aided Design	285
6.2.8. Summary	287
6.3. Direct Coupled Amplifiers	287
6.3.1. Definitions and General Considerations	287
6.3.2. Two-Stage Direct Coupled Amplifiers	288
6.3.3. Differential Amplifiers	292
6.3.4. Electrometer Amplifiers	298
6.3.5. Chopper Amplifiers	300
6.3.6. Summary	305

6.4. Broadband Amplifiers (Video, Pulse)	305
6.4.1. Definitions	305
6.4.2. Design Considerations	306
6.4.3. Conclusions	308
6.5. Operational Amplifiers	309
6.5.1. Definitions	309
6.5.2. Design Considerations	311
6.5.3. Conclusions	314
6.6. Tuned Amplifiers	315
6.6.1. Definitions; Basic Types; Relation to Signal Specifications	315
6.6.2. Design Considerations	317
6.6.3. Conclusions	319
6.7. Power Amplifiers .	320
6.7.1. Definitions	320
6.7.2. Design Considerations	320
6.7.3. Conclusions	324
6.8. Low-Noise Amplifiers	325
6.8.1. Definitions	325
6.8.2. Design Considerations	326
6.8.3. Summary	332
6.9. Active Filters	333
6.9.1. Definitions and General Considerations	333
6.9.2. Design Considerations	333
6.9.3. Summary	336
6.10. Modulators and Detectors	336
6.10.1. Definitions	336
6.10.2. Examples of Basic Types	337
6.10.3. Conclusions	339
7. Oscillators	
by F. H. SCHLERETH and R. J. McFADYEN	
7.1. General Considerations	341

7.2. Harmonic Oscillators	343
7.2.1. Circuit Configurations	343
7.2.2. Voltage Control	347
7.2.3. Conclusions	348
7.3. Relaxation Oscillators	348
7.3.1. General Description	348
7.3.2. Oscillators That Use Negative Resistance Devices	351
7.3.3. Astable Circuits	355
7.3.4. Summary	359
8. Nonlinear Circuits	
8.1. General Discussion	361
by F. H. SCHLERETH and R. J. McFADYEN	
8.2. Nonlinear Devices	361
by F. H. SCHLERETH and R. J. McFADYEN	
8.2.1. Junction Transistors	362
8.2.2. Field-Effect Transistors	362
8.2.3. Diodes	362
8.3. Nonregenerative Nonlinear Circuits	369
by F. H. SCHLERETH and R. J. McFADYEN	
8.3.1. Limiters	369
8.3.2. Linear Gates	377
8.3.3. Comparators	382
8.3.4. Clamping Circuits	385
8.3.5. Pulse Stretchers	389
8.3.6. Other Nonregenerative Nonlinearities	395
8.4. Regenerative Nonlinear Circuits	395
by F. H. SCHLERETH and R. J. McFADYEN	
8.4.1. Schmitt Trigger	396
8.4.2. Monostable Multivibrator	397
8.4.3. Flip-Flop (Bistable Multivibrator)	398
8.4.4. Sweep Circuits	401
8.5. Special Circuits	402
by F. H. SCHLERETH and R. J. McFADYEN	
8.5.1. Mixers, Multipliers, Square-Law Devices	402

8.5.2.	Automatic Gain Control	404
8.5.3.	Transistor Core Drivers	404
8.6.	Logic Circuits	409
	by T. A. SMAY	
8.6.1.	Logic Design	409
8.6.2.	Analog-to-Digital (A/D) Converters	416
8.6.3.	Digital-to-Analog (D/A) Converters	419
AUTHOR INDEX		423
SUBJECT INDEX		427

