

# Contents



<b>1</b>	<b>Ideal Components</b>	<b>1</b>
	The Ideal Resistor	1
	The Ideal Capacitor	3
	The Ideal Inductor	4
	The Ideal Voltage Source	5
	The Ideal Current Source	7
	The Ideal Switch	7
	The Ideal Transformer	8
	The Ideal Transmission Line	9
	Exercises	13
<b>2</b>	<b>The Laplace Transform and Its Application to Transients in Linear Circuits</b>	<b>21</b>
	Laplace Transforms of Some Simple Functions	22
	Basic Laplace Transform Theorems	22
	Inversion of the Laplace Transform	23
	Transient Response of an $R$ - $C$ Circuit	26
	Transient Response of a Series $R$ - $L$ - $C$ Circuit	29
	Transient Response of a Series-Parallel $R$ - $L$ - $C$ Circuit	33
	Transients in Ideal Transmission Lines	35
	Exercises	40
<b>3</b>	<b>Transient Response of Cascaded Circuits and Ladder Networks</b>	<b>43</b>
	The Transfer Function	43
	The Elmore Delay and the Elmore Risetime	44
		ix

**x • Contents**

Cascaded Circuits	45
Ladder Networks	47
Exercises	54
<b>4 Real Components</b>	<b>57</b>
Resistors	57
Capacitors	59
Inductors	60
Transformers	61
Transmission Lines	63
Exercises	67
<b>5 Junction Diodes</b>	<b>69</b>
Characteristics	69
Stored Charge and Capacitances	72
Body Resistance and Conductivity Modulation	73
The Diode Model	74
Transients in Junction Diode Circuits	75
Exercises	93
<b>6 Tunnel-Diodes</b>	<b>95</b>
Analysis of Tunnel-Diode Transient Using a Simplified Equivalent Circuit	97
Analysis of Tunnel-Diode Transient Using the Complete Equivalent Circuit	103
Exercises	109
<b>7 Junction Transistors</b>	<b>111</b>
The PNP Transistor	111
The NPN Transistor	114
Small-Signal Parameters	116
The Grounded Base Configuration	116
The Grounded Emitter Configuration	118

The Grounded Collector Configuration (Emitter Follower)	119
Transient Response of the Emitter Follower	121
Exercises	129
<b>8 The Emitter-Coupled Transistor Pair</b>	<b>131</b>
Computation of the Switching Transient Results	131
Exercises	137
<b>9 Digital Fanout Circuits</b>	<b>149</b>
Single-Stage Circuit	149
Two-Stage Circuit	151
Multi-Stage Circuits	152
Exercises	154
<b>10 Linear Amplifiers</b>	<b>155</b>
The Gain-Cell of Gilbert	155
Transient Response	156
Input Impedance	158
Exercises	158
<b>Answers to Selected Exercises</b>	<b>159</b>
<b>References</b>	<b>161</b>
<b>Index</b>	<b>165</b>