

Contents

1 General Background	
1.1 Need	1
1.2 Single Balance Stage	3
1.3 Common Signal Rejection	3
1.4 Differential Amplifier	5
1.5 Differential and Common Signals	5
1.6 Historical Notes	7
2 Terminal Quantities	
2.1 Comments	9
2.2 Configuration	9
2.3 Linear Analysis	10
2.4 Linear Operation	12
2.5 New Port Variables	12
2.6 Amplifier Operation	15
2.7 Signal Source	15
2.8 Signal Load	21
2.9 Signal Source-Load Combination	25
3 Single-Stage Static Design	
3.1 Introduction	28
3.2 Circuit Bisection	29
3.3 Graphical Design	30
3.4 Design Example	33
3.5 Field-Effect Transistors (FET) Circuit Design	35
3.6 Electron Tube Circuit Design	37
3.7 Source Bias Arrangements	39
3.8 Temperature Effects	39
	ix

x Contents

4 Small-Signal Operation

4.1 Comments	50
4.2 General Differential Operation	50
4.3 General Common Operation	55
4.4 Discrimination Ratios	57
4.5 Source Dissymmetry	57
4.6 Load Dissymmetry	58
4.7 General Dissymmetry	60
4.8 Recapitulation	64

5 Circuit Modifications

5.1 Comments	66
5.2 Constant-Current Source	66
5.3 Constant-Current Design Example	69
5.4 Feedback Current Source	70
5.5 Darlington Input	72
5.6 Balance Circuits	80

6 Small-Signal Performance

6.1 Comments	81
6.2 Equivalent Circuits	81
6.3 Bipolar Transistor Differential Amplifier Operation	84
6.4 Bipolar Transistor with Constant-Current Source	88
6.5 Field-Effect Transistor Differential Amplifier Operation	91
6.6 Unsymmetrical Bipolar Transistor Differential Amplifier	97

7 Large-Signal Operation

7.1 Comments	111
7.2 Without Feedback	111
7.3 With Feedback	115
7.4 Power Output	119

8 Multistage Amplifiers

8.1 Introduction	126
8.2 Basic Cascade Arrangements	126
8.3 Static Design	131
8.4 Multistage Circuit Design	131
8.5 Integrated Amplifiers	139

9 Limiting Performance	
9.1 Introduction	158
9.2 Input Bias Current	158
9.3 Gain-Bandwidth Product	159
9.4 Noise	161
9.5 Stability	172
10 Evaluation	
10.1 Introduction	176
10.2 Signal Source	176
10.3 Signal Detector	178
10.4 Input Impedance	179
10.5 Output Impedance	180
10.6 Common Voltage Amplification	180
10.7 Common To Differential Voltage Amplification	180
10.8 Differential Voltage Amplification	180
10.9 Differential To Common Voltage Amplification	181
10.10 Current Amplifications	181
10.11 Single-Ended Input Measurements	182
10.12 Single-Ended Output Measurements	183
10.13 Single-Ended Input And Output Measurements	184
10.14 Noise Factor Measurements	186
Appendix I Definitions	191
Appendix II Small-Signal Operation of an Unsymmetrical Differential Amplifier	199
Appendix III Noise Factor of an Unsymmetrical Differential Amplifier	208
Selected Bibliography	216
Index	223