

# Contents

<i>Preface</i>	7
<i>Principal symbols</i>	11
1 TRANSISTOR PHYSICS	1
2 SMALL-SIGNAL EQUIVALENT CIRCUITS	25
3 BIASING CIRCUITS	89
4 SINGLE STAGE AMPLIFIERS	98
5 MULTISTAGE AMPLIFIERS	148
6 POWER AMPLIFIERS	182
7 NEGATIVE FEEDBACK AMPLIFIERS	208
8 TUNED AMPLIFIERS	317
9 SINUSOIDAL OSCILLATORS	341
10 NEGATIVE IMPEDANCE CONVERTERS	367
11 LARGE SIGNAL RESPONSE	386
12 SWITCHING CIRCUITS	418
<i>Appendixes</i>	
1 TRANSIENT RESPONSE	483
2 STEADY STATE RESPONSE	488
3 ANALYSIS OF 4-POLE NETWORKS	492
4 TRANSISTOR $h$ -PARAMETERS	502
ANSWERS TO PROBLEMS	509
<i>Index</i>	515