

Contents

1.	Introduction	1
2.	Radiation Detectors and Related Circuits	4
2.1.	Ionization Chamber	4
2.1.1.	Energy Required for the Generation of One Charge Carrier Pair	5
2.1.2.	Mobility of the Charge Carriers	6
2.1.3.	The Pulse Shape	6
2.1.4.	Preamplifier Circuits	11
2.2.	Proportional Counters	14
2.2.1.	Detection Mechanism and Pulse Shape in the Proportional Counter	14
2.2.2.	Statistics of the Multiplication Process	16
2.2.3.	Preamplifier Circuits	17
2.3.	Geiger-Müller-Counters	20
2.3.1.	Detection Mechanism and Pulse Shape in the GM Counter	20
2.3.2.	Quenching Circuits	24
2.4.	Semiconductor Detectors	27
2.4.1.	Characteristic Properties of Semiconductor Detectors	27
2.4.2.	Energy Required to Form a Hole-Electron Pair	31
2.4.3.	The Pulse Shape in the <i>pn</i> and <i>pin</i> Detectors	34
2.4.4.	Preamplifiers and Related Circuits	38
2.5.	Scintillation and Čerenkov Counters	48
2.5.1.	Principle of a Scintillation Counter	48
2.5.2.	The Pulse Shape	51
2.5.3.	Photomultiplier Statistics and the Pulse Height	55
2.5.4.	Thermal Noise	56
2.5.5.	Signal Circuits Used in Scintillation Counters	60
2.5.6.	Auxiliary Circuits	66
2.5.7.	Scintillation Counter Stabilizer Circuits	70
2.5.8.	Čerenkov Counter	74

Contents

3.	Analog Circuits	75
3.1.	Linear Pulse Amplifiers	75
3.1.1.	General Considerations, Linearity	76
3.1.2.	The Transient Response of an Amplifier	84
3.1.3.	Pulse Shaping	90
3.1.4.	Sum Effects	106
3.1.5.	Overload Recovery	111
3.1.6.	Practical Design Criteria	114
3.1.7.	Amplifiers with Variable Gain	115
3.2.	Arithmetic Operations on Analog Signals	117
3.2.1.	Operational Amplifiers	117
3.2.2.	Arithmetic Operations on Pulse Amplitudes	120
3.2.3.	Practical Circuits	122
3.3.	Window Amplifiers	128
3.4.	Linear Gates	131
3.5.	Pulse Stretchers	137
3.6.	Fast Pulse Amplifiers	142
4.	Analog-to-Digital Converters	151
4.1.	Pulse Height Discriminators	152
4.1.1.	The Principle of a Multivibrator	152
4.1.2.	Integral Discriminators	158
4.1.3.	Differential Discriminators	169
4.1.4.	Multiple Arrays of Differential Discriminators	177
4.1.5.	Conservation of the Time Information in a Discriminator	179
4.1.6.	Fast Tunnel Diode Discriminators	183
4.2.	Digital Encoding of the Pulse Height	191
4.2.1.	Converters of the Wilkinson Type	192
4.2.2.	Other Converter Systems	201
4.3.	Pulse Shape Discriminators	205
5.	Evaluation of the Time Information	213
5.1.	General Considerations, Resolution	213
5.2.	Pulse Shapers for Coincidence Circuits and Time-to-Digital Converters	217
5.3.	Coincidence Circuits	227
5.3.1.	Ideal Coincidence Stage	227
5.3.2.	Practical Circuits	231

5.3.3.	The Chronotron Principle	240
5.4.	Digital Encoding of the Time Interval	243
5.4.1.	Direct Digital Encoding	244
5.4.2.	Principle of a Time-to-Pulse-Height Converter	246
5.4.3.	Start-Stop Converter	250
5.4.4.	Overlap Converter	256
5.4.5.	The Vernier Principle	261
5.5.	Auxiliary Circuits	264
6.	Digital Circuits	268
6.1.	Basic Digital Circuits	269
6.1.1.	Fundamentals of Boolean Algebra, Gates	269
6.1.2.	Circuitry of Different Logics	278
6.1.3.	The Flip-Flop	286
6.1.4.	Practical Flip-Flop Circuits	290
6.1.5.	Tunnel Diode Circuits	292
6.2.	Scalers and Registers	296
6.2.1.	Shift Registers	296
6.2.2.	Pulse Scalers	299
6.3.	Logical and Arithmetical Digital Circuits	308
6.4.	Memories	316
6.5.	Data Output	320
6.6.	Count Rate Meters	324
7.	Data Processing	327
7.1.	Simple Counting Systems	327
7.2.	Multiscaler Arrays	329
7.3.	Multichannel Analyzers	332
7.4.	Multiparameter Analyzers	336
7.5.	On-Line Computers	342
8.	Appendix	347
8.1.	Laplace Transform Calculus	347
8.1.1.	Networks	347
8.1.2.	Naive Operational Calculus	350
8.1.3.	Laplace Transformation	354
8.1.3.1.	Rules of the Laplace Transformation	355

Contents

8.1.3.2. Application of the Laplace Transformation in the Network Analysis.	357
8.1.3.3. Inverse Transformation of Rational Functions $F(p)$	359
8.1.3.4. Stability Considerations	361
8.1.3.5. Approximations	361
8.2. Noise	364
8.2.1. General Considerations, Concept of Equivalent Noise Charge	364
8.2.2. Noise Sources	365
8.2.3. The Noise of an Amplifier with the Transfer Function $G(p)$	366
8.2.4. Noise in a Charge Sensitive Amplifier	368
8.2.5. Properties of Input Stages with Vacuum Tubes, Bipolar Transistors and FET	370
8.2.6. Noise and Resolution	373
9. References	377
10. Subject Index	399