

Contents

Preface	v		
1. Alarm circuits	1	51. Modulator circuits	393
2. Amplifier circuits	8	52. Motor control circuits	404
3. Analog circuits	30	53. Multiplier circuits	413
4. Audio circuits	38	54. Multivibrator circuits	417
5. Automatic frequency control circuits	54	55. Noise circuits	439
6. Automatic gain control circuits	57	56. Oscillator circuits	447
7. Automotive circuits	65	57. Phase control circuits	465
8. Battery charging circuits	72	58. Photoelectric circuits	475
9. Beacon circuits	76	59. Photography circuits	485
10. Bridge circuits	81	60. Power supply circuits	491
11. Capacitance control circuits	85	61. Preamplifier circuits	497
12. Cathode ray circuits	89	62. Protection circuits	501
13. Character generator circuits	100	63. Pulse amplifier circuits	511
14. Chopper circuits	103	64. Pulse generator circuits	516
15. Clock circuits	109	65. Pulse height analyzer circuits	533
16. Comparator circuits	114	66. Pulse processing circuits	537
17. Computer circuits	120	67. Pulse shaping circuits	541
18. Control circuits	127	68. Radar circuits	545
19. Converter circuits	138	69. Radiation circuits	558
20. Counter circuits—objects	148	70. Receiver circuits	568
21. Counter circuits—pulses	151	71. Recorder circuits	581
22. Current control circuits	167	72. Regulated power supply circuits	588
23. D-c amplifier circuits	172	73. Remote control circuits	615
24. Delay circuits	178	74. Sampling circuits	623
25. Demodulator circuits	190	75. Sawtooth generator circuits	629
26. Differential amplifier circuits	193	76. Scanner circuits	639
27. Discriminator circuits	200	77. Servo circuits	643
28. Display circuits	204	78. Shift register circuits	664
29. Electronic heating circuits	209	79. Signal generator circuits	669
30. Electronic music circuits	213	80. Simulator circuits	677
31. Filter circuits	216	81. Staircase generator circuits	685
32. Flash circuits	223	82. Stereo circuits	689
33. Flip-flop circuits	231	83. Sweep circuits	696
34. Frequency divider circuits	240	84. Switching circuits	703
35. Frequency measuring circuits	246	85. Tape recorder circuits	714
36. Frequency modulation circuits	250	86. Telemetry circuits	723
37. Frequency multiplier circuits	256	87. Television camera circuits	734
38. Function generator circuits	265	88. Television circuits—black-and-white	739
39. Gate circuits	269	89. Television circuits—color	747
40. I-f amplifier circuits	281	90. Temperature control circuits	755
41. Infrared circuits	289	91. Test circuits	764
42. Integrated circuits	295	92. Timer circuits	783
43. Integrator circuits	306	93. Transceiver circuits	792
44. Inverter circuits	313	94. Transmitter circuits	796
45. Latching circuits	327	95. Trigger circuits	807
46. Limiter circuits	330	96. Tuner circuits	821
47. Logic circuits	335	97. Ultrasonic circuits	825
48. Magnetic amplifier circuits	350	98. Video circuits	838
49. Measuring circuits	356	99. Voltage measuring circuits	850
50. Medical circuits	377	100. Welding circuits	859
		Index	865