

# Contents

<b>I. Device Models</b>	<b>1</b>
1.1 <i>p-n</i> Junction Diodes,	1
1.2 Junction Transistors,	3
Large-Signal Static Characteristics,	3
Large-Signal Dynamic Characteristics,	7
Small-Signal Characteristics,	10
1.3 Junction Gate Field Effect Transistors,	14
1.4 Insulated Gate Field Effect Transistors,	18
1.5 Tunnel Diodes,	21
1.6 Passive Devices,	22
1.7 Parasitic Elements,	26
<b>2. The Quiescent Point</b>	<b>29</b>
2.1 Device Parameters,	29
2.2 Specified Power Design,	30
Emitter Degeneration,	30
Emitter and Collector Degeneration,	32
Collector Degeneration and Diode Compensation,	32
Transistor Compensation,	35
Emitter Coupled Pair,	35
Feedback Pair,	35
Multistage Direct Coupled Circuits,	36
2.3 Specified Stability Design,	36
2.4 Effects of Imperfect Element Isolation,	37

**3. Low-Frequency Amplifiers**

3.1 Input Stages, 42

Impedance Matching, 42

Minimum Loading, 43

FET Inputs, 45

3.2 Intermediate Stages, 46

Specified Number of Stages, 46

Specified Total Resistance, 48

3.3 Driver Stages, 50

Basic Design, 52

Low-Distortion Design, 53

Transformer Coupling, 54

3.4 Output Stages, 56

Class B Transformer Coupled Circuits, 57

Class B Complementary Symmetry Circuits, 59

A Monolithic Hearing Aid Amplifier, 59

A Monolithic Acoustic Horn Amplifier, 61

3.5 Class D or Two-State Amplifiers, 61

**4. Wideband Amplifiers**

4.1 Input Stages, 67

4.2 Intermediate Stages, 69

Bipolar Transistor Circuits, 69

FET Circuits, 77

4.3 Output Stages, 81

**5. Tuned Amplifiers**

5.1 The Iterative Stage, 84

Gain, 84

Center Frequency, 86

Bandwidth, 87

Stability, 87

5.2 The Common Emitter Amplifier, 89

5.3 The Cascode Amplifier, 92

5.4 A Monolithic Tuned Amplifier, 96

**6. Low-Noise Amplifiers**

6.1 A Transistor Noise Model, 98

6.2 Noise Figure, 99

6.3 Low-Frequency Amplifiers, 101

Flicker Noise Region, 101

Shot Noise Region, 101

6.4 High-Frequency Amplifiers,	103
6.5 Monolithic Low-Noise Amplifiers,	108
<b>7. Mixers and Detectors</b>	<b>110</b>
7.1 Mixers,	110
The Equivalent Circuit of a Mixer,	110
Mixer Noise Figure,	113
Conversion Gain,	115
7.2 A Monolithic Mixer,	116
7.3 Detectors,	116
<b>8. Feedback Amplifiers</b>	<b>121</b>
8.1 Sensitivity,	121
Local Emitter Feedback,	123
Local Emitter and Collector Feedback,	126
Alternate Emitter and Collector Feedback Stages,	128
Multistage Feedback,	129
8.2 Distortion,	130
8.3 Bandwidth,	131
8.4 Stability,	132
8.5 Quiescent Power,	133
<b>9. Harmonic Oscillators</b>	<b>134</b>
9.1 Simplified Design,	134
Common-Emitter Hartley Oscillator,	135
Common-Base Hartley Oscillator,	138
9.2 Generalized Design,	140
9.3 Micropower Monolithic Oscillators,	143
<b>10. Direct Current Amplifiers</b>	<b>145</b>
10.1 DC Gain,	145
10.2 Common-Mode Rejection,	147
10.3 Input Offset Voltage,	150
10.4 Drift,	151
10.5 Noise,	152
10.6 Frequency Response,	153
10.7 A Monolithic Micropower dc Amplifier,	154
10.8 A Micropower Operational Amplifier,	154
<b>11. Bipolar Transistor Digital Circuits</b>	<b>157</b>
11.1 The Basic Inverter Circuit,	157
Static Behavior,	157
Dynamic Behavior,	161

<b>11.2</b>	An Iterative Chain of Inverters,	169
<b>11.3</b>	Resistor Transistor Logic (RTL),	173
	Worst Case Analysis,	173
	Performance Trade-Offs,	180
	Storage Circuits,	183
<b>11.4</b>	Transistor Resistor Logic (TRL),	186
<b>11.5</b>	Diode Transistor Logic (DTL),	187
<b>11.6</b>	Transistor Transistor Logic (TTL),	189
<b>11.7</b>	Emitter Coupled Logic (ECL),	190
<b>11.8</b>	Tunnel Device Logic (TDL),	193
<b>11.9</b>	Complementary Diode Transistor Logic (CDTL),	196
<b>11.10</b>	Pulse Powered Circuits (PPC),	201
<b>12.</b>	<b>Field Effect Transistor Digital Circuits</b>	<b>210</b>
<b>12.1</b>	The FET Inverter,	210
	Linear Resistor Loads,	210
	Depletion Transistor Loads,	216
	Enhancement Transistor Loads,	217
	Complementary Transistor Loads,	218
	Junction Gate Field Effect Transistor Inverters,	222
<b>12.2</b>	Logic Circuits	223
<b>12.3</b>	Storage Circuits,	226
<b>12.4</b>	Multiphase Dynamic Circuits,	229
	Two-Phase Circuits,	231
	Four-Phase Circuits,	233
<b>13.</b>	<b>Applications</b>	<b>238</b>
<b>13.1</b>	Portable Equipment,	238
<b>13.2</b>	Aerospace Electronics,	241
<b>13.3</b>	Biomedical Electronics,	243
<b>List of Symbols</b>		<b>247</b>
<b>Index</b>		<b>259</b>