

# CONTENTS

	Preface	<i>ix</i>	
chapter	<b>1</b>	Review of Selected Topics in Electronic Circuit Theory	<b>1</b>
	<b>2</b>	Linear Wave Shaping: <i>RC</i> , <i>RL</i> , and <i>RLC</i> Circuits	<b>27</b>
	<b>3</b>	Pulse Transformers and Delay Lines	<b>64</b>
	<b>4</b>	Wideband Amplifiers (Uncompensated)	<b>111</b>
	<b>5</b>	Wideband Amplifiers (Compensated)	<b>147</b>
	<b>6</b>	Steady-state Switching Characteristics of Devices	<b>179</b>
	<b>7</b>	Clipping and Comparator Circuits	<b>225</b>
	<b>8</b>	Clamping and Switching Circuits	<b>262</b>
	<b>9</b>	Logic Circuits	<b>306</b>
	<b>10</b>	Bistable Multivibrators	<b>362</b>
	<b>11</b>	Monostable and Astable Multivibrators	<b>404</b>
	<b>12</b>	Negative-resistance Devices	<b>452</b>

<b>chapter</b>	<b>13</b>	<b>Negative-resistance Switching Circuits</b>	<b>476</b>
	<b>14</b>	<b>Voltage Time-base Generators</b>	<b>514</b>
	<b>15</b>	<b>Current Time-base Generators</b>	<b>571</b>
	<b>16</b>	<b>Blocking-oscillator Circuits</b>	<b>597</b>
	<b>17</b>	<b>Sampling Gates</b>	<b>627</b>
	<b>18</b>	<b>Counting and Timing</b>	<b>668</b>
	<b>19</b>	<b>Synchronization and Frequency Division</b>	<b>716</b>
	<b>20</b>	<b>Transient Switching Characteristics of Diodes and Transistors</b>	<b>745</b>
<b>appendix</b>	<b>A</b>	<b>Ringling Circuit with Nonzero Initial Conditions</b>	<b>795</b>
	<b>B</b>	<b>Distributed-parameter Delay Lines</b>	<b>798</b>
	<b>C</b>	<b>Lumped-parameter Delay Lines</b>	<b>800</b>
	<b>D</b>	<b>Tube Characteristics</b>	<b>809</b>
		<b>Problems</b>	<b>815</b>
		<b>Index</b>	<b>951</b>