

# CONTENTS

---

---

1	INTRODUCTION	1
2	PHYSICS OF ELECTRON DEVICES	5
	Energy-Level Diagrams of Atoms, 5. Energy-Level Diagrams of Gases and Solids, 9. Semiconductor Structure; Conduction in Semiconductors, 13. Holes and Hole Current, 15. Conduction in Intrinsic Semiconductors and Insulators, 17. <i>N</i> -type and <i>P</i> -type Semiconductors, 19. Fermi Probability Function, 24. Fermi Level and Equilibrium Charge Densities in Intrinsic Semiconductors, 25. Fermi Level in Extrinsic Semiconductors, 29. Constancy of the $p \cdot n_0$ Product, 30. Conduction in Metals, 31. Electron Affinity and Work Function; Contact Difference of Potential, 32. Electron Emission from Solids into Space; Thermionic Emission, 34. Richardson's Equation, 36. Practical Thermionic Emitters, 38. Photoelectric Effect, 40. Secondary Emission; Field Emission; Radioactive-Disintegration Emission, 43. Dynamics of Charge Carriers in Space and in Semiconductors, 44. Diffusion Coefficient, Mobility, and Lifetime, 45. Relations Between Mobility, Diffusion Constant, and Conductivity, 47. The Continuity Equation, 49. Applications of the Continuity Equation, 51.	
3	THEORY OF SEMICONDUCTOR DIODES	61
	Physical Explanation of <i>P-N</i> -Junction Barrier Potential, 61. The <i>P-N</i> Diode at Zero Applied Voltage, 65. Effect of Voltage Applied to a <i>P-N</i> Junction, 66. Rectification by a <i>P-N</i> Junction, 69. Energy-Band Diagram for a <i>P-N</i> Junction, 74. Derivation of the <i>P-N</i> Diode Current-Voltage Equation, 75. Carrier Injection as a Function of Junction Voltage, 77. Departures of Diode Characteristics from the Theoretical Form, 78. Breakdown Diodes, 80. <i>P-N</i> -Junction Variational Resistance, 81. Junction Capacitance, 81. Diffusion Capacitance, 83. Junction-Diode Transients, 84. Tunnel (Esaki) Diodes, 87.	
4	VACUUM DIODES	97
	Introduction, 97. Types of Cathodes, 97. Child's Law, 98. Diode Dissipation, 101. Voltage Ratings, 102.	
5	ELECTRICAL CONDUCTION IN GASES	103
	Types of Electric Discharges in Gases, 103. Theory of Glow Discharge, 104. Normal and Abnormal Glow Discharge, 109. Potential Distribution in the Glow Discharge, 110. Paschen's Law, 112. Breakdown, 113. Dynamic Current-Voltage Characteristics, 114. Grid Control of Glow Discharge, 114. Arcs, 118. Mercury-pool Arc Tubes, 119. Heated-Cathode Arc Tubes, 121. Grid Control of Heated-cathode Arc Tubes, 123.	

6	TRANSISTORS	128
	Basic Junction-Transistor Structure, 128. Physical Explanation of Transistor Operation, 129. Transistor Currents, 129. Current Amplification Factor, 131. Junction-Transistor Characteristics, 133. Effect of Temperature on Transistor Characteristics, 137. Voltage, Current, and Dissipation Limits, 138. Junction and Diffusion Capacitance, 139. Carrier Storage and Transient Behavior, 139. Transistor Fabrication, 142. Phototransistors, 145. The Field-Effect Transistor, 146. Structure and Characteristics of $P-N-P-N$ Devices, 148.	
7	GRID-CONTROLLED VACUUM TUBES	156
	Introduction, 156. Theory of Grid Control, 157. Triode Plate Current, 157. Triode Characteristic Curves, 158. Tube Parameters, 159. Remote-cutoff Structure, 160. Interelectrode Capacitance and Transit-Time Effects, 161. The Screen-grid Tetrode, 162. The Pentode, 163. The Beam Pentode, 164. Multigrid Tubes, 165. Vacuum Phototubes, 165.	
8	RECTIFICATION AND POWER CONTROL	167
	Introduction, 167. Basic Rectifier Circuits, 167. Smoothing Filter, 170. Capacitor Filter, 171. Inductor Filter, 173. Inductor-Input Filter, 175. Capacitor-Input Filters, 177. Multisection Filters, 178. Special-Purpose Rectifier Circuits, 178. Voltage Stabilizers, 180. Controlled-Rectifier Supply, 184. Circuits for Controlled Rectifiers, 184. Controlled Rectifier with Inductive Load, 190. Additional Control Circuitry, 193. Considerations in Thyatron-Circuit Design, 195. Considerations in Silicon Controlled Rectifier Circuit Design, 195. Ignitron Circuits, 197. Controlled Rectifiers with DC supply, 198. Inverter Circuits, 201.	
9	GRAPHICAL METHODS	205
	The Operating Point and Basic Biasing Methods, 205. Superposition of Direct and Alternating Quantities, 207. Definition of Letter Symbols, 208. Load Lines, 210. Use of Load Lines to Determine Amplification, 212. Efficiency and Dissipation, 214. Distortion, 214. Shift of the Operating Point, 217. Selected-Point Method of Harmonic Analysis, 219. Distortion Factor, 223. Causes of Operating-Point Instability, 223. Temperature Stabilization of Transistor Circuits, 226. Temperature Stabilization by Temperature-Sensitive Elements, 229.	
10	UNTUNED POWER AMPLIFIERS	233
	Introduction, 233. Class of Operation and Efficiency, 233. Limiting Factors in Power Amplifiers, 235. Thermal Calculations for Transistors, 238. Class A Single-Ended Amplifiers—Output Power and Efficiency, 241. <i>Case 1: Small-Signal Linear Device</i> , 243. <i>Case 2: Load Line Bounded by <math>I_{\min}</math> and <math>V_{\min}</math>, and Centered on a Specific Operating Voltage</i> , 244. <i>Case 3: Load Line Tangent to the <math>P_a</math> line; Point A on the Current Axis; Point B on the Voltage Axis</i> , 246. <i>Case 4: Load Line Tangent to the <math>P_a</math> line; Point A on the <math>V_{\min}</math> (or <math>R_{\text{sat}}</math>) Line; Point B on the Voltage Axis</i> , 247. <i>Case 5: Identical with Case 4</i>	

except that  $V_B = V_{max}$ , 248. Case 6: Load Line Bounded by  $P_a$ ,  $R_{at}$ ,  $V_{max}$ , and  $I_{min}$ , 248. Summary, 249. Input Distortion in Class A Transistor Amplifiers, 250. Class A Push-Pull Amplifiers, 253. Graphical Analysis of Push-Pull Amplifiers, 257. Class AB and Class B Push-Pull Amplifiers, 261. Class B Amplifier Efficiency and Output Power, 263. The Complementary-Symmetry Amplifier, 268. Crossover Distortion in Class B Push-Pull Amplifiers, 269. Power Gain in Amplifiers, 271. Bias Circuits for Power Amplifiers, 272. Power-Supply and Transformer Resistance, 275. Other Amplifier Configurations, 276.

## 11 TUNED POWER AMPLIFIERS AND HARMONIC GENERATORS 279

Introduction, 279. Power Amplifiers with Tuned Load Networks, 280. Class B Tuned Amplifiers, 281. Class C Amplifiers, 284. Grid Bias for Class C Vacuum-tube Amplifiers, 286. Choice of Operating Conditions for the Class C Amplifier, 287. Determination of the Grid Bias, 289. Output Networks for Class C Amplifiers, 290. *Parallel LC Network*, 291. *Pi Network*, 292. Neutralization of Class C Amplifiers, 293. Calculation of Performance, 296. Fourier-Analysis of a Pulse Current Waveform, 297. Harmonic Generators, 299. Transistor Class C Amplifiers, 302. Series-Tuned Saturating Transistor Amplifiers, 303. Varactor Frequency Multipliers, 306.

## 12 SMALL-SIGNAL ANALYSIS OF AMPLIFIERS 310

Introduction, 310. Two-port Networks, 310. Measurements of Parameters, 313. Relations Among Parameters, 314. Basic Amplifier Configurations and Analysis, 315. Tee and Pi Equivalent Circuits, 320. Dependence of Parameters Upon Operating Condition, 321. Voltage, Current, and Power Amplification, 324. Input and Output Impedance, 326. High-Frequency Operation, 328.

## 13 SMALL-SIGNAL-AMPLIFIER CHARACTERISTICS 336

Introduction, 336. Direct Coupling and Compound Connection, 337. RC-Coupled Amplifiers, 340. Design Considerations for RC-Coupled Transistor Stages, 348. Design Considerations for RC-Coupled Vacuum-Tube Stages, 350. Additional Design Considerations, 352. Use of Common-Collector or Common-Plate Stages in Multistage Amplifiers, 355. Low-Frequency Compensation, 356. High-Frequency Compensation by Shunt Peaking, 357. High-Frequency Compensation by Series Peaking, 361. Transformer-Coupled Stages, 363. Basic Forms of Tuned Stages, 367. RC-Coupled Tuned Stages, 368. Transformer-Coupled Tuned Stage, 370. Double-Tuned Stage, 371. Phase Inverters, 375. Distributed Amplifiers, 376. Impedance Converters, 377.

## 14 FEEDBACK AMPLIFIERS 380

Introduction, 380. Block-Diagram Analysis, 381. Modification of Amplification, 382. Reduction of Noise and Distortion, 383. Modification of Impedance or Admittance Levels, 385. Identification of  $A$  and  $\beta$ , 387. Vacuum-tube Example, 391. Stability, 393. Nyquist Diagram, 395. Equalizers, 397.

- 15 **NEGATIVE-RESISTANCE CIRCUITS** 405
- Introduction, 405. Examples of Negative-Resistance Circuits, 407. Criteria for Voltage-Stable and Current-Stable Ports, 409. The Basic Negative-Resistance Circuits, 412. Transistor Negative-Resistance Circuits, 414. Determination of Current-Voltage Characteristics by Inspection, 420.  $P-N-P-N$  Transistors and Diodes, 423. Vacuum-Tube Negative-Resistance Circuits, 424. The Unijunction Transistor and the Tunnel Diode, 427.
- 16 **MULTISTABLE CIRCUITS** 434
- Stability of Equilibrium Points, 434. Transition Between States of Equilibrium, 438. The Eccles-Jordan Bistable Circuit, 440. Triggering of the Eccles-Jordan Circuit, 443. Commutation of the Eccles-Jordan Circuit, 444. Speed of Transition of Tube Eccles-Jordan Circuits, 448. Binary Counting Circuits, 452. Decade Counters, 454.
- 17 **ASTABLE AND MONOSTABLE CIRCUITS** 459
- Analysis of Negative-Resistance Circuits Containing both  $L$  and  $C$ , 459. Graphical Analysis of Astable and Monostable Circuits, 465. Typical Paths of Operation for Astable Circuits, 467. Effect of Change of  $C/L$  Ratio, 469. Paths of Operation for Astable Circuits Based upon Voltage-Stable Elements, 471. Synthesis of Astable Circuits, 472. The Multivibrator, 474. Waveforms of Multivibrator Voltages and Currents, 477. Variants of the Multivibrator, 479. Multivibrator Oscillation Frequency, 480. Synchronization of Relaxation Oscillators, 483. Monostable Circuits, 484. Analysis of the One-shot Multivibrator, 486. Sawtooth-Voltage Generators, 488. Frequency of Oscillation of the Sawtooth-Wave Oscillator, 491. Effect of Changes of  $R$ ,  $C$ , and  $V_s$ , 493.
- 18 **SINE-WAVE OSCILLATORS** 496
- One-Port and two-Port Sine-Wave Oscillators, 496. Desired Features of Sine-Wave Oscillators, 496. *Harmonic Content, Frequency Stability, and Amplitude Stability*, 497. Analysis of One-Port Oscillators, 498. Determination of  $R_i$  or  $G_i$ , 501. Type of Resonator Required, 502. Dynamic Negative-Resistance Circuits, 503. Shunt and Series Equivalent Circuits, 503. Amplitude Limitation of Parallel-Resonator Negative-Resistance Oscillators, 504. Amplitude Hysteresis, 506. Minimization of Harmonic Content, 507. Amplitude Stabilization, 508. Frequency Stability of Negative-Resistance Oscillators, 511. Multifrequency Oscillation, 512. Admittance Diagram, 516. Practical Negative-Resistance Oscillators, 517. Feedback (Two Port) Oscillators, 519. Analysis of Circuits in Which  $y_i$  and  $y_r$  Are Small, 521. Admittance Diagrams for Feedback Oscillators, 523. Parallel-Resonator Feedback Oscillators (Tuned Output, Tuned-Input, Hartley, and Colpitts Circuits), 525. Frequency of Oscillation and Criterion for Oscillation of Parallel-Resonator Feedback Oscillators, 530. Amplitude Limitation in Feedback Oscillators, 532. Frequency Stability of Feedback Oscillators, 537. Null-Network Oscillators, 540. Wien-Bridge Oscillator, 541. Ladder-Network (Phase Shift) Oscillators, 543. Sum- and Difference-Circuit Oscillators, 545. Crystal-Controlled Oscillators, 546. Beat-Frequency (Heterodyne) Oscillators, 549.

- 19 FUNCTIONAL CIRCUITS 555
- Simulation of Nonlinear Circuits by Means of Diodes and Resistances, 555. Summing Amplifiers, 562. Differential Amplifier, 564. Differentiating Circuits, 566. Effect of Source Resistance and Load Capacitance upon Differentiators, 568. Inverse-Feedback Differentiator, 570. Integrating Circuits, 572. Stabilized DC Amplifier for Adding, Differentiating, and Integrating Circuits, 575. Clippers (Amplitude Comparators), 577. Clamping Circuits, 581. Pulse Sharpeners and Stretchers, 584. Electronic Switches (Gates), 585. Diode Gates, 586. Cathode-Follower Gate; Special Gate Tubes, 588. Transistor Switches, 589. Common-Emitter and Common-Collector Switches, 591. Circuit Modifications, 593. Special Considerations in the Use of Switching Transistors, 597. *Or* Circuits, *And* (Coincidence) Circuits, and *Not* (Anticoincidence) Circuits, 597.
- 20 AMPLITUDE MODULATION AND DETECTION 608
- Introduction, 608. General Modulation Theory, 608. Characteristics of Amplitude Modulation, 610. Frequency Spectrum and Power Relations in Amplitude Modulation, 611. Double-Sideband and Single-Sideband Systems, 613. Amplitude Modulators, 615. Amplitude Modulation by Curvature of Characteristics, 616. *Mathematical Analysis*, 617. Balanced Modulators, 619. Modulation by Rectification or Switching, 620. Diode-Bridge (Balanced) Modulators, 627. Linear Power Modulators, 628. Plate-Modulated Class C Amplifier, 629. Grid and Cathode Modulation, 633. Collector Modulation of Transistors, 636. Detection of Amplitude-Modulated Waves, 641. *SSB Detection*, 641. *DSB Detection*, 642. Diode Envelope Detectors, 642. Negative-Peak Clipping in Envelope Detectors, 645. Diode Detector Efficiency and Input Resistance, 647. Signal-to-Interference Ratio in Envelope Detectors, 648. Frequency Converters, 650.
- 21 ANGLE MODULATION AND DETECTION 658
- Introduction, 658. Angle Modulation, 659. PM and FM Waves with Sinusoidal Modulating Functions, 661. *Phasor Diagrams*, 662. Spectra of Angle-Modulated Waves, 663. Phase Modulation vs. Frequency Modulation, 667. Generation of Frequency-Modulated Waves, 670. Direct Frequency Modulation, 671. *Frequency Stabilization in a Direct-FM System*, 674. Indirect Frequency Modulation, 676. Detection of Frequency-Modulated Waves, 678. Discriminator, 679. Ratio Detector, 682. Interference Suppression in FM Detection, 684.
- 22 PULSE MODULATION 690
- Introduction, 690. The Sampling Principle, 691. Pulse Amplitude Modulation (PAM), 692. *Detection of PAM Waves*, 694. Pulse Time Modulation, 695. Pulse Code Modulation, 697. *Pulse Regeneration*, 697. *Pulse Coding*, 697. *Quantization*, 698. Detection, Synchronization, and Signal-to-Noise Ratio, 699. *Signal-to-Noise Ratio*, 700. Description of a PCM System, 701.

---

23	NOISE	705
	Introduction, 705. Noise Power and Noise Figure (Noise Factor), 706. Thermal Noise and Noise Equivalent Bandwidth, 708. Available Noise Power, Noise Temperature, 710. Shot Noise and Flicker Noise, 711. <i>Noise in Vacuum Tubes</i> , 711. <i>Noise in Semiconductor Diodes</i> , 713. <i>Noise in Transistors</i> , 714. <i>Summary</i> , 715.	
	APPENDIX	718
	SYMBOL INDEX	723
	INDEX	728