
CONTENTS

<i>Preface</i>	vii
<i>Chapter</i> 1 Characteristics of Electron Devices	1
2 Vacuum Triodes and Transistors as Circuit Elements	61
3 Basic Amplifier Principles	89
4 Untuned Potential Amplifiers	112
5 Feedback in Amplifiers	147
6 Rectifiers	194
7 Power Supplies	215
8 Electronic Computing Circuits	246
9 Special Electronic Circuits	282
10 Untuned Power Amplifiers	313
11 Tuned Potential Amplifiers	338
12 Tuned Power Amplifiers	367
13 Oscillators	398
14 Heavily Biased Relaxation Circuits	452
15 Saw-tooth Sweep Generators	504
16 Special Sweep Generators	527
17 Amplitude Modulation	546
18 Demodulation	574
19 Frequency Modulation and Detection	600
20 Electronic Instruments	640
<i>Appendix</i> A Network Theorems	659
B Plate Characteristics of Vacuum Tubes	661
C Characteristics of Transmitting Tubes	678
D Table of Bessel Functions of the First Kind	680
<i>Index</i>	681