

Contents

1. NETWORK DESCRIPTION

1.1 The Signal	1
1.2 Two-Ports	5
1.3 Two-Port Description	7
1.4 Matrix Description of Networks	14
1.5 Three-terminal Networks	20
1.6 Impedance, Hybrid and Transmission Parameters	29
1.7 n -Terminal Networks and n -Ports	36
1.8 Problems	46

2. NETWORK MODIFICATION

2.1 Parallel Connection of Terminals and Ports	49
2.2 Unconnected Terminals and Ports	56
2.3 Short-circuit of Terminals	61
2.4 Neglect of Terminals and Ports	62
2.5 Introduction of Ideal Transformers	66
2.6 General Network Embedding	68
2.7 Problems	72

3. NETWORK SOLUTION AND PROPERTIES

3.1 Introduction	74
3.2 Determinants	75
3.3 Solution of Simultaneous Linear Equations	79
3.4 Solution of an n -Terminal Network	82
3.5 n -Terminal Network Solution: Theory	88
3.6 n -Port Network Solution	93

3.7 Properties of Two-Ports	96
3.8 Power Gain	105
3.9 Problems	109
4. ACTIVITY	
4.1 Signal Power	112
4.2 Definition of Activity	115
4.3 Condition for Activity	116
4.4 Characterization of Activity	121
4.5 Matrix Properties Associated with Activity	127
4.6 Matrix Description of Activity	131
4.7 Problems	136
5. NONRECIPROCITY	
5.1 Tellegen's Theorem	139
5.2 Reciprocity	145
5.3 Generalized Form of Tellegen's Theorem	150
5.4 The Gyrator	153
5.5 Antireciprocity	156
5.6 Models of Nonreciprocal Devices	158
5.7 Nonreciprocity and Activity	165
5.8 Problems	170
6. STABILITY	
6.1 The Characteristic Equation	173
6.2 Return Difference and Return Ratio	175
6.3 The Nyquist Criterion	182
6.4 Potential Stability of Two-Ports	189
6.5 Stabilization of a Terminated Two-Port	197
6.6 Stability, Activity and Nonreciprocity	204
6.7 Problems	206
7. POWER GAIN I	
7.1 Conjugate Matching	207
7.2 Power Gain	212
7.3 The Upper Bound on G_c	214
7.4 The Use of General Parameters	218
7.5 Power Gain of an Embedded Device	219
7.6 Movement in the Gain Plane	230
7.7 Stability of Conjugate-matched Amplifiers	241
7.8 Lossy Embedding	244
7.9 Problems	250

8. POWER GAIN II

8.1 Gain and Stability Measures	253
8.2 Maximization of Transducer Gain	254
8.3 Mismatched Amplifier with Large Stability Factor	258
8.4 Two-Port Power Flow	263
8.5 Power Gain	267
8.6 The Load Termination	269
8.7 Potential Instability and Power Flow	274
8.8 Problems	277

9. OSCILLATORS

9.1 Nonlinearity	279
9.2 Justification for a Linear Analysis	280
9.3 Maximally-loaded Oscillators	287
9.4 Embedding for Oscillation	290
9.5 Large-Signal Transistor Description	302
9.6 Non-Maximum Loading: The General Oscillator	306
9.7 Problems	313

10 NETWORK SENSITIVITY

A. Immittance Sensitivity

10.1 The Work of Bode	315
10.2 Similar Dependence	320
10.3 Large Variations in Parameters	323
10.4 Tellegen's Theorem	326

B. Amplifier Power Gain Sensitivity

10.5 The Conjugate-Matched Amplifier	332
10.6 The Mismatch-stabilized Amplifier	339

C. Oscillator Sensitivity

10.7 Frequency Sensitivity	340
10.8 Problems	351

INDEX	353
------------------------	------------