



# *Contents*

PREFACE	xii
1. INTRODUCTION, FUNDAMENTAL CONCEPTS, AND DEFINITIONS	1
1.1 Linearity and Nonlinearity	1
1.2 Frequency Generation	4
1.3 Nonlinear Phenomena	13
1.4 Approaches to Analysis	16
1.5 Power and Gain Definitions	19
1.6 Stability	24
References	25
2. SOLID-STATE DEVICE MODELING FOR QUASISTATIC ANALYSIS	27
2.1 Nonlinear Device Models	28
2.2 Nonlinear Lumped Circuit Elements and Controlled Sources	29
2.2.1 The Substitution Theorem	31
2.2.2 Nonlinear Conductance or Resistance	33
2.2.3 Nonlinear Capacitor	36
2.2.4 Relationship between $I/V$ , $Q/V$ and $G/V$ , $C/V$ Expansions	40
2.3 Schottky-Barrier and Junction Diodes	41
2.3.1 The Schottky-Barrier Diode Model	42
2.3.2 Mixer Diodes	49
2.3.3 Schottky-Barrier Varactors	53
2.3.4 $p^+n$ Junction Varactors	55
2.3.5 Step-Recovery Diodes	57
2.4 GaAs MESFETs	59
2.4.1 MESFET Operation	59
2.4.2 MESFET Modeling	63

2.5	Determining the Model Parameters	73
2.5.1	Direct Measurement of $C/V$ and $I/V$	74
2.5.2	Indirect Measurement of Diode Parameters	76
	References	79
3.	HARMONIC-BALANCE AND LARGE-SIGNAL-SMALL-SIGNAL ANALYSIS	81
3.1	Harmonic Balance	81
3.1.1	Large-Signal, Single-Tone Problems	81
3.1.2	Solution Algorithms	94
3.1.3	Selecting the Number of Harmonics and Time Samples	110
3.1.4	Comparison of Algorithms	113
3.2	Large-Signal-Small-Signal Analysis Using Conversion Matrices	115
3.2.1	Formulating the Conversion Matrices	116
3.2.2	Applying Conversion Matrices to Time-Varying Circuits	127
3.2.3	Multitone Excitation and Intermodulation in Time-Varying Circuits	137
3.3	Generalized Harmonic-Balance Analysis	146
3.3.1	Generalizing the Harmonic-Balance Concept	146
3.3.2	Reformulation and Fourier Transformation	148
3.3.3	Almost-Periodic Fourier Transforms	149
	References	152
4.	VOLTERRA-SERIES AND POWER-SERIES ANALYSIS	155
4.1	Power-Series Analysis	156
4.1.1	Power-Series Model and Multitone Response	156
4.1.2	Frequency Generation	163
4.1.3	Intercept Point and Power Relations	164
4.1.4	Interconnections of Weakly Nonlinear Components	170
4.2	Volterra-Series Analysis	172
4.2.1	Introduction to the Volterra Series	172
4.2.2	Volterra Functionals and Nonlinear Transfer Functions	174
4.2.3	Determining Nonlinear Transfer Functions by the Harmonic-Input Method	178
4.2.4	Applying Nonlinear Transfer Functions	186
4.2.5	Circuit Analysis via the Method of Nonlinear Currents	190
4.2.6	Application to Circuits Having Multiple Nodes	199
4.2.7	Controlled Sources	207
	References	207

<b>5. BALANCED AND MULTIPLE-DEVICE CIRCUITS</b>	209
<b>5.1 Balanced Circuits Using Microwave Hybrids</b>	209
<b>5.1.1 Properties of Ideal Hybrids</b>	209
<b>5.1.2 Practical Hybrids</b>	212
<b>5.1.3 Properties of Hybrid-Coupled Components</b>	220
<b>5.2 Direct Interconnection of Microwave Components</b>	231
<b>5.2.1 Harmonic Properties of Two-Terminal Device Interconnections</b>	232
<b>5.2.2 Properties of Direct Parallel Interconnection of Two-Port Components</b>	243
<b>References</b>	246
<b>6. DIODE MIXERS</b>	247
<b>6.1 Mixer Diodes</b>	247
<b>6.1.1 Diode Model</b>	248
<b>6.1.2 Mixer Diode Types</b>	251
<b>6.2 Nonlinear Analysis of Mixers</b>	254
<b>6.2.1 Large-Signal Analysis</b>	255
<b>6.2.2 Small-Signal Analysis</b>	258
<b>6.3 Single-Diode Mixer Design</b>	262
<b>6.3.1 Design Approach</b>	262
<b>6.3.2 Diode Selection</b>	266
<b>6.3.3 Mixer Design Example</b>	268
<b>6.4 Balanced Mixers</b>	272
<b>6.4.1 Singly Balanced Mixers</b>	272
<b>6.4.2 Doubly Balanced Mixers</b>	276
<b>References</b>	280
<b>7. DIODE FREQUENCY MULTIPLIERS</b>	283
<b>7.1 Varactor Frequency Multipliers</b>	284
<b>7.1.1 Noise Considerations</b>	284
<b>7.1.2 Power Relations and Efficiency Limitations</b>	285
<b>7.1.3 Design of Varactor Frequency Multipliers</b>	290
<b>7.1.4 Bias and Stability</b>	296
<b>7.2 Frequency Multipliers Using Step-Recovery Diodes</b>	297
<b>7.2.1 Multiplier Operation</b>	297
<b>7.2.2 Multiplier Design</b>	304
<b>7.3 Resistive Diode Frequency Multipliers</b>	307
<b>7.3.1 Approximate Analysis and Design of Resistive Doublers</b>	307
<b>7.4 Balanced Multipliers</b>	316
<b>References</b>	319

8. MESFET SMALL-SIGNAL AMPLIFIERS	321
8.1 Review of Linear Amplifier Theory	321
8.1.1 Stability Considerations in Linear Amplifier Design	321
8.1.2 Amplifier Design	326
8.2 Nonlinear Analysis of Small-Signal FET Amplifiers	331
8.2.1 Nonlinearities in the MESFET Equivalent Circuit	331
8.2.2 Nonlinear Phenomena in FET Amplifiers	332
8.2.3 Calculating the Nonlinear Transfer Functions	337
8.3 Optimizing the Linearity of MESFET Amplifiers	344
8.3.1 Modeling the MESFET	345
8.3.2 Bias Effects	346
8.3.3 Effects of Source and Load Impedances	349
8.3.4 Effect of Constraints on the Gain, Match, and Noise Figure	351
8.3.5 Effect of Source and Load Terminations at Low-Order Mixing Frequencies	354
8.3.6 Effects of Individual Nonlinear Elements	356
8.3.7 Conclusions	357
References	358
9. MESFET POWER AMPLIFIERS	359
9.1 Power MESFETs	359
9.1.1 Structure of Power MESFETs	359
9.1.2 Modeling Power MESFETs	362
9.2 Fundamental Considerations in Power-Amplifier Design	363
9.3 Design of MESFET Power Amplifiers	370
9.3.1 Approximate Design of Class-A FET Amplifiers	371
9.3.2 Approximate Design of Class-B FET Amplifiers	375
9.3.3 Design Examples and Performance Study	376
9.3.4 Effect of Nonzero Harmonic Terminations	383
9.4 Harmonic-Balance Analysis of FET Power Amplifiers	388
9.5 Practical Considerations	394
References	396
10. FET FREQUENCY MULTIPLIERS	397
10.1 Design Philosophy	397
10.2 Approximate Design of FET Frequency Multipliers	399
10.3 Harmonic-Balance Analysis of FET Frequency Multipliers	409
10.4 Other Aspects of FET Frequency-Multiplier Design	411
10.4.1 Effect of Gate and Drain Terminations at Unwanted Harmonics	411
10.4.2 Balanced Frequency Multipliers	413
10.5 Some Practical Concerns	415
References	416

11. FET MIXERS	417
11.1 Approximate Design of Single-Gate FET Mixers	417
11.1.1 Design Philosophy	417
11.1.2 Design Procedure	420
11.1.3 Matching Circuits in FET Mixers	425
11.2 Large-Signal-Small-Signal Analysis of FET Mixers	425
11.2.1 Large-Signal Analysis	426
11.2.2 Small-Signal Analysis	428
11.3 Design Examples	432
11.4 Dual-Gate FET Mixers	438
11.5 Balanced FET Mixers	442
11.5.1 Singly Balanced Mixers	442
11.5.2 Doubly Balanced FET Mixers	444
References	447
12. OSCILLATORS	449
12.1 Classic Oscillator Theory	449
12.1.1 Negative-Resistance Oscillators and Oscillation Conditions	449
12.1.2 Negative Resistance in Transistors	452
12.1.3 Oscillator Design via the Classic Approach	456
12.2 Nonlinear Analysis of Transistor Oscillators	461
12.3 Practical Aspects of Oscillator Design	463
12.3.1 Circuit Topology	463
12.3.2 Performance Parameters	467
References	469
Appendix 1: Relationships between Fourier Series and Phasors	471
Index	475