

CONTENTS

1. GENERAL ASPECTS OF DC TRANSMISSION AND COMPARISON OF IT WITH AC TRANSMISSION	1
1-1 Historical Sketch	1
1-2 Constitution of EHV AC and DC Links	9
1-3 Kinds of DC Links	11
1-4 HV DC Projects from 1954 to 1970	12
1-5 Limitations and Advantages of AC and DC Transmission	19
1-6 Summary of Advantages and Disadvantages of HV DC Transmission	32
1-7 Principal Applications of DC Transmission	32
1-8 Economic Factors	33
1-9 The Future of DC Transmission	35
Bibliography	36
2. CONVERTER CIRCUITS	49
2-1 Valve Characteristic	49
2-2 Properties of Converter Circuits	50
2-3 Assumptions	51
2-4 Single-Phase Converters	51
2-5 Three-Phase Converters	56
2-6 Pulse Number	61
2-7 Additional Six-Pulse Converter Circuits	62
2-8 Choice of Best Circuit for HV DC Converters	65
2-9 Twelve-Pulse Cascade of Two Bridges	67
Problems	68
Bibliography	70

3. ANALYSIS OF THE BRIDGE CONVERTER	71
3-1 Analysis with Grid Control but no Overlap	73
3-2 Analysis with Grid Control and with Overlap less than 60°	80
3-3 Analysis with Overlap Greater than 60°	92
3-4 Complete Characteristics of Rectifier	103
3-5 Inversion	105
3-6 Series and Parallel Arrangements of Valves, Anodes, or Bridges	112
3-7 Multibrige Converters	115
Problems	123
Bibliography	126
4. CONVERTER CHARTS	129
4-1 Chart 1 with Rectangular Co-ordinates of Direct Current and Voltage	129
4-2 Chart 2 with Rectangular Co-ordinates of Active and Re- active Power	138
4-3 Relations between the Two Charts	146
Problems	146
Bibliography	147
5. CONTROL	148
5-1 Grid Control	148
5-2 Basic Means of Control	152
5-3 Power Reversal	153
5-4 Limitations of Manual Control	154
5-5 Constant Current versus Constant Voltage	156
5-6 Desired Features of Control	157
5-7 Actual Control Characteristics	158
5-8 Constant-Minimum-Ignition-Angle Control	164
5-9 Constant-Current Control	165
5-10 Constant-Extinction-Angle Control	167
5-11 Stability of Control	174
5-12 Tap-Changer Control	179
5-13 Power Control and Current Limits	180
5-14 Frequency Control	182
5-15 Multiterminal Lines	183

5-16 Measuring Devices	187
Problems	192
Bibliography	194
6. MISOPERATION OF CONVERTERS	198
6-1 Malfunctions of Mercury-Arc Valves	198
6-2 Bypass Valves	199
6-3 Arcback	206
6-4 Short Circuit on a Rectifier	220
6-5 Commutation Failure	222
6-6 Arcthrough	227
6-7 Misfire	228
6-8 Quenching	229
6-9 Generalization of Inverter Faults and Certain Rectifier Faults	230
6-10 Consequential Faults in Rectifier	231
Problems	233
Bibliography	234
7. PROTECTION	235
7-1 General	235
7-2 DC Reactors	235
7-3 Voltage Oscillations and Valve Dampers	247
7-4 Current Oscillations and Anode Dampers	260
7-5 DC Line Oscillations and Line Dampers	270
7-6 Clearing Line Faults and Reenergizing the Line	272
7-7 Circuit Breakers	280
7-8 Overvoltage Protection	282
Problems	291
Bibliography	292
8. HARMONICS AND FILTERS	295
8-1 Summary	295
8-2 Characteristic Harmonics	296
8-3 Uncharacteristic Harmonics	318
8-4 Troubles Caused by Harmonics	323
8-5 Definitions of Wave Distortion or Ripple	325

8-6	Means of Reducing Harmonics	332
8-7	Telephone Interference	333
8-8	Harmonic Filters	343
	Problems	386
	Bibliography	386

9. GROUND RETURN 391

9-1	Advantages and Problems	391
9-2	The Current Field in the Earth Near an Electrode	393
9-3	The Current Field between the Electrodes	417
9-4	The Natural Current Field in the Earth	419
9-5	Compatibility with Other Services	423
9-6	Design of Electrodes—General	443
9-7	Design of Land Electrodes	445
9-8	Design of Sea and Shore Electrodes	465
	Problems	476
	Bibliography	478

APPENDICES 484

A.	Effective Value of Alternating Current of a Six-pulse Converter	484
B.	Fundamental Current, Power, and Reactive Power of a Six-pulse Converter	490
C.	Inclusion of Direct Voltage Drops Due to Resistance and Arcs in Converter Equations	494

INDEX 496