

Table of Contents

INTRODUCTION: The Electrostatic Shield	1
1 Electrostatics	5
1.1 Charge	5
1.2 Forces Between Charges	5
1.3 Electric Field	6
1.4 Voltage	7
1.5 Voltage Gradient	7
1.6 A Spherical Conductor with a Charge	8
1.7 The Electric Field at a Conductor	9
1.8 The Displacement Field D	10
1.9 Field Representations	10
1.10 Points of Difficulty	12
1.11 MKS System of Units	13
1.12 Charges on Spherical Shells	14
1.13 Typical Charge Distributions	17
1.14 Cylindrical Surfaces	18
1.15 Parallel Plate Capacitors	19
2 Capacitance and Energy Storage	21
2.1 General Comments	21
2.2 Green's Reciprocation Theorem	21
2.3 Self- and Mutual Elastance	23
2.4 Self- and Mutual Capacitance	24
2.5 Electric Screening (Shielding)	24
2.6 Energy in a Single Capacitor	26
2.7 Energy Stored on a Multiple-Conductor System	26
2.8 Energy in Terms of the Field	27

3	Applying Electrostatics to Practical Processes	29
3.1	General	29
3.2	Current in Capacitors	29
3.3	Voltage Sources	31
3.4	Electrostatic Shielding	32
3.5	The Earth Plane	33
3.6	Typical Capacitances	34
3.7	Room Pickup	34
4	Practical Shielding of Instruments	37
4.1	The Amplifier Shield	37
4.2	Signal Entrances to a Shield Enclosure	39
4.3	Shield Currents	40
4.4	Shield-Drain Direction	41
4.5	Shield Connections—Segments	41
4.6	Power Entrances	42
4.7	Power-Transformer Conventions	42
4.8	Power Transformer with a Single Shield	43
4.9	Coil-to-Shield Capacitance	43
4.10	The Single Transformer Shield and its Connections	45
4.11	The Double Electrostatic Shield	46
4.12	Single-Ended Amplifiers	48
4.13	Segmenting the Amplifier Shield	48
4.14	A Shield-Enclosure Rule	49
4.15	Primary-Shield Ties	50
4.16	A Note on Locating Current Loops	50
5	The Differential Amplifier	53
5.1	General	53
5.2	A Basic Instrumentation Problem	54
5.3	Instrumentation Differential Amplifiers	55
5.4	Common-Mode Voltage	56
5.5	Common-Mode Content	57
5.6	Common-Mode Rejection Ratio or CMR	57
5.7	Solutions to the Differential-Amplifier Problem	58
5.8	The Flux-Coupled Differential DC Amplifier	60
5.9	Input Modulator Techniques with Flux Coupling	61
5.10	Postmodulator Techniques in Flux-Coupled Instruments	62
5.11	Merits of Flux-Coupled Instruments	63
5.12	The Electronically Coupled Differential DC Amplifier	64

5.13	Postamplification in Electronically Coupled Instruments	64
5.14	Preamplification in Electronically Coupled Instruments	65
5.15	Return-Path Requirements in Electronically Coupled Instruments	67
5.16	Merits of Electronically Coupled Instruments	67
6	General Application Problems	69
	A Few Explanations	69
6.1	When Single-Ended Amplifiers Should Be Used	69
6.2	Charge Amplifiers	70
6.3	Input Coax Applied to a Single-Ended Amplifier	70
6.4	Coax-to-Twinax Interface	71
6.5	Resistance-Bridge Applications (Strain Gages)	71
6.6	Isolated Resistance Bridge and a Grounded Observation Point	72
6.7	Single-Ended Amplifiers and Thermocouples	73
6.8	When Differential Amplifiers Should be Used	74
6.9	Floating Sources and Differential Amplifiers	75
6.10	A <i>Misapplied</i> Shield for Thermocouples	76
6.11	The Double Input Shield for Thermocouples	77
6.12	Grounding vs Floating Signal Lines	78
6.13	Shield-Current Control (The Medical Problem)	79
6.14	The Use of Isolation Transformers	81
6.15	Isolation Transformers for Rack Isolation	83
6.16	Single-Ended to Differential Conversion by Using Buffers	84
6.17	A Calibration Problem	85
7	Shielding in Resistance-bridge Systems	89
7.1	General	89
7.2	The Resistance Bridge and its Signal Environment	89
7.3	The Floating Power Supply	90
7.4	Floating Power-Supply Shielding	91
7.5	Multiconductor Cable	92
7.6	Differential Amplifiers and Resistance Bridges	93
7.7	Common Power-Supply Excitation	94
7.8	Shielding Calibrate Processes	95
7.9	Amplifier Power-Supply Combinations	97
8	Magnetic Processes in Instrumentation	99
8.1	Introduction	99
8.2	Basic Ideas	99

8.3	Lenz's Law	102
8.4	Ampere's Law	103
8.5	Coaxial Current Flow	104
8.6	Magnetic Loop Areas	104
8.7	Magnetic Units	105
8.8	Mutual and Self-Inductance	106
8.9	Signal Circuit Coupling by Magnetic Field	106
8.10	An Electrostatic-Shield Problem	107
8.11	Parallel Cable Runs	108
8.12	Flux Coupling to Shield Connections	108
8.13	Use of Conduit for Field Reduction	109
8.14	Practical Transformer Shields	109
8.15	Ultrashielded Isolation Transformers	110
8.16	Shielding a Toroidal Core	114
8.17	Balanced Transformer Construction	115
8.18	A Special Shielding Technique	115
8.19	Measuring Transformer Mutual Capacitances	116
8.20	Active Measurements of Mutual Capacitance	117
9	Rf Processes in Instrumentation	119
	General	119
9.1	Radiation Energy	119
9.2	Controlled Rf Paths	120
9.3	The Transmission Line	121
9.4	Transmission Lines in Instrumentation	122
9.5	Rf Comments	122
9.6	Waveguides	122
9.7	Rf Shielding	123
9.8	Skin Effect	124
9.9	Ground Conductors	124
9.10	Shielded Enclosures	125
9.11	Rf-Pickup Elimination	126
9.12	Rf Common-Mode Signals	126
9.13	The Isolation Transformer	127
9.14	Long Signal Lines	128
9.15	Driven Lines for Capacitance Reduction	129
9.16	Transmission-Line Equations	131
9.17	Signal Cables	131
9.18	Cable Frequency vs Amplitude Response	132
9.19	Cable-Shield Effectiveness	132
9.20	Low-Noise Cable	133

10 The Earth Plane**135**

10.1	General	135
10.2	Units of Resistivity	135
10.3	Typical Soil Resistivities	136
10.4	Resistance and Capacitance Analogy	136
10.5	The Driven Rod	136
10.6	Utility Practice vs Lightning	137
10.7	Utility Practices	137
10.8	A Problem in Earthing Many Conductors	138
10.9	Ground Bus	138
10.10	Flow of Neutral Current	139
10.11	Floating the Instrument Racks	140