
CONTENTS

| | |
|--|-------------|
| Preface to the First Edition | xi |
| Preface to the Second Edition | xiii |
| Symbols | xv |
| Subscripts | xvii |
| | |
| Chapter 1 Power Semiconductor Devices | 1 |
| The p–n Junction | 2 |
| The Transistor | 5 |
| The power MOSFET | 7 |
| The insulated-gate bipolar transistor (IGBT) | 9 |
| The cascade switch | 11 |
| The Thyristor | 13 |
| Mechanical construction | 15 |
| The Switching Behaviour of Diodes and Thyristors | 16 |
| The turn-on process in thyristors | 18 |
| Turn-off processes | 20 |
| Reverse recovery | 21 |
| Forced Commutation | 22 |
| Forced commutation with substantial reverse voltage | 23 |
| Determination of commutating capacitance | 24 |
| Commutation with inverse-parallel diode | 26 |
| Characteristics and Ratings of Diodes and Thyristors | 29 |
| Effects of temperature | 30 |
| Voltage ratings | 31 |
| Forward current rating | 33 |
| Gate firing characteristics and gate ratings | 35 |
| Holding and latching currents | 37 |
| di/dt | 38 |
| dv/dt | 39 |
| Special Thyristor Structures | 41 |
| Shorted emitter | 41 |
| Amplifying gate | 42 |
| Asymmetrical thyristor | 43 |
| The gate turn-off thyristor (GTO) | 43 |
| Bi-directional thyristors | 45 |

| | |
|---|-----------|
| Chapter 2 Naturally Commutating Converters | 47 |
| Definitions | 47 |
| The Single-phase Half-wave Rectifier | 48 |
| Multi-phase Single-way Rectifiers | 51 |
| Commutation in multi-phase rectifiers | 53 |
| D.C. output voltage and a.c. input current | 53 |
| Practical forms of single-way rectifier | 54 |
| The utilization of compounds in simple single-way rectifiers | 59 |
| Input current harmonics | 62 |
| The relationship of transformer utilization and current waveforms | 63 |
| Input power factor | 64 |
| Multiplex Single-way Rectifiers | 65 |
| The hexaphase rectifier with interphase reactor | 68 |
| Magnetizing current in the interphase reactor | 70 |
| Phase Multiplication and Input Harmonics | 71 |
| 12-pulse and 24-pulse Rectifiers | 73 |
| Bridge Rectifiers | 74 |
| Three-phase Bridge Rectifier | 75 |
| Single-phase Bridge Rectifier | 78 |
| Multiplex Bridge Rectifiers | 79 |
| General Comparison of Rectifier Circuits | 81 |
| Controlled Converters | 81 |
| Input harmonics, power factor and transformer utilization | 84 |
| Multiplex and Bridge Converters | 85 |
| The Half-controlled Bridge | 86 |
| Input current | 88 |
| Input power factor of half-controlled bridges | 89 |
| Controlled Rectifiers with Free-wheel Diodes | 92 |
| Single-way rectifier | 93 |
| Bridge rectifier with free-wheel diode | 95 |
| Input characteristics of controlled rectifiers with free-wheel diodes | 96 |
| Two-bridge Half-controlled Rectifier | 97 |
| Generalized Output Waveforms and Ripple Voltage | 98 |
| Output ripple from half-controlled bridge rectifiers | 102 |
| Controlled rectifiers with free-wheel diodes | 105 |
| Interphase Reactor Rating in Controlled Converters | 106 |
| Operation of Converters with Finite Source Inductance | 107 |
| Single-way converters | 107 |
| Voltage-time integrals and voltage drop | 108 |
| Overlap angle | 109 |
| Overlap in bridge converters | 111 |
| Half-controlled bridge rectifiers with finite source inductance | 113 |
| Relationships between per-unit reactance and voltage drop | 113 |
| Overlap during inversion: loss of commutation | 114 |
| Loss of commutation in half-controlled rectifiers | 117 |
| Reduction of input harmonics due to overlap | 118 |
| Effect of overlap on output ripple | 121 |
| Smoothing | 122 |
| Critical inductance | 123 |
| Uncontrolled rectifier | 125 |
| Controlled converter with smooth output voltage | 127 |
| Controlled converter with LR load | 129 |
| Discontinuous-current Characteristics | 130 |
| Controlled converters | 131 |
| Uncontrolled rectifiers | 134 |
| Overload and Short-circuit Characteristics of Rectifiers | 134 |

| | |
|--|-----|
| Single-phase rectifiers | 135 |
| Three-phase single-way rectifier | 136 |
| Three-phase bridge rectifier | 137 |
| Multiplex rectifiers | 137 |
| Total Voltage Drop | 138 |
| Weighted ripple | 139 |
| Applications of Converters: Double Converters | 140 |
| Appendix 2(i) Two-pulse Rectifier with Capacitive Load | 142 |
| Appendix 2(ii) The Overall Power Factor of Rectifier Equipment | 143 |
| Appendix 2(iii) Analysis of Input Current Waveform of a Three-phase Bridge Rectifier | 145 |
| Problems | 149 |

Chapter 3 A.C. Regulators 151

| | |
|---|-----|
| Single-phase Regulator | 151 |
| Three-phase A.C. Regulators | 153 |
| Three-phase three-wire a.c. regulators | 154 |
| Thyristor-diode regulators | 157 |
| Open-star regulators | 158 |
| Thyristor voltage ratings | 160 |
| Regulators with Inductive Load | 161 |
| A.C. Regulators Conjoined with Rectifiers | 163 |
| Input Power Factor and Harmonics | 164 |
| Integral-half-cycle Control | 166 |
| Thyristor Tap-changers | 169 |
| Problems | 171 |

Chapter 4 D.C. Switching Regulators 173

| | |
|---|-----|
| Harmonic content of output and input | 177 |
| Practical step-down regulator | 179 |
| Discontinuous output current | 180 |
| Regulator without voltage smoothing | 182 |
| Modes of control | 184 |
| Step-up Regulators | 184 |
| The Step-up/Step-down or Buck-boost Converter | 189 |
| Continuous-mode operation | 189 |
| Discontinuous-mode operation | 190 |
| Circuit applications | 191 |
| The Ćuk converter | 192 |
| Bi-directional and Four-quadrant Regulators | 193 |
| Multi-phase Switching Regulators | 195 |
| Commutation Circuits | 198 |
| Commutation with inverse parallel diode | 206 |
| Switching regulators without auxiliary thyristors | 208 |
| Two- and four-quadrant regulators | 210 |
| Converters Having Isolation between Input and Output | 210 |
| The forward converter | 210 |
| Flyback or energy storage converter | 214 |
| Other isolated converters | 220 |
| Off-line Switched-mode Power Supplies | 221 |
| Appendix 4(i) Fourier Analysis of Switching Regulator Waveforms | 223 |
| Problems | 224 |

| | |
|--|----------------|
| Chapter 5 Static Power Inverters | 229 |
| Voltage-fed Inverters | 230 |
| Basic operation | 230 |
| Reactive feedback diodes | 231 |
| Bridge inverter with inductive load | 232 |
| Bridge inverter with leading load | 236 |
| Three-phase bridge inverter | 237 |
| Methods of forced commutation | 241 |
| The McMurray inverter | 241 |
| The bi-phase inverter | 243 |
| Output voltage control | 244 |
| Voltage control in three-phase inverters | 247 |
| Output voltage harmonics | 249 |
| Reduction of output harmonics | 251 |
| Phase multiplication | 254 |
| Multiple pulse-width control | 255 |
| Selected harmonic reduction | 259 |
| Pulse-width modulation | 261 |
| Current-fed Inverters | 264 |
| Operation with significant turn-off time | 266 |
| Operation in practice | 267 |
| Untuned parallel inverters | 268 |
| Variation of output voltage with load | 270 |
| Reactive feedback in current-fed inverters | 271 |
| Control of circulating current | 272 |
| Further current-fed inverter configurations | 275 |
| Comparison of Inverter Techniques | 278 |
| Appendix 5(i) Characteristics of Resonant Loads | 279 |
| Appendix 5(ii) McMurray Commutation Circuit | 281 |
| Appendix 5(iii) Fourier Analysis of Rectilinear Waveforms | 286 |
| Appendix 5(iv) Output Voltage of Simple Current-fed Inverter with <i>CR</i> Load | 287 |
| Appendix 5(v) Commutation in Current-fed Inverters with Reactive Feedback | 288 |
| Appendix 5(vi) Harmonics Generated by Sinusoidal P.W.M. in a Bridge Inverter | 291 |
| Problems | 293 |
| Chapter 6 Application Techniques | 295 |
| Cooling of Semiconductor Devices | 295 |
| Mounting of semiconductor devices | 296 |
| Air coolers | 297 |
| Natural air cooling | 297 |
| Forced air cooling | 298 |
| Thermal time response | 298 |
| Multiple cooler assemblies | 299 |
| Liquid cooling | 300 |
| The Estimation of Instantaneous Temperature in Semiconductor Devices | 300 |
| Single rectangular pulse | 302 |
| Repeated rectangular pulse | 303 |
| Extended train of similar rectangular pulses | 304 |
| Single pulse of other than rectangular waveform | 306 |
| Extended train of pulses of other than rectangular waveform | 307 |
| Overcurrent Protection in Thyristor and Diode Circuits | 308 |

| | |
|---|----------------|
| Overcurrent protection by fuses | 310 |
| Matching of thyristors and fuses in a.c. circuits | 313 |
| Fuses in d.c. circuits | 316 |
| Fuses in series and parallel | 316 |
| Automatic current limiting | 316 |
| dv/dt Suppression | 317 |
| Overvoltage Protection | 320 |
| Transformer switching surges | 320 |
| Protection of switching converters and regulators against internally generated transients | 324 |
| The CRD dissipative snubber | 326 |
| The energy-recovery snubber | 328 |
| Turn-on snubbers | 330 |
| Passive flux resetting circuit for transformer-coupled converters | 330 |
| Supply-borne transients | 334 |
| Rectifier-fed suppression capacitors | 334 |
| Surge voltages due to carrier storage | 335 |
| Non-linear surge suppressors | 335 |
| Crowbar circuits | 337 |
| Series Operation of Diodes and Thyristors | 337 |
| Steady-state voltage sharing | 338 |
| Transient voltage sharing | 339 |
| Reverse recovery | 339 |
| Variations in turn-on time | 340 |
| Overall design of sharing networks | 342 |
| Selection of cells for series operation | 342 |
| Parallel Operation of Diodes and Thyristors | 343 |
| Current sharing in diodes and thyristors | 343 |
| Current sharing with individual inductors | 344 |
| Firing parallel-connected thyristors | 348 |
| The Firing of Thyristors | 349 |
| Gate current amplitude and rise time | 349 |
| Gate pulse duration | 350 |
| Pulse waveforms | 351 |
| Spurious triggering | 352 |
| Firing-angle determination in naturally commutating converters | 352 |
| Variable phase shift | 352 |
| Magnetic amplifiers | 353 |
| Waveform-intersection systems | 353 |
| Digital systems | 354 |
| Additional design features | 354 |
| Appendix 6(i) Basic Heat-transfer Relationships | 354 |
| Appendix 6(ii) Response of Damped <i>LCR</i> Circuits | 356 |
| Problems | 360 |
| Bibliography | 363 |
| Answers to Problems | 365 |
| Index | 367 |