

CONTENTS

| | |
|---|-----------|
| List of Symbols | xix |
| 1 INTRODUCTION | 1 |
| 1.1 What Is a Transformer? | 1 |
| 1.2 Electronic Transformers | 2 |
| 1.3 New Technology | 2 |
| 1.4 Transformer Fundamentals | 7 |
| 1.5 Sinusoidal Voltage | 8 |
| 1.6 Equivalent Circuit and Vector Diagram | 8 |
| 1.7 Magnetizing Current | 11 |
| 1.8 Flux and Average Voltage | 13 |
| 1.9 Ideal Transformer | 14 |
| 1.10 Polarity | 15 |
| 1.11 Regulation, Efficiency, and Power Factor | 16 |
| 1.12 Wave Shapes | 16 |
| 2 TRANSFORMER CONSTRUCTION, MATERIALS, AND RATINGS | 20 |
| 2.1 Configuration | 20 |
| 2.2 Transformer Cores | 20 |
| 2.3 Core Materials | 24 |
| 2.4 Properties of Important Ferromagnetic Elements | 30 |
| 2.4.1 Iron-Silicon Alloys | 30 |
| | xi |

| | | |
|---------|-------------------------------------|----|
| 2.4.2 | Iron-Nickel Alloys | 31 |
| 2.4.3 | Iron-Cobalt Alloys | 31 |
| 2.4.4 | Ferrites | 31 |
| 2.4.5 | Powdered Cores | 31 |
| 2.4.5.1 | Molybdenum Permalloy Powder Cores | 31 |
| 2.4.5.2 | Iron Powder Cores | 32 |
| 2.4.6 | Amorphous Alloys | 32 |
| 2.5 | Windings | 32 |
| 2.5.1 | Winding Machines | 42 |
| 2.6 | Insulation | 42 |
| 2.6.1 | Dielectric Properties of Insulation | 45 |
| 2.7 | Impregnation | 45 |
| 2.8 | Size Versus Rating | 46 |
| 2.9 | Intermittent Ratings | 53 |

| | | |
|----------|---|-----------|
| 3 | RECTIFIER TRANSFORMERS AND INDUCTORS | 56 |
| 3.1 | Rectifiers with Inductor Input Filters | 57 |
| 3.2 | Rectifiers with Capacitor Input Filters | 59 |
| 3.3 | Voltage Doublers | 61 |
| 3.4 | Three-Phase Capacitor Input Filters | 61 |
| 3.5 | Transformers with Unrectified Outputs | 64 |
| 3.6 | Low-Voltage Power Transformer Design | 65 |
| 3.7 | Anode Transformers | 70 |
| 3.8 | Leakage Inductance | 71 |
| 3.9 | Anode Transformer Design | 72 |
| 3.10 | Power Supply Frequency | 74 |
| 3.11 | 400-Hertz Transformer Design | 76 |
| 3.12 | Polyphase Transformers | 78 |
| 3.13 | Design Chart | 79 |
| 3.14 | Inductors | 83 |
| 3.15 | Inductors with Large AC Flux | 88 |
| 3.16 | Linear Inductor Design | 91 |
| 3.17 | Linear Inductor Chart | 93 |
| 3.18 | Air-Gap Flux Fringing | 95 |
| 3.19 | Similitude in Design | 96 |
| 3.20 | Inductor Current Interruption | 96 |
| 3.21 | Transformers with DC Flux | 98 |
| 3.22 | Power Transformer Tests | 99 |

| | | |
|----------|---|------------|
| 4 | RECTIFIER PERFORMANCE | 104 |
| 4.1 | Ripple | 104 |
| 4.2 | Single-Phase Rectifiers | 105 |
| 4.3 | Polyphase Rectifiers | 106 |
| 4.4 | Multistage Filters | 108 |
| 4.5 | Capacitor Input Filters | 111 |
| 4.6 | Rectifier Regulation | 112 |
| 4.7 | Capacitor Effect | 115 |
| 4.8 | Tuned Rectifier Filters | 118 |
| 4.9 | Rectifier Currents | 118 |
| 4.10 | Rectifier Transients | 121 |
| 4.11 | Rectifier Filter Charts | 124 |
| 4.12 | Rectifier Efficiency | 129 |
| 4.13 | Rectifier Tests | 129 |
| 5 | AMPLIFIER TRANSFORMERS | 131 |
| 5.1 | Amplifiers | 132 |
| 5.2 | Transformer-Coupled Amplifiers | 134 |
| 5.3 | Amplifier Classification | 136 |
| 5.4 | Decibels; Impedance Matching | 141 |
| 5.5 | Wide-Band Transformers | 141 |
| 5.5.1 | Low-Frequency Response | 143 |
| 5.5.2 | High-Frequency Response | 145 |
| 5.5.3 | Harmonic Distortion | 149 |
| 5.6 | Push-Pull Amplifier Transformers | 154 |
| 5.7 | Effects of Transformer Impedance Changes on Device Currents | 157 |
| 5.8 | Pentodes, FETs, and Bipolar Transistors | 159 |
| 5.9 | Calculation of Inductance and Capacitance | 162 |
| 5.10 | Core Selection | 165 |
| 5.11 | Amplifier Transformer Design | 166 |
| 6 | AMPLIFIER CIRCUITS | 171 |
| 6.1 | Wide-Band Amplifiers | 172 |
| 6.2 | Inverse Feedback | 172 |
| 6.3 | Current Amplifiers | 178 |
| 6.4 | Wave Filters | 179 |
| 6.5 | Limitations of Wave Filters | 181 |
| 6.6 | Artificial Lines | 183 |
| 6.7 | Inductor Design for Wave Filters | 184 |

| | | |
|----------|---|------------|
| 6.8 | Other Core Materials | 188 |
| 6.9 | Class D Amplifiers | 189 |
| 6.10 | Driver Transformers | 193 |
| 6.11 | Transformer-Coupled Oscillators | 194 |
| 6.12 | Shielding | 196 |
| 6.12.1 | Magnetic Shielding | 196 |
| 6.12.2 | Electrostatic Shielding | 199 |
| 6.13 | Hybrid Transformers | 199 |
| 6.14 | Amplifier Tests | 203 |
| 7 | HIGHER-FREQUENCY TRANSFORMERS | 205 |
| 7.1 | Laminated Core Transformers | 205 |
| 7.2 | Other Core Materials | 208 |
| 7.3 | Capacitance Evaluation | 212 |
| 7.4 | Leakage Inductance at High Frequencies | 215 |
| 7.5 | Wide-Band Transformers | 216 |
| 7.6 | Air-Core Transformers | 218 |
| 7.7 | Multiple Tuned Circuits | 221 |
| 7.8 | Mutual Inductance | 222 |
| 7.9 | Tuning Slugs | 225 |
| 7.10 | RF Inductors | 226 |
| 7.11 | Large Power Coupling Inductors | 228 |
| 8 | SATURABLE MAGNETIC CIRCUITS | 231 |
| 8.1 | Saturable Inductors | 231 |
| 8.2 | Simple Magnetic Amplifiers | 232 |
| 8.3 | Graphical Performance of Simple Magnetic Amplifiers | 235 |
| 8.4 | Response Time | 238 |
| 8.5 | Feedback in Magnetic Amplifiers | 239 |
| 8.6 | Bistable Amplifiers | 241 |
| 8.7 | Current Transducers | 242 |
| 8.8 | Self-Saturated Magnetic Amplifiers | 243 |
| 8.9 | Hysteresis Loops and Transfer Curves | 245 |
| 8.10 | Self-Saturated Magnetic Amplifier Circuits | 248 |
| 8.11 | Half-Wave Control of Magnetic Amplifiers | 253 |
| 8.12 | Magnetic Amplifier Design | 255 |
| 8.13 | Magnetic Amplifier Limitations | 259 |
| 8.14 | Magnetic Pulse Generators | 260 |

| | | |
|-----------|--|------------|
| 9 | HIGH VOLTAGE | 263 |
| 9.1 | High-Voltage Magnetic Devices | 263 |
| 9.2 | High-Voltage Power Transformers | 263 |
| 9.3 | Filter Inductors | 265 |
| 9.4 | Isolation Transformers | 266 |
| 9.5 | Pulse Transformers | 267 |
| 9.6 | High-Voltage Insulation | 267 |
| | 9.6.1 Liquids | 267 |
| | 9.6.2 Solids | 270 |
| | 9.6.3 Gases | 271 |
| | 9.6.3.1 Stress Concentrations | 272 |
| 9.7 | Voltage Stress on Different Dielectrics in Series | 273 |
| | 9.7.1 Stress Distribution in AC Fields | 273 |
| | 9.7.2 Stress Distribution in DC fields | 273 |
| 9.8 | Dielectric Strength | 274 |
| 9.9 | Flashover and Creepage | 274 |
| | 9.9.1 Creepage in Oil Insulation | 278 |
| 9.10 | Partial Discharge | 280 |
| | 9.10.1 Partial Discharge in AC Systems | 280 |
| | 9.10.2 Partial Discharge in DC Systems | 280 |
| | 9.10.3 Partial Discharge in Combined AC and DC Systems | 281 |
| 9.11 | Partial Discharge Detection | 281 |
| 9.12 | High-Voltage Transformer Design | 282 |
| 10 | PULSE AND VIDEO TRANSFORMERS | 286 |
| 10.1 | Square Waves | 286 |
| 10.2 | Transformer-Coupled Pulse Amplifiers | 289 |
| 10.3 | Leading-Edge Response | 290 |
| 10.4 | Response at the Top of the Pulse | 292 |
| 10.5 | Trailing-Edge Response | 293 |
| 10.6 | Total Response | 296 |
| 10.7 | Step-Down Transformers | 298 |
| 10.8 | Frequency Response and Wave Shape | 300 |
| 10.9 | Core Material | 301 |
| 10.10 | Windings and Insulation | 304 |
| 10.11 | Efficiency | 308 |
| 10.12 | Nonlinear Loads | 309 |

| | | |
|-----------|--|------------|
| 10.13 | Design of Pulse Transformers | 312 |
| 10.13.1 | Requirements | 312 |
| 10.13.2 | Start of Design | 312 |
| 10.13.3 | Final Calculations | 313 |
| 10.14 | Testing | 317 |
| 11 | PULSE CIRCUITS | 321 |
| 11.1 | Blocking Oscillators | 322 |
| 11.2 | Line-Type Pulsers | 324 |
| 11.3 | False Echoes After Main Pulse | 326 |
| 11.4 | DC Charging Inductors | 331 |
| 11.5 | Sweep Generators | 332 |
| 11.6 | Magnetic Sweep Circuits | 336 |
| 12 | INVERTER TRANSFORMERS | 337 |
| 12.1 | Comparison of Inverter Transformers to Conventional Pulse Transformers | 337 |
| 12.2 | Developing Design Parameters | 338 |
| 12.3 | Voltage Rise | 339 |
| 12.4 | Top of Pulse | 343 |
| 12.5 | Voltage Decay | 344 |
| 12.6 | Superposed Oscillations | 344 |
| 12.7 | Selecting Proper Transformer Parameters | 346 |
| 12.8 | Controlling Undesirable Conditions | 348 |
| 12.9 | Core Selection | 350 |
| 12.10 | Windings | 352 |
| 12.11 | Higher-Frequency Inverters | 355 |
| 12.12 | Testing | 359 |
| 13 | INVERTER CIRCUITS | 360 |
| 13.1 | Types of Inverter Circuits | 360 |
| 13.2 | Transistor Operation | 365 |
| 13.3 | Thyristor Operation | 369 |
| 13.4 | DC-to-DC Inverters | 370 |
| 13.5 | DC-to-AC Inverters | 377 |
| 13.6 | Special Circuits | 378 |
| 14 | OTHER MAGNETIC DEVICES | 380 |
| 14.1 | Thyratron Transformers | 380 |
| 14.2 | Peaking Transformers | 384 |
| 14.3 | Current-Limiting Transformers | 385 |

| | | |
|------|---------------------------|-----|
| 14.4 | Autotransformers | 387 |
| 14.5 | Static Voltage Regulators | 388 |
| 14.6 | Current Transformers | 389 |
| 14.7 | Balun Transformers | 390 |

| | |
|-------------------|------------|
| REFERENCES | 393 |
|-------------------|------------|

| | |
|--------------|------------|
| INDEX | 397 |
|--------------|------------|