

Contents

Page		
xv		Introduction
1	1	Physics of Optical Radiation
3	1.1	Optical radiation and light
3	1.1.1	Basic definitions
3	1.1.2	The quantum nature of radiation
4	1.1.3	The dualism of waves and particles
4	1.1.4	Wavelength and propagation speed
5	1.2	Radiation and luminescence phenomena
5	1.2.1	Atomic and band model
8	1.2.2	Luminescence, Fluorescence, Phosphorescence
9	1.2.3	Luminescence phenomena in semiconductors, injection luminescence
13	1.3	Photoelectric effect
13	1.3.1	External photoeffect
14	1.3.2	Internal photoeffect
16	1.3.3	Junction photoeffect
19	2	Principles of calculation in radiation physics and optics
21	2.1	Radiant flux – Luminous flux, Radiant energy – Light quantity
22	2.2	Parameters related to the radiation source
22	2.2.1	Radiant emittance – Luminous emittance
23	2.2.2	Radiant intensity – Luminous intensity
24	2.2.3	Radiance – Luminance
26	2.2.4	Units of luminance
26	2.2.5	Radiant efficiency and luminous efficiency
27	2.3	Parameters related to the receiver
27	2.3.1	Irradiance – Illuminance
28	2.3.2	Irradiation – Light exposure
29	2.3.3	Relationship between irradiance or illuminance and the reflected radiance or luminance
29	2.3.4	Spectral radiation – physical units
33	3	Laws of radiation
35	3.1	Solid angle
36	3.2	Lambert's radiator
36	3.2.1	Fundamental law of photometry
37	3.2.2	Lambert's cosine law
38	3.3	Calculation of radiation with small surface radiators and surface receivers
40	3.3.1	Inverse square law

43	4	Laws of Radiation from a Black Body
45	4.1	Black and "Non-black" bodies
45	4.1.1	Black bodies
46	4.1.2	Non-black bodies
46	4.2	Laws of radiation
46	4.2.1	Planck's law of radiation
47	4.2.2	Stefan-Boltzmann law
48	4.2.3	Wien displacement law
50	4.2.4	Emittivity
51	4.2.5	Kirchhoff's law
51	4.2.6	Radiation isotherms
51	4.2.7	Reduced law of radiation
57	5	General and Photometric Evaluation of Radiation
59	5.1	The human eye
59	5.2	Optical sensitivities
60	5.3	Photometric evaluation of radiation
62	5.3.1	Determination of the conversion constants C and C'
64	5.3.2	Photometric radiation equivalent
67	5.3.3	Photometric radiation equivalent of the photopic sensitivity of the eye
69	5.4	Calculation of the photometric radiation equivalent K for different radiation sources
69	5.4.1	Calculation of the photometric radiation equivalent K of a Planck radiator with the temperature laid down for the definition of the candela
69	5.4.2	Calculation of the photometric radiation equivalent K for standard light A
70	5.4.3	Calculation of the photometric radiation equivalent K of the luminescence radiation from light-emitting diodes
74	5.5	Conversion of radiometric units into photometric, photopic units
74	5.5.1	Conversion of radiometric units into photometric units for Planck radiation
76	5.5.2	Conversion of radiometric units into photometric units for the luminescence radiation from light-emitting diodes
77	5.6	Actinic value
77	5.6.1	Actinic value of a radiation for photodetectors and for the human eye
80	5.6.2	Actinic value of Planck radiation and luminescence radiation for the eye as a photodetector
83	6	Interaction between optical radiation and matter
85	6.1	Absorption, transmission and reflection factors
85	6.2	Spectral transmission factor and spectral absorption factor
86	6.3	Scatter
86	6.4	Reflection of radiation
87	6.4.1	Spectral reflectivity
88	6.5	Basic laws of absorption, attenuation and scatter

90	6.6	Absorption and transmission spectra
96	6.7	Refraction
101	7	Radiation sources
103	7.1	Natural radiation sources
103	7.1.1	The Sun
104	7.1.2	The Moon
104	7.1.3	Clouds
104	7.2	Artificial radiation sources
104	7.2.1	Open fire
104	7.2.2	Filament lamps
105	7.3	Luminescence radiators
105	7.3.1	Hot gases
105	7.3.2	Discharges through gases
107	7.3.3	Discharge lamps
107	7.3.4	Discharge tubes
109	7.3.5	Xenon lamps
109	7.3.6	Metal-vapour lamps
109	7.3.6.1	Sodium-vapour lamps
109	7.3.6.2	Low-pressure mercury-vapour lamps
109	7.3.6.3	High-pressure mercury-vapour lamps
110	7.3.6.4	Fluorescent lamps
110	7.4	Mixed-light lamps
111	7.5	Flash-discharge tubes in photography
113	7.6	Luminescent diodes
113	7.6.1	Silicon-doped GaAs diodes
113	7.6.2	GaP diodes
114	7.6.3	Zinc-doped GaAsP diodes
114	7.6.4	Considerations on quantum efficiency
117	8	Photodetectors
119	8.1	Photodetectors with external photoeffect
120	8.2	Photodetectors with internal photoeffect
120	8.2.1	Photoconductors or photoresistors
121	8.3	Junction photodetectors
123	9	Parameters of IR Detectors and Junction Photodetectors
125	9.1	Quantum efficiency of junction photodetectors
126	9.1.1	Quantum efficiency and photocurrent gain of avalanche photodiodes
130	9.2	Spectral sensitivity of junction photodetectors
132	9.2.1	Scottky-Barrier PIN photodiodes
132	9.2.2	Planar diffused Si photodiodes
134	9.2.3	Photodiodes by the CDI process
134	9.2.4	Effect of temperature on the spectral sensitivity of photodiodes
134	9.2.5	Possibilities for shifting the spectral sensitivity of photodiodes
136	9.3	Evaluation of radiation by non-amplifying junction photodetectors for monochromatic radiatic

137	9.4	Evaluation of radiation by non-amplifying junction photodetectors for chromatic radiation (mixed radiation)
139	9.5	Evaluation of radiation by amplifying junction photodetectors
144	9.6	Area-dependent sensitivity values for junction photodetectors
145	9.7	Actinic values of IR luminescence radiation from GaAs diodes for silicon junction photodetectors
151	9.8	Dark current of junction photodetectors
153	9.8.1	Dark current of avalanche photodiodes
154	9.9	Sensitivity parameters of IR detectors
159	10	Parameters common to emitters and receivers
161	10.1	Evaluation of the radiation and receiving characteristics of optoelectronic components
167	10.2	Optical tolerances of optoelectronic components
168	10.2.1	Effect of wafer centering, lens quality, distance from lens to wafer, refractive index of epoxy resin and shape of dome and case
170	10.2.2	Effect of internal case reflections and wafer geometry
173	10.2.3	Tolerance levels which occur
176	10.3	Coupling characteristics, transfer ratios and contrast current ratios of short optical links
176	10.3.1	Coupling characteristics and transfer ratios
181	10.3.2	Contrast ratio
184	10.4	Half-power and half-value points
186	10.5	Dynamic data
191	10.6	Reliability of optoelectronic components
205	11	Parameters of Luminescence diodes
207	11.1	Quantum efficiency
213	11.2	Thermal calculations
213	11.2.1	Basic principles
215	11.2.2	Determination of the thermal resistance
217	11.2.3	Loss power calculation for luminescence diodes in plastic packages
217	11.2.4	Loss power calculation for luminescence diodes in metal cans with infinitely large heat-sinks
217	11.2.5	Loss power calculation for luminescence diodes in metal cans without heat-sink
218	11.2.6	Loss power calculation for luminescence diodes in metal cans with heat-sink
218	11.2.7	Calculation of the maximum permissible forward current
220	11.3	Radiant power
223	11.4	Radiant efficiency
224	11.5	Spectral radiant efficiency
226	11.6	Electrical parameters
228	11.7	Pulse operation

231	12	Radiation measurements
233	12.1	General Considerations
233	12.2	Measurement of colour temperature of standard light A
235	12.3	Measurement of radiant power with thermal photodetectors
237	12.4	Measurement of radiant power of standard light A with the thermopile
238	12.5	Measurement of irradiance of standard light A with Si photodetectors
240	12.6	Measurement of a luminescence diode radiation with Si photodetectors
240	12.6.1	General measurement problems
242	12.6.2	Measurement of relative spectral sensitivity with a monochromator
242	12.6.3	Measurement of irradiance of a luminescence diode radiation with Si photodetectors
245	12.7	Measurement of the total radiant power of a luminescence diode
247	13	Optoelectronic couplers
249	13.1	Direct optoelectronic couplers
250	13.2	Reflection optoelectronic couplers
252	13.3	Optocouplers with non-stationary source emission
252	13.4	Simple examples of optocouplers
254	13.5	Optocouplers with lenses
259	13.6	Optocouplers with unmodulated optical radiation
260	13.7	Optocouplers with modulated optical radiation
263	14	Operation of luminescence diodes with direct current
265	14.1	Operation through series resistances
265	14.2	Operation from constant-current sources
269	14.3	Drive with logic circuits
273	15	Photodetector circuits
275	15.1	Principle of operation
276	15.2	Detector circuits for two-pole junction photodetectors
276	15.2.1	Direct relay control with phototransistors
276	15.2.2	Photo-Darlington circuits
277	15.2.3	Control of thyristors and triacs with phototransistors
280	15.2.4	Driving of transistor- and operational amplifiers with phototransistors, photodiodes and photocells
285	15.2.5	Driving of multivibrators with phototransistors
288	15.3	Detector circuits for three-pole phototransistors
288	15.3.1	Operating modes of three-pole phototransistors
288	15.3.1.1	Photocell and photodiode operation of the TIL 81 phototransistor
288	15.3.1.2	Advantages of the TIL 81 phototransistor in photocell and photodiode operation
291	15.3.1.3	Phototransistor operation of the TIL 81
293	15.3.2	Driving of amplifiers with three-pole phototransistors

294	15.3.3	Photo-trigger circuits and photomultivibrators
298	15.4	Simple optocouplers with filament lamp and two-pole phototransistors
302	15.5	Logic circuits with phototransistors
304	15.6	Photodetector circuits to drive TTL circuits
309	16	Modulated transmitters with luminescence diodes
311	16.1	The simplest modulator circuits for luminescence diodes
312	16.2	Sine-wave-modulated transmitter with luminescence diodes
313	16.2.1	Modulation operation with bias voltage sources
318	16.2.2	Modulation operation with constant-current sources
320	16.3	Pulse-modulated transmitter with luminescence diodes
325	17	Photodetector circuits for modulated radiation
327	17.1	Circuits with phototransistors
328	17.2	Circuits with the TIL 81 photodetector as photodiode and as photocell
335	18	Practical measurement of the photocurrent sensitivity of Si phototransistors
337	18.1	Theoretical circuits of test equipments
338	18.2	Test equipment for measurement of the relative spectral sensitivity of phototransistors
341	19	Light measurement with Si phototransistors in electronic flash units
343	19.1	Principle of an electronic flash unit
344	19.2	Types of exposure control
345	19.3	Circuit of a flash unit
346	19.4	Si phototransistors for the automatic flash exposure control
349	20	Circuits with light-emitting diodes
351	20.1	Simple indicators
352	20.2	Diode tester
352	20.3	Logic tester
354	20.4	Polarity and voltage tester
355	20.5	Large-format seven-segment display unit
355	20.6	Analogue indication of digital values
357	20.7	Analogue measuring instruments with LED indication
361	21	Numeric and alphanumeric display units
363	21.1	Seven-segment display units
365	21.2	Multiplex operation of display units
368	21.3	Numerical display units with integrated logic
371	21.4	Monolithic display units
374	21.5	5 × 7-point matrix display units

381	22	Direction-dependent photocell units
383	22.1	Principle of operation
384	22.2	Direction-dependent counter
385	22.3	Direction-dependent optocouplers
387	22.4	Digital control knob
389	23	Optoelectronic rangefinder
391	23.1	Phase measurement as a measuring principle
394	23.2	Practical circuit of the rangefinder
399	24	Data transmission with optocouplers
401	24.1	Interference on transmission links
401	24.2	Construction and characteristics of optoelectronic couplers
401	24.2.1	Current transfer ratio
402	24.2.2	Mechanical construction
403	24.2.3	Dynamic performance
403	24.2.3.1	Photodiode operation
404	24.2.3.2	Phototransistor operation
404	24.3	Simple transmission links
406	24.4	Improvement of the switching performance of optocouplers
408	24.5	Optocouplers in photodiode operation
409	24.6	Duplex operation with optocouplers
410	24.7	Common-mode suppression of optocouplers
413	25	Light exposure switch for photographic enlargers
413	25.1	Principle of construction of a light exposure switch
416	25.2	The timing system
418	25.3	Practical circuit of the light exposure switch
419	26	Optoelectronic couplers as switches for analogue signals
421	26.1	Semiconductor switches and potential isolation
421	26.2	The phototransistor as a switch in the optocoupler
421	26.2.1	Steady-state performance
423	26.2.2	Dynamic performance
425	26.3	Application of optocouplers in a digital voltmeter
425	26.3.1	Voltage measurement method used
426	26.3.2	Practical circuit of the digital voltmeter
426	26.3.2.1	Analogue section
428	26.3.2.2	Digital section
429	26.3.2.3	Voltage converter
429	26.4	D.C. voltage amplifier with chopper
431	26.5	Line tester
431	26.5.1	Test principle
433	26.5.2	Practical circuit of the line tester
435		Index