

Contents

Preface	xiii
1 High-voltage technology	1
1.1 Introduction	1
1.2 Classification of voltage levels	2
1.3 Historical development of high voltage	4
1.4 Electricity supply network	6
1.5 Components of a high-voltage system	7
1.5.1 Synchronous generators	7
1.5.2 Transformers.	8
1.5.3 Circuit breakers	11
1.5.4 Lightning arresters (surge diverters)	15
1.5.5 Shielding of transmission lines	17
1.5.6 Overhead lines	19
1.5.7 Cables	21
1.6 Overvoltages.	30
1.6.1 Lightning discharge	30
1.6.2 Lightning frequency	31
1.6.3 Lightning characteristics	34
1.6.4 Travelling waves and their shapes	36
1.6.5 Switching surges	37
1.7 Insulation co-ordination	39
References	41
2 Electrical insulating materials	43
2.1 Introduction	43
2.2 Insulation behaviour of gases	44
2.2.1 Impact ionization by electrons	45
2.2.2 Photoionization	45
2.2.3 Negative-ion formation	46
2.2.4 Simple theory of Townsend breakdown	47

2.3 Practical factors affecting the breakdown voltage	49
2.3.1 Corona	50
2.3.2 Non-uniform fields	52
2.3.3 Time lag to breakdown	54
2.3.4 Compressed gases	55
2.3.5 Vacuum as an insulator	56
2.4 Liquids as insulators	58
2.4.1 Transformer oil	59
2.4.2 Electrical properties of an insulating liquid	60
2.4.3 Breakdown in liquids	63
2.4.4 Synthetic liquids	64
2.5 Solids as insulators	65
2.5.1 Classification of solids	65
2.5.2 Breakdown in solids	66
2.6 Liquid-solid insulators	72
References	73
3 Field plotting	76
3.1 Introduction	76
3.2 Curvilinear squares: an approximate graphical method	77
3.3 Analogue methods.	79
3.3.1 Conducting paper	79
3.3.2 The electrolytic tank	79
3.4 Analytical methods	80
3.4.1 Direct solution of Laplace's equation	81
3.4.2 Using a conformal transformation	81
3.5 Numerical methods	86
3.5.1 Monte Carlo methods	86
3.5.2 Integral methods	87
3.5.3 Differential methods	89
3.5.4 Comment on numerical methods	91
3.6 Use of field plots in high-voltage design	92
References	93
4 Generation of high voltages	94
4.1 Alternating voltages	94
4.1.1 Single step-up transformers	94
4.1.2 Transformers in cascade	95
4.1.3 Voltage control of testing transformers	96
4.1.4 Series resonant circuits	98
4.2 Direct voltages	99
4.2.1 Half-wave and full-wave rectification	99
4.2.2 Voltage doubler and cascade circuits	100
4.2.3 Electrostatic generators	102

4.3 Impulse voltages	103
4.3.1 Single-stage generator	104
4.3.2 Multi-stage Marx generator	105
4.4 Practical multistage generators	108
4.4.1 Nominal characteristics of generators	108
4.4.2 Tripping of generator	112
4.4.3 Recording of impulse	114
4.4.4 Polarity of impulse	114
4.5 Impulse currents	115
References	116
5 High-voltage measurement	117
5.1 Introduction	117
5.2 Electrostatic voltmeters	117
5.3 Flashover between spheres	118
5.4 Voltage measurement using an ammeter and series resistor	120
5.5 Low-voltage instruments with potential dividers	121
5.5.1 Resistor dividers	121
5.5.2 Capacitor dividers	125
5.5.3 Mixed dividers	127
5.5.4 Low-voltage measuring instruments	127
5.6 Measurement of peak voltages	129
5.7 The field-mill (generating) voltmeter	132
5.8 Voltage transformers	133
5.9 Current measurements	134
5.9.1 Current transformers	134
5.9.2 Current shunts	135
5.9.3 The Rogowski coil	137
5.9.4 Hall-effect probes	137
5.9.5 Faraday-effect current transformers	137
5.10 Measurement of dielectric loss	138
5.10.1 The Schering bridge	139
5.10.2 Bridges for measuring low losses	141
References	141
6 High-voltage testing	143
6.1 Introduction	143
6.2 Types of test	143
6.3 Power-frequency tests	144
6.3.1 Dry withstand test	144
6.3.2 Wet withstand test	145
6.3.3 Separate-source-voltage withstand test	146
6.4 Impulse withstand test	147
6.4.1 Impulse voltage distribution in transformers	149

6.4.2	Testing a transformer	151
6.4.3	Transmission-line insulators	155
6.4.4	Cables	157
6.4.5	Circuit breakers	158
References		160
7	Partial discharges	162
7.1	Introduction	162
7.2	The discharge process	163
7.2.1	The process in voids	163
7.2.2	The process at electrodes	164
7.2.3	Discharge patterns in cavities	165
7.2.4	The energy in a discharge	166
7.2.5	Damage to the dielectric	168
7.3	The detection and measurement of discharges	169
7.3.1	The observable effects of discharges	169
7.3.2	Power loss in the dielectric	169
7.3.3	Straight current-pulse and voltage-pulse techniques	171
7.3.4	Balanced methods	172
7.3.5	Discharge measurement in power-system apparatus	174
7.3.6	Calibration methods	176
7.4	The location of discharges	177
7.4.1	Electrical methods	177
7.4.2	Acoustical methods	179
7.4.3	Other methods	180
7.5	Surface discharges	180
7.6	Discharges in direct-voltage systems	182
7.6.1	The discharge process	182
7.6.2	Discharge detection	183
7.6.3	Conclusions	183
References		184
8	High-voltage design and applications	185
8.1	Introduction	185
8.2	High-voltage bushings	185
8.2.1	The simple bushing	185
8.2.2	Grading of bushing insulation	186
8.2.3	Other design considerations	188
8.3	Power cables	189
8.3.1	Historical problems and solutions	189
8.3.2	Self-contained oil-filled designs	190
8.3.3	High-pressure oil-filled cables	192
8.3.4	Solid dielectric cables	193
8.3.5	Accessories	194

8.3.6 Compressed gas-insulated designs	196
8.3.7 D.c. transmission cables	197
8.3.8 Other cable designs.	198
8.4 Transformers	199
8.4.1 Transformer insulating materials	199
8.4.2 Winding design	200
8.4.3 The surge voltage problem	201
8.5 Switchgear	202
8.5.1 Insulation in switchgear	202
8.5.2 Oil circuit breakers	204
8.5.3 Air-blast circuit breakers	205
8.5.4 Sulphur hexafluoride circuit breakers.	206
8.5.5 Vacuum circuit breakers	207
8.6 Overhead lines	208
8.6.1 Conductor arrangements	208
8.6.2 Insulators	209
8.7 Applications.	212
8.7.1 Electrostatic precipitators	212
8.7.2 Paint spraying and powder coating	213
8.7.3 Ore separation	214
8.7.4 Propulsion of space vehicles	214
8.7.5 High-energy physics	215
8.8 Electrostatic hazards	215
8.8.1 Sources of unwanted charge	215
8.8.2 Problem situations	215
8.8.3 Prevention of hazards	216
Bibliography	216
Appendix 1 An analysis of the single-stage impulse generator	218
Appendix 2 Screening of resistors	222
Problems	225
Answers to Problems	233
Subject Index	237