

Contents

Preface	ix
Chapter 1 General Background	1
1.1 Definitions for Lossless Lines	1
1.2 Effects of Losses	7
1.3 Basic Electromagnetics	10
1.4 Constitutive Relations	18
1.5 Energy and Power	21
1.6 Basic Circuit Theory	23
Problems	31
Chapter 2 The Lossless LC Line Model	33
2.1 Definitions	33
2.2 TEM Fields on a Homogeneous, Two-Conductor Lossless Transmission Line	38
2.3 Relations for the Magnetic Field	44
2.4 Reactive Parameters of a Transmission Line	46
2.5 TEM Propagation along a Homogeneous, Two-Conductor Lossless Transmission Line	49
2.6 Transmission Line Equations	52
2.7 Energy and Power	59
Problems	63
Chapter 3 Transverse Dependence of the Fields	65
3.1 Laplace's Equation	65
3.2 Coaxial Line	70
3.3 Conformal Mapping	73
3.4 Balanced Bifilar Line	81
3.5 Offset Tubular Line	89
3.6 Flat Conductor Lines	92
3.7 Approximate Methods	101
Problems	109

Chapter 4 Losses	111
4.1 Complex Notation for Sine Waves	111
4.2 Losses in the Propagation Medium	118
4.3 Losses in the Conductors	121
4.4 Transmission Lines at Low Frequencies and dc	125
4.5 Transmission Line at Medium Frequencies	129
4.6 Transmission Line at High Frequencies	131
Problems	137
Chapter 5 Generalized Transmission Line	139
5.1 Definitions	139
5.2 Propagation Factor γ	146
5.3 Equivalent Circuits and Matrices	151
5.4 Reflection Factor and Local Impedance	158
5.5 Energy and Power	161
5.6 Determination of α and β from the Voltage Pattern	164
5.7 Lossy LC Line	168
Problems	172
Chapter 6 Line Ends	175
6.1 Description	175
6.2 Loads	178
6.3 The Smith Chart	183
6.4 Use of Calculator Programs	193
6.5 Boundary Condition at the Generator	197
6.6 Power Transfer from Generator to Load	199
Problems	203
Chapter 7 Matching	205
7.1 Definitions	205
7.2 Matching with a Line Section and a Reactance	213
7.3 Matching with Transformers	216
7.4 Matching with a Double-Stub Tuner	221
7.5 Final Remarks	223
Problems	225
Chapter 8 Periodically Loaded Lines	227
8.1 Introduction	227
8.2 Asymptotic Development	232
8.3 Finite, Periodically Loaded Transmission Line	236
Problems	241
Chapter 9 Coupled Lines	243
9.1 Definitions	243
9.2 General Mathematical Development	246
9.3 Boundary Conditions	250
9.4 Particular Case: Reflectionless Terminations, Excitation of a Single Line	255

9.5 Symmetrical Coupled Lines	259
9.6 Lossless Coupled Lines	261
9.7 Concluding Remarks	263
Problems	264
Chapter 10 Time-Domain Analysis	267
10.1 Signals	267
10.2 Signals on Matched Lines	273
10.3 Signals in Mismatched Transmission Lines	279
Problems	284
Chapter 11 Appendices	285
11.1 Vector Calculus	285
11.2 Integral Relationships	291
11.3 Complex Calculus	293
11.4 Properties of Materials Used in Electrical Engineering	302
Solutions	305
Chapter 1	305
Chapter 2	307
Chapter 3	310
Chapter 4	314
Chapter 5	317
Chapter 6	321
Chapter 7	326
Chapter 8	329
Chapter 9	334
Chapter 10	339
Calculator Codes	345
Complex Calculations	345
Transmission Line Parameters	350
Reflections and Impedances	357
Transfer of Power	360
Periodic Obstacles	362
Pulse Response	365
Bibliography	369
Glossary	375
Index	381