

CONTENTS

APPLICATIONS

Chapter 1 Analysis of Signals

1

- 1-1 Introduction, 1
- 1-2 Classification of Signals, 1
- 1-3 Periodic Signals, 2
 - 1-3.1 Fourier Series, 2
 - 1-3.2 Harmonic Distortion, 9
 - 1-3.3 Correlation, 10
- 1-4 Aperiodic Signals, 13
 - 1-4.1 Fourier Transforms, 13
 - 1-4.2 Spectral Density, 16
 - 1-4.3 Dirac Delta Function, 19
 - 1-4.4 Correlation, 21
 - 1-4.5 Aperiodic Functions Made Periodic, 22
- 1-5 Random Signals, 23
 - 1-5.1 Probability Density Functions, 23
 - 1-5.2 Characteristic Functions, 27
 - 1-5.3 Chi-Square Revisited, 31
 - 1-5.4 Nonstationary, Stationary, and Ergodic Processes, 33
 - 1-5.5 Correlation and Power Spectra, 38
 - 1-5.6 Errors Associated with Determining Probability Density, Correlation, and Power Spectra, 44
- 1-6 Summary, 47
 - 1-6.1 Classification of Signals, 47
 - 1-6.2 Periodic Signals, 47
 - 1-6.3 Aperiodic Signals, 48
 - 1-6.4 Random Signals, 48
 - References, 49

Chapter 2 Filters**51**

- 2-1 Introduction, 51
- 2-2 Ideal Filters, 52
 - 2-2.1 Definition of Impulse Response and Transfer Function, 52
 - 2-2.2 Ideal Filters, 54
 - 2-2.3 Impulse Response of Ideal Filters, 54
 - 2-2.4 Correlation and Spectral Density, 56
 - 2-2.5 Basic Properties of Filters, 60
- 2-3 Nonideal (Practical) Filters, 64
 - 2-3.1 Introduction, 64
 - 2-3.2 *RC* Filters, 68
- 2-4 Types of Practical Filters, 71
 - 2-4.1 General Classification, 71
 - 2-4.2 Octave Filters, 72
 - 2-4.3 Frequency Analyzers, 72
 - 2-4.4 Tracking Filter, 73
 - 2-4.5 Sweep Spectrum Analyzer, 75
 - 2-4.6 Notch (Rejection) Filter, 76
 - 2-4.7 Comparison of Various Filters, 77
- 2-5 Error Considerations, 79
 - 2-5.1 Introduction, 79
 - 2-5.2 Scan Rates and Averaging Time, 79
 - 2-5.3 Total Analysis Time, 81
- 2-6 Common Practical Filters, 85
 - 2-6.1 Introduction, 85
 - 2-6.2 Butterworth Filters, 85
 - 2-6.3 Chebyshev Filters, 86
 - 2-6.4 Linear-Phase Filters, 86
 - 2-6.5 Comparison of the Three Filters, 87
- 2-7 Matched Filters, 87
- 2-8 Optimum Prediction (Interpolation) Filter, 91
- 2-9 Summary, 92
 - 2-9.1 General, 92
 - 2-9.2 Ideal Filter, 92
 - 2-9.3 Basic Properties of Filters, 92
 - 2-9.4 Practical Filters, 93
- References, 94

Chapter 3 Amplifiers**97**

- 3-1 Introduction, 97
- 3-2 Noise Characterization, 98

- 3-2.1 Introduction, 98
- 3-2.2 Thermal Noise, 98
- 3-2.3 Shot Noise, 99
- 3-2.4 Optimum Noise Source, 100
- 3-3 Noise in an Amplifier, 100
- 3-4 Linearity, 105
- 3-5 Dynamic Range, 106
- 3-6 Impedance Matching, 107
- 3-7 Frequency Response and Rise Time of Cascaded Amplifiers, 115
- 3-8 Negative Feedback in Amplifiers, 116
- 3-9 Operational Amplifiers, 118
- 3-10 Basic Properties of Operational Amplifiers, 119
 - 3-10.1 Introduction, 119
 - 3-10.2 Inverting Feedback Configuration, 120
 - 3-10.3 Noninverting Feedback Configuration, 122
 - 3-10.4 Stability of Operational Amplifiers, 124
 - 3-10.5 Maximum Input and Output Voltage Characteristics, 125
 - 3-10.6 Dc Characteristics of Operational Amplifiers, 126
- 3-11 Operational Amplifiers Used for Signal Conditioning, 126
 - 3-11.1 Introduction, 126
 - 3-11.2 Inverting Amplifier, 127
 - 3-11.3 Noninverting Amplifier, 128
 - 3-11.4 Summing Amplifier, 129
 - 3-11.5 Differential Amplifier, 130
 - 3-11.6 Comparator (Schmitt Trigger), 131
 - 3-11.7 Integrator, 132
 - 3-11.8 Differentiator, 133
 - 3-11.9 Charge Amplifiers, 134
 - 3-11.10 Automatic Gain-Control (AGC) Amplifier, 136
- 3-12 Operational Amplifiers Used with Nonlinear Elements, 141
 - 3-12.1 Introduction, 141
 - 3-12.2 Logarithmic Amplifiers, 141
 - 3-12.3 Diode Function Generators, 142
- 3-13 Applications Using Operational Amplifiers with Nonlinear Elements, 143
 - 3-13.1 Introduction, 143
 - 3-13.2 Inverse Operations, 144
 - 3-13.3 Multiplication and Division, 145
 - 3-13.4 Generation of an Arbitrary Power of the Input, 146

- 3-14 Zero Drive Amplifier, 146
- 3-15 Active Filters, 147
- 3-16 Dc Amplifiers, 150
 - 3-16.1 Introduction, 150
 - 3-16.2 Chopper Amplifier, 150
 - 3-16.3 Chopper-Stabilized Amplifier, 151
- 3-17 Power Supplies, 153
 - 3-17.1 Introduction, 153
 - 3-17.2 Constant-Voltage/Constant-Current Supply, 153
 - 3-17.3 Overvoltage Load Protection, 156
 - 3-17.4 Dual Output Supply, 156
 - 3-17.5 Series and Parallel Operation of Power Supplies, 157
- 3-18 Summary, 157
 - References, 158

Chapter 4 Voltage Detectors **161**

- 4-1 Introduction, 161
- 4-2 Peak Detection, 161
- 4-3 Average Detection, 163
- 4-4 Rms Detection, 165
- 4-5 Summary of Results of Peak, Rectified Average, and rms Detection, 170
- 4-6 Phase Detector (Phase-Lock Amplifier), 171
 - References, 175

Chapter 5 Recorders **177**

- 5-1 Introduction, 177
- 5-2 Oscillograph Recorder, 177
- 5-3 X-Y Plotters, 180
- 5-4 Graphic Level Recorder, 181
- 5-5 Magnetic Tape Recording, 183
 - 5-5.1 Direct Record, 183
 - 5-5.2 Bias, 185
 - 5-5.3 High-Frequency Response, 188
 - 5-5.4 Frequency-Modulated (FM) Recording, 190
 - 5-5.5 Tape-Recorder Heads, 191
 - 5-5.6 Cross Talk, 191
 - 5-5.7 Tape-Transport Mechanisms, 192
 - 5-5.8 Digital Recording, 193

- 5-5.9 Comparison of Recording Techniques, 195
- 5-5.10 Manipulation of Data Using Magnetic Tape, 196
- 5-6 Oscilloscope, 199
 - 5-6.1 General Description, 199
 - 5-6.2 Schmitt Trigger, 200
 - 5-6.3 Delayed Sweep, 203
- 5-7 Fiber-Optic Oscilloscope, 208
- 5-8 Summary, 209
 - References, 210

Chapter 6 Signal Generators 211

- 6-1 Introduction, 211
- 6-2 Sinusoidal Signal Generators, 211
 - 6-2.1 Feedback Oscillators, 211
 - 6-2.2 Beat-Frequency Oscillator, 213
 - 6-2.3 Voltage to Frequency Converters (Voltage-Controlled Oscillators—VCO), 217
- 6-3 Pulse Generators, 219
- 6-4 Random-Noise Generators, 226
- 6-5 Summary, 231
 - References, 232

Chapter 7 Digital Systems—Components and Techniques 233

- 7-1 Introduction, 233
- 7-2 Sampling Principles, 233
 - 7-2.1 Band-Limited Signals, 233
 - 7-2.2 Bandpass Signal, 237
- 7-3 Aliasing Errors, 238
- 7-4 Binary Codes, 241
 - 7-4.1 Straight Binary, 241
 - 7-4.2 Binary-Coded Decimal (BCD), 242
 - 7-4.3 Gray (Cyclic) Code, 243
 - 7-4.4 Complement Codes, 244
 - 7-4.5 Series/Parallel Binary Information, 245
- 7-5 Quantization, 246
- 7-6 Logic Circuits, 248
 - 7-6.1 Introduction, 248
 - 7-6.2 Logic Gates, 248
 - 7-6.3 Shift Register, 251
 - 7-6.4 Counters, 253

- 7-7 Analog-to-Digital Conversion (Digitizing, Encoding), 255
 - 7-7.1 Ramp-Type Converter, 255
 - 7-7.2 Successive-Approximation-Type Converter, 257
 - 7-7.3 Cyclic Converter, 257
 - 7-7.4 Practical Considerations and Limitations of Analog-to-Digital Converters, 258
- 7-8 Digital-to-Analog Conversion (Decoding), 261
- 7-9 Time-Division Multiplexing, 262
- 7-10 Counters, 266
 - 7-10.1 Measurement of Frequency, 266
 - 7-10.2 Measurement of Period and Time Interval, 268
- 7-11 Digital Voltmeters, 270
 - 7-11.1 Introduction, 270
 - 7-11.2 Error Considerations, 271
 - 7-11.3 Digital-Voltmeter Techniques, 272
- 7-12 Digital Delay Line/Transient Recorder, 274
- 7-13 Transient Peak Voltmeter, 275
- 7-14 Small Word-Length Digital Computers, 276
 - 7-14.1 Introduction, 276
 - 7-14.2 Computer Timing and Memory Cycles, 276
 - 7-14.3 Working Registers, 278
 - 7-14.4 Bus System, 280
 - 7-14.5 Instruction Logic, 280
 - 7-14.6 Word Length, Format, and Memory Addressing, 280
 - 7-14.7 Computer Arithmetic Operation, 283
 - 7-14.8 Computer Memory, 284
 - 7-14.9 Software, 288
 - 7-14.10 Input/Output, 288
- 7-15 Signal Averagers, 292
- 7-16 Real-Time Spectrum Analyzers, 295
 - 7-16.1 Introduction, 295
 - 7-16.2 The $\frac{1}{3}$ -Octave Analyzer, 296
 - 7-16.3 Constant Bandwidth Spectrum Analyzer, 297
- 7-17 Summary, 299
 - References, 301

- Glossary** **303**
- Appendix A Decibels** **323**
- Appendix B Transmission Cables** **327**

Appendix C	Ground Loops	331
Appendix D	Types of Signal Sources	333
Appendix E	Amplifier Input Configurations	337
Index		339