

Contents

1. Introduction. By H. Kressel (With 6 Figures)	1
1.1 Background	1
1.2 Outline	5
References	7
2. Laser Diodes and LEDs for Fiber Optical Communication	
By H. Kressel, M. Ettenberg, J. P. Wittke, and I. Ladany (With 38 Figures)	9
2.1 Materials for Heterojunction Structures	11
2.2 The Double-Heterojunction Diode	14
2.2.1 General Description	14
2.2.2 Current Voltage Characteristics	16
2.2.3 Threshold Current Density and Efficiency	16
2.3 Device Fabrication	21
2.3.1 Stripe-Contact Diodes	23
2.3.2 Laser Construction and Packaging	25
2.4 Laser Characteristics	27
2.4.1 Power Emission vs Current of Practical cw Lasers	27
2.4.2 Laser Radiation Patterns	29
2.4.3 Spectral Emission	36
2.4.4 The Power-Current Curve Linearity	36
2.5 Light-Emitting Diodes	37
2.5.1 Structures	37
2.5.2 Optical Power and Fiber Coupling	40
2.5.3 LED-Fiber Coupling and Transmission	40
2.5.4 Carrier Lifetime and Diode Bandwidth	45
2.6 Diode Reliability	52
2.6.1 Facet Damage	52
2.6.2 Gradual Degradation	54
2.6.3 Accelerated Aging Tests	55
2.6.4 Changes in Various Laser Parameters with Aging	58
List of Symbols	59
References	60

3. Photodetectors

By D. P. Schinke, R. G. Smith, and A. R. Hartman (With 12 Figures)	63
3.1 Simple Photodiode Structures	63
3.1.1 Response	63
3.1.2 Reverse Currents	65
3.1.3 Speed of Response	65
3.1.4 Linearity	66
3.2 Avalanche Photodiodes (APD)	66
3.2.1 Principles of Operation	67
3.2.2 Structures	67
3.2.3 Response	69
3.2.4 Speed of Response	70
3.2.5 Noise in Avalanche Photodiodes	72
3.2.6 Linearity and Saturation	77
3.3 Fabrication Technology	78
3.4 Photodiodes for Longer Wavelengths	80
3.4.1 Germanium Photodiodes	81
3.4.2 III-V Compound Semiconductors	82
List of Symbols	85
References	85

4. Receiver Design for Optical Fiber Communication Systems

By R. G. Smith and S. D. Personick (With 40 Figures)	89
4.1 Introductory Remarks	89
4.1.1 General Considerations	89
4.1.2 Scope and Organization	90
4.2 The Basic Receiver	90
4.2.1 Essential Components	90
Photodetector	91
Preamplifier and Amplifier	92
Equalizer	93
Filter	93
4.2.2 Noise Analysis	93
Photodetector Noise	95
Amplifier and Circuit Noise	97
Normalization	98
Values of I_1, I_2, I_3, Σ	103
Bit Rate Dependence of the Noise	110
Noise Corner Frequency	111
4.3 Noise of FET and Bipolar Amplifiers	112
4.3.1 FET Front End	112
Minimum FET Noise	114
Example	115
Effects of Thermal and Shot Noise	115

4.3.2 Bipolar Front End 117
 Optimum Collector Current 119
 Minimum Bipolar Noise 120
 Base Resistance Noise 121
 Example 122
 4.3.3 FET vs Bipolar Front Ends 123
 4.4 Front End Designs 124
 4.4.1 Straightforward Termination 124
 4.4.2 High Impedance or Integrating Front End 125
 4.4.3 Transimpedance Amplifier 126
 4.4.4 Experimental Results 128
 Optimized Transimpedance Amplifier 130
 4.5 Sensitivity of Digital Receivers 132
 4.5.1 Gaussian Approximation 133
 4.5.2 p-i-n Detector 136
 Bit Rate Dependence 138
 Experimental Results 139
 4.5.3 Avalanche Photodetector 139
 Experimental Results 143
 Effect of Finite Extinction Ratio 143
 Multiplied Dark Current 145
 Intersymbol Interference 146
 4.6 Effects of Transmitter and Channel Parameters on System
 Performance 146
 4.6.1 Dispersion and Equalization 147
 4.6.2 Transmitter Parameters 150
 4.7 Analog Systems 151
 4.7.1 p-i-n Detector 152
 4.7.2 Avalanche Detector 153
 4.7.3 Example 153
 4.8 Remaining Work 155
 List of Symbols 156
 References 159

5. Lightwave Transmitters

By P. W. Shumate, Jr. and M. DiDomenico, Jr. (With 32 Figures) 161
 5.1 Characteristics 161
 5.1.1 Power 162
 5.1.2 Spectral Width 163
 5.1.3 Speed 164
 5.1.4 Linearity 165
 5.1.5 Thermal Behavior 165
 5.1.6 Reliability 166
 5.1.7 Other Factors 167
 5.2 Modulation Formats 167

5.3 Source Comparisons	169
5.4 Digital Drive Circuitry	170
5.5 LED Drivers	171
5.6 Laser Drivers	182
5.7 Analog Drive Circuitry	189
5.8 Subsystem Considerations	194
List of Symbols	197
Reference	198
6. Fiber Couplers. By M. K. Barnoski (With 11 Figures)	201
6.1 Source-to-Fiber Coupling	201
6.2 Fiber-to-Fiber Coupling	207
List of Symbols	210
References	211
7. Modulation of Laser Diodes	
By G. Arnold, P. Russer, and K. Petermann (With 25 Figures)	213
7.1 Background	213
7.2 The Rate Equations	214
7.3 Direct Modulation of Injection Lasers	217
7.4 Modulation Behavior of Specific Laser Structures	224
7.5 Effect of Modulation on Spectrum and Near Field	226
7.6 Self-Pulsing Phenomena	231
7.7 Coupled Laser Structures	234
7.8 Outlook	236
List of Symbols	238
References	240
8. The Effect of Junction Heating on Laser Linearity and Harmonic Distortion. By J. K. Butler (With 10 Figures)	243
8.1 Static Laser Characteristics	243
8.2 Transient Analysis	244
8.3 Harmonic Analysis	249
8.4 Conclusion	256
List of Symbols	257
9. An Illustrative Optical Communication System	
By J. H. Mullins (With 12 Figures)	259
9.1 Background and Purpose	259
9.1.1 General Fiber Optic System and Range of Applications	259
9.1.2 Economic Considerations	260
9.1.3 Other Considerations	262
9.2 Digital Interoffice Trunking	263
9.2.1 The Telephone Trunk Network	263
9.2.2 Conventional Digital Metallic Facilities	263

9.2.3 The Physical Environment 264

9.2.4 Comparative Economics 265

9.3 The Chicago Lightwave Project, System Components 266

9.3.1 Basic System Parameters 266

9.3.2 Cable and Splicing 268

9.3.3 Cable Terminations and Single Fiber Connectors 269

9.3.4 Optical Components – Laser, LED, APD 271

9.3.5 Electronic Components – Regenerator 272

9.3.6 Test Equipment 273

9.4 Configuration and Installation of the System 276

9.4.1 Route Description 276

9.4.2 System Configuration 277

9.4.3 Installation of the Cable 278

9.4.4 Installation of Equipment 279

9.5 Performance and Results 279

9.5.1 Cable Characteristics 279

9.5.2 Electro-Optical Performance 281

9.5.3 Current Performance and Future Prospects 281

9.6 Concluding Remarks 282

References 283

10. Light Sources – an Update

By H. Kressel and M. Ettenberg (With 3 Figures) 285

10.1 InGaAsP/InP Devices 285

10.2 AlGaAs Devices 289

10.3 Applications 291

References 291

11. Photodetectors and Receivers – an Update

By R. G. Smith (With 2 Figures) 293

11.1 Material for Photodetectors 293

11.1.1 Germanium 293

11.1.2 InGaAsP 294

11.1.3 GaAlAsSb 294

11.2 *p-i-n* Photodiodes 294

11.2.1 Dark Current 295

11.2.2 Quantum Efficiency 296

11.2.3 Speed of Response 297

11.3 Avalanche Photodetectors 297

11.4 Other Detectors 299

11.5 Receivers 299

11.6 Heterodyning 300

References 301