



# Contents

**Preface**

xxxiii

## **1. CHARACTERISTICS OF RESISTORS**

1.1	Introduction	1-1
1.2	General Description	1-1
1.3	Resistor Terms and Parameters	1-3
	Resistance	1-3
	Tolerance	1-3
	Temperature Coefficient of Resistance	1-3
	Power Rating	1-3
	Rated Continuous Working Voltage	1-4
	Critical Resistance	1-4
	Noise	1-4
	Frequency Effects	1-4
	Drift	1-5
	Taper	1-5
	Resolution	1-6
	End Resistance	1-6
	Contact Resistance	1-6
	Wiper (Slider) Current	1-6
	Setting Stability	1-6
1.4	Fixed Resistors	1-8
	Carbon Composition	1-8
	Metal Film	1-8
	Thin film	1-8
	Tin oxide	1-8
	Metal glaze	1-8
	Cermet	1-9
	Bulk film	1-9
	Carbon Film	1-9
	Wire-wound	1-10
1.5	Color Coding of Resistors	1-11
1.6	Connecting Resistors	1-11
	Resistors in Series	1-11
	Resistors in Parallel	1-12

1.7	Special Resistors	1-13
	High-Voltage Resistors	1-13
	High-Megohm Resistors	1-13
	DIP Networks	1-13
1.8	Variable Resistors (Pots)	1-13
	Types of Materials	1-15
	Carbon	1-15
	Cermet	1-15
	Conductive plastic	1-15
	Wire-wound	1-16
	Rheostat	1-16
1.9	Chip Resistors	1-16
1.10	Thermistors	1-16
	Characteristic Curves and Parameters	1-16
	Resistance-temperature characteristic	1-16
	Static voltampere characteristics	1-17
	Current-time characteristic	1-18
1.11	Varistors	1-19

## **2. CHARACTERISTICS OF CAPACITORS**

2.1	Introduction	2-1
	Applications	2-1
2.2	General Description	2-1
	Relative Dielectric Constant	2-3
	Charge and Energy	2-3
2.3	Capacitor Terms and Parameters	2-4
	Capacitance	2-4
	Ambient Temperature	2-4
	Tolerance	2-4
	Temperature Coefficient	2-5
	Working Voltage	2-5
	Breakdown Voltage	2-5
	DC Leakage	2-5
	Insulation Resistance	2-5
	Capacitive Reactance	2-5
	Power Factor	2-5
	Equivalent Series Resistance	2-6
	Impedance	2-6
	Dissipation Factor	2-6
	Quality Factor (Q)	2-7
	Ripple Current and Voltage	2-7
2.4	Fixed Capacitors	2-7
	Mica	2-7
	Silvered Mica	2-8
	Paper	2-8
	Plastic Film	2-8
	Ceramic	2-8
	Glass	2-8

	Contents	lx
Vacuum		2-9
Energy Storage		2-9
Metallized Dielectrics		2-9
Electrolytic		2-9
2.5 Connecting Capacitors		2-10
Capacitors in Parallel		2-10
Capacitors in Series		2-10
2.6 Color Coding of Capacitors		2-11
2.7 Variable Capacitors		2-11
Trimners		2-12
2.8 Chip Capacitors		2-13
2.9 Voltage-Variable Capacitors (Varactors)		2-15
Parameters		2-16
Total diode capacitance ( $C_1$ )		2-16
Series resistance ( $R_s$ )		2-16
Figure of merit ( $Q$ )		2-16
Cutoff frequency ( $f_{co}$ )		2-16
Variation of capacitance with temperature		2-16
$C_1$ ratio		2-16
Conversion efficiency ( $\eta$ )		2-17

### 3. COILS

3.1 Introduction	3-1
3.2 Types of Ferrous Cores and Their Effects in Coils	3-1
Iron-Power Cores	3-1
Ferrite Cores	3-1
Laminated Cores	3-1
Tuning Cores, Slugs, and Toroids	3-3
Core Permeability	3-3
3.3 Types of Nonferrous Cores	3-3
3.4 Computing the Inductance of Air-Core Coils	3-3
3.5 Mutual Inductance	3-5
Coupled Coils in Series and in Parallel	3-6
Computing the Mutual Inductance of Single-Layer Air-Core Coils	3-7
3.6 Computing the Value of Inductance from Measurements	3-9
3.7 The Coefficient of Coupling	3-10
3.8 Coil and Conductor Resistance at Radio Frequencies	3-10
Eddy Currents in Conductors	3-10
Dielectric Losses	3-10
Distributed Capacitance	3-11
3.9 Methods Used to Decrease Skin Effect, Eddy Current Loss, Dielectric Loss, and Distributed Capacitance in Coils	3-11
Litzendraht, or Litz, Wire	3-11
Flat Copper Strip	3-11
Tubular Conductors	3-12
Special Winding Methods Used to Reduce Distributed Capacitance	3-12
The Use of Powdered Iron and Ferrite Cores	3-12
3.10 The $Q$ or Figure of Merit of a Coil	3-13

3.11 True Inductance and Apparent Inductance	3-14
3.12 Determining the Self-Resonant Frequency of an Inductor	3-14
3.13 Determining the Distributed Capacitance of a Coil by Measurement	3-15
3.14 Measuring Coil Inductance	3-16
Measuring High Inductance R-F Chokes	3-17
3.15 Determining the Q of a Coil	3-17
3.16 Coils with Powdered Iron or Ferrite Cores	3-18
3.17 Computing Iron Powder and Ferrite-Core Coils	3-18
3.18 Change of Coil Inductance with Direct Current	3-23
3.19 Testing and Measuring Iron-Powder and Ferrite-Core Coils	3-23
3.20 Measuring Method for Coils Carrying Both R-F and DC	3-24
3.21 Nomograms	3-24

#### **4. MAGNETIC CIRCUITS**

4.1. Introduction	4-1
4.2 Magnets, Natural and Artificial	4-1
4.3 Magnetic Materials	4-1
4.4 The Magnetic Compass	4-3
4.5 Magnetic Poles	4-3
Coulomb's Law	4-4
The Unit Magnetic Pole	4-4
Magnetic Pole Computations	4-4
4.6 The Earth's Magnetic Field	4-5
4.7 Electromagnetism	4-5
The Right-Hand Rule and the Left-Hand Rule for Magnetic Fields Around Wires	4-6
4.8 The Right-Hand Rule and the Left-Hand Rule for Coils	4-6
4.9 Units of Measurement in Magnetics	4-7
Magnetic Flux	4-7
Unit Poles	4-7
Flux Density	4-8
Magnetomotive Force	4-8
Reluctance	4-9
Comparison of Electric and Magnetic Circuits	4-9
Magnetizing Force	4-10
Relative Permeability	4-11
4.10 Rowland's Law	4-11
4.11 Reluctances in Series	4-12
4.12 Reluctances in Parallel	4-13
4.13 Variation of Permeability with Magnetizing Force	4-14
Magnetization Curves	4-14
4.14 Magnetic Circuit Computations	4-16
4.15 Electromagnets	4-17
4.16 Saturation	4-17
4.17 Retentivity	4-18
4.18 Coercivity or Coercive Force	4-18

4.19 Hysteresis	4-19
4.20 Eddy Currents	4-19
4.21 Iron-Powder Cores	4-20

## **5. TRANSFORMERS**

5.1 Introduction	5-1
5.2 The Basic Transformer	5-1
5.3 Mutual Induction	5-1
5.4 Transformer Voltage Relationships	5-4
5.5 Transformer Current Relationships	5-5
5.6 The Fundamental Equation of the Transformer	5-6
5.7 Discussion of No-Load Conditions	5-8
5.8 Vector Representation of No-Load Conditions	5-9
5.9 Conditions Under Load	5-11
5.10 Operating a Transformer on Lower or Higher than Rated Frequency	5-12
5.11 Connecting Transformers in Series and Parallel	5-14
Series Operation	5-14
Parallel Operation	5-14
Phasing Transformers for Parallel Operation	5-14
5.12 Transformer Losses	5-15
Copper Loss	5-15
Determination of Copper Loss	5-15
Core-Loss Test	5-16
5.13 Efficiency	5-17
5.14 Equivalent Resistances	5-18
5.15 Voltage Regulation	5-19
5.16 The Isolation Transformer	5-21
5.17 The Autotransformer	5-21
5.18 The Variable Autotransformer	5-24
Using Variable Autotransformers at Higher than Rated Voltages	5-26
Switching	5-26
5.19 Instrument Transformers	5-26
The Potential Transformer	5-27
The Current Transformer	5-27
5.20 Transformers in Two- and Three-Phase Systems	5-28
Connecting Three Separate Transformers for Three-Phase Operation	5-28
Wye-to-Wye Transformation	5-29
Delta-to-Delta Transformation	5-29
Wye-to-Delta Transformation	5-30
Delta-to-Wye Transformation	5-31
5.21 The Scott or T Connection	5-32
Two-Phase to Three-Phase Transformation	5-33
Three-Phase to Two-Phase Transformation	5-33
5.22 Filter Chokes	5-34
5.23 Swinging Chokes	5-36
5.24 The Tuned Filter Choke	5-36

5.25 Transformer Cores	5-37
Laminations	5-38
Grain-Oriented Laminations	5-40
Tape-Wound Cores	5-41
Tape-Wound Bobbin Cores	5-41

**6. PRACTICAL CIRCUIT ANALYSIS**

6.1 Introduction	6-1
6.2 Notation	6-1
6.3 Definitions	6-1
Passive and Active Elements	6-1
Ideal Elements	6-1
Resistor $R$	6-1
Inductor $L$	6-2
Capacitor $C$	6-2
Voltage source $e$	6-2
Current source $i$	6-2
Dependent (controlled) sources	6-2
Model	6-2
Linear Element	6-3
Nonlinear Element	6-3
Linear Circuit	6-3
Nonlinear Circuit	6-3
Series Circuit	6-3
Parallel Circuit	6-3
6.4 $RC$ and $RL$ Circuits	6-3
6.5 Energy and Power	6-5
6.6 Circuit Laws and Theorems	6-5
Kirchhoff's Laws	6-5
Conductance	6-8
6.7 Topology of Networks	6-8
6.8 Equivalent Resistance	6-9
Resistors in Series	6-9
Resistors in Parallel	6-9
Resistors in Series-Parallel	6-10
6.9 Voltage Divider	6-10
6.10 Current Divider	6-10
6.11 Superposition Theorem	6-11
6.12 Thévenin's Theorem	6-12
6.13 Norton's Theorem	6-14
Source Conversion	6-14
6.14 Periodic Waveforms	6-15
6.15 Sine Wave	6-15
Basic Definition	6-16
Frequency	6-16
Period	6-16
Angular Frequency	6-17

Phase Angle	6-17
Phase Relationships	6-18
6.16 Average (DC) Value of Waveforms	6-19
6.17 Effective (RMS) Value of Waveforms	6-19
6.18 Complex Numbers	6-20
Complex Conjugate	6-20
Adding and Subtracting Complex Numbers	6-21
Multiplying and Dividing Complex Numbers	6-21
6.19 Reactance	6-22
Equivalent Reactance	6-22
6.20 Impedance and Admittance	6-22
Admittance	6-23
Ohm's Law for AC Circuits	6-23
6.21 Phasor Diagrams	6-24
6.22 AC Circuit Analysis	6-25
6.23 Power in AC Circuits	6-26
Reactive Power	6-27
Apparent Power	6-27
6.24 Maximum Power Transfer Theorem	6-28

## **7. METERS AND MEASUREMENTS**

7.1 Introduction	7-1
7.2 Parallax and Other Problems in Using Instruments	7-1
7.3 Percent Accuracy	7-3
7.4 Basic Instruments and Their Use for Servicing Electronics	
Equipment	7-3
Ammeters	7-3
Voltmeters	7-4
Ohmmeters	7-5
Multimeters	7-6
7.5 Meter Movements in Measuring Instruments	7-8
Meters that Utilize the Magnetic Field of a Current for Measurement	7-9
Moving-Coil Meters	7-9
Meters that Depend on the Heating Effect of a Current	7-11
7.6 Meter Circuits	7-11
Calculation of Meter Shunts	7-11
Calibration of Current-Reading Meters	7-13
Calculation of Meter Multipliers	7-14
7.7 Vacuum-Tube Voltmeters	7-16
7.8 Digital Multimeters	7-18
Digital Displays	7-19
Theory of Operation	7-20
The 1/2 digit	7-21
Digital meter specifications	7-21
7.9 Calibration of Voltmeters	7-22
Ohmmeter Circuits	7-22



7.10	Determination of Meter Resistance	7-24
7.11	The Wheatstone Bridge	7-25
7.12	AC Bridges	7-28
	Resonance and Frequency Bridges	7-28
	Inductance Bridges	7-29
	Capacitance Bridges	7-32

**8. SEMICONDUCTOR DEVICES AND TRANSISTORS**

8.1	Introduction	8-1
8.2	Elementary Semiconductor Theory	8-1
	Atomic Structure	8-1
	Energy Bands	8-3
	Doping	8-4
	n-Type Silicon	8-4
	p-Type Silicon	8-5
8.3	Junction Diode	8-5
	Diode Characteristics	8-5
	Rectifier, R-F, and Switching Diodes	8-7
	Diode Parameters	8-7
8.4	Zener Diodes	8-8
	Zener and Avalanche Breakdown	8-8
	Regulator and Reference Diodes	8-9
	Double-Anode Regulator	8-9
	Zener Diode Parameters	8-9
8.5	Bipolar Junction Transistor	8-9
	Operation of the BJT	8-10
	BJT Parameters and Curves	8-12
8.6	Field-Effect Transistor	8-13
	Junction FET	8-13
	Operation	8-14
	MOSFET	8-15
	Operation of depletion-type MOSFET	8-15
	Operation of enhancement-type MOSFET	8-17
	FET Parameters	8-17
8.7	Silicon-Controlled Rectifier	8-18
	Operation of the SCR	8-19
	Light-Activated SCR	8-20
	Characteristic Curves	8-20
	SCR Parameters	8-21
8.8	Bidirectional Triode Thyristor	8-21
8.9	Unijunction Transistor	8-22
	Operation of the UJT	8-22
	Programmable Unijunction Transistor	8-24
	UJT Curves and Parameters	8-24
8.10	Light-Emitting Diode	8-25
	Characteristic Curves	8-25
	LED Parameters	8-26

8.11 Other Semiconductor Devices	8-26
Tunnel Diode	8-26
Schottky Barrier Diode	8-27
Photodiodes	8-27
Phototransistor	8-28
Opto-Isolator	8-28
Charge-Coupled Device	8-28
Microwave Power Diodes	8-29
8.12 Semiconductor Chips	8-30
Flip Chip	8-30
Beam-Lead Device	8-30
Leadless Inverted Device	8-30
8.13 Understanding Data Sheets	8-30

## **9. INTEGRATED CIRCUIT TECHNOLOGY**

9.1 Introduction	9-1
9.2 Dimensioning Integrated Circuits	9-1
9.3 Monolithic Technology	9-1
Basic Processing Steps	9-2
P-type substrate	9-3
Epitaxial layer	9-3
Oxide layer	9-3
Photoresist	9-4
Artwork	9-4
Exposure of collector mask	9-6
Diffusion	9-6
Etching	9-7
p-type diffusion	9-7
Oxidation and resist	9-8
Exposure to base mask	9-8
Base diffusion	9-8
Oxidation and resist	9-8
Forming the emitter	9-8
Exposure to $n^+$ mask	9-8
$n^+$ diffusion	9-8
Oxidation and resist	9-8
Exposure to contact mask	9-8
Metallization	9-8
Exposure to interconnection mask	9-9
Testing and packaging	9-9
9.4 Electrical Isolation	9-9
Junction Isolation	9-9
Dielectric Isolation	9-9
Beam-Lead Isolation	9-9
Parasitics	9-10
9.5 Properties and Characteristics of Diffused Elements	9-10
Bipolar Junction Transistor (BJT)	9-10
Lateral pnp Transistor	9-10

Field-Effect Transistor (FET)	9-11
Diode	9-11
Resistor	9-11
Four-Point Probe	9-12
Capacitor	9-12
Inductor	9-13
9.6 Making a Monolithic IC	9-13
Isolation mask	9-14
p-diffusion mask	9-14
n <sup>+</sup> diffusion mask	9-14
Contact and interconnection masks	9-14
Buried Crossover	9-15
9.7 Large-Scale Integration (LSI)	9-16
9.8 Thin-Film Technology	9-16
Producing Thin Films	9-17
Thin-Film Components	9-17
Resistor	9-17
Capacitor	9-18
Inductor	9-18
Thin-Film Processing	9-19
9.9 Thick-Film Technology	9-19
Screen-Process Printing	9-19
Thick-Film Pastes (Inks)	9-20
Thick-Film Components	9-21

## **10. TUNED CIRCUITS**

10.1 Introduction	10-1
Analogies	10-2
Some Uses of Tuned Circuits	10-2
10.2 Types of Tuned Circuits	10-3
Fixed-Tuned Circuits	10-3
Tunable Circuits	10-4
Circuit Bandwidth	10-4
Single-Tuned and Double-Tuned Circuits	10-4
Series-Tuned and Parallel-Tuned Circuits	10-5
10.3 Comparison of Series-Tuned and Parallel-Tuned Circuits	10-5
10.4 Series-Tuned Circuits	10-5
Applications	10-5
Fundamentals	10-6
Series-Tuned Voltages at Resonance	10-8
10.5 Parallel-Tuned Circuits	10-10
Applications	10-10
Fundamentals	10-11
10.6 Selectivity Bandwidth, and Q Factor	10-15
Bandwidth	10-15
Q Factor	10-16
Application Requirements	10-18
10.7 Double-Tuned (Multiple-Tuned) Circuits (also called Stagger Tuned)	10-18

10.8 Coupled Tuned Circuits	10-20
Critical Coefficient of Coupling	10-21
10.9 Temperature Compensation of Tuned Circuits	10-22
Selecting a Temperature-Compensating Capacitor	10-23
Practical Considerations	10-24

## **11. FILTERS**

11.1 Introduction	11-1
11.2 Classification of Filters	11-1
Applications	11-2
11.3 Filter Terminology	11-4
11.4 Filter Components	11-6
11.5 Methods of Designing LC Filters	11-6
Image-Parameter Design	11-6
Network Method of Design	11-7
11.6 The Significance of Filter Impedance	11-7
11.7 Design of Constant-k Filters	11-9
Low-Pass Filter Design	11-9
High-Pass Constant-k Filter Design	11-11
Bandpass Filter Design	11-12
Band-Rejection Filter Design	11-14
11.8 Summary of Constant-k Filter Characteristics	11-15
11.9 m-Derived Filters	11-15
Low-Pass m-Derived Filter Design (Series Type)	11-17
Low-Pass m-Derived Filter Design (Shunt Type)	11-17
High-Pass m-Derived Filter Design (Series Type)	11-18
High-Pass m-Derived Filter Design (Shunt Type)	11-19
11.10 Summary and Design Example of m-Derived Filters	11-19
11.11 Some Additional Types of Filters	11-21
Butterworth Filter	11-22
Chebyshev Filter	11-22
Crystal Filter (sometimes called "Quartz Filter")	11-22
Ceramic Filter	11-23
Mechanical Filters (also called "Magnetostrictive Filters")	11-25
11.12 Active Filters	11-26
High-pass filter	11-28
Bandpass filter	11-29
Band-reject filter	11-29

## **12. TRANSISTOR AMPLIFIERS AND OSCILLATORS**

12.1 Introduction	12-1
12.2 Classification of Amplifiers	12-1
12.3 Characteristics of Amplifiers	12-2
Voltage Gain	12-3
Current Gain	12-3
Power Gain	12-3
Input Resistance	12-3
Output Resistance	12-3

Bandwidth	12-3
Distortion	12-4
Harmonic distortion	12-4
Intermodulation distortion	12-4
Slewing Rate	12-4
12.4 Biasing and Stabilization	12-4
Biasing the Common-Emitter Amplifier	12-4
Biasing the Common-Base Amplifier	12-6
Biasing the Emitter Follower	12-7
Stabilizing the Common-Emitter Amplifier	12-7
Current-feedback stabilization	12-8
Voltage-feedback stabilization	12-8
Bypass and decoupling capacitors	12-9
Diode stabilization	12-9
Biasing JFET and Depletion-Type MOSFET Amplifiers	12-9
Biasing the Enhancement-Type MOSFET	12-11
12.5 Small-Signal Amplifiers	12-11
Analyzing the BJT Amplifier	12-11
Simplified hybrid model	12-12
Application of the simplified hybrid model	12-13
Practical considerations	12-14
Analyzing the FET Amplifier	12-15
12.6 Frequency Response of an Amplifier	12-17
High-Frequency Model of Common-Emitter Amplifier	12-17
Simplified hybrid-pi model	12-18
Figures of merit	12-19
High-Frequency Model of Common-Source Amplifier	12-20
Low-Frequency Response	12-21
12.7 Cascading Amplifier Stages	12-21
Coupling Cascaded Stages	12-21
Frequency Response of a Cascaded Amplifier	12-22
12.8 Power Amplifiers	12-22
Class A Power Amplifier	12-23
Collector Dissipation	12-23
Second-Harmonic Distortion	12-24
Push-Pull Power Amplifiers	12-24
Crossover Distortion	12-25
Heat Sinks	12-25
12.9 Feedback Amplifiers	12-26
Properties of Negative Feedback	12-26
Bandwidth	12-28
Distortion	12-28
Instability	12-28
Effects on Input and Output Resistance	12-28
12.10 Sinusoidal Oscillators	12-28
Phase-Shift Oscillators	12-29
Tuned-Circuit Oscillators	12-30
Frequency Stability	12-30
Crystal Oscillators	12-31

## 13. OPERATIONAL AMPLIFIERS

13.1	Introduction	13-1
13.2	The Basic OP AMP	13-1
	Ideal Characteristics	13-1
	Feedback	13-2
13.3	Applications	13-3
	Noninverting Amplifier	13-3
	Difference Amplifier	13-3
	Voltage Follower	13-4
	Summing Amplifier	13-4
	Logarithmic Amplifier	13-5
	Current-to-Voltage Converter	13-6
13.4	Practical Considerations	13-6
	Frequency Response and Compensation	13-6
	Offset	13-8
	Input offset current	13-8
	Input offset voltage	13-8
	Input offset current drift	13-8
	Input offset voltage drift	13-8
	Offset Correction	13-8
	Slewing Rate	13-8
13.5	OP AMP Circuitry	13-9
	Differential Amplifier	13-10
	Current Sink	13-11
	Cascading Stages	13-12
	DC Level Shifter	13-13
	Output Stage	13-13
13.6	Examples of Practical OP AMPS	13-14
13.7	Understanding the Data Sheet for an OP AMP	13-15

## 14. DIGITAL CIRCUIT FUNDAMENTALS

14.1	Introduction	14-1
14.2	Binary Numbers	14-1
	Decimal-to-Binary Conversion	14-2
	Decimal-to-Binary Fraction Conversion	14-2
	Binary-to-Decimal Conversion	14-3
	Binary-to-Decimal Fraction Conversion	14-3
14.3	Diode as a Switch	14-4
14.4	Transistor as a Switch	14-4
14.5	Basic Logic Circuits	14-6
	OR Gate	14-6
	Positive and negative logic	14-7
	OR gate circuit	14-7
	AND Gate	14-7
	AND gate circuit	14-8
	INVERTER	14-8
	INVERTER circuit	14-8

14.6	Half-Adder	14-10
14.7	INHIBIT and EXCLUSIVE OR Gates	14-11
14.8	NAND and NOR Gates	14-12
	NAND Gate	14-12
	NOR Gate	14-13
14.9	Multivibrators	14-14
	Bistable MV	14-15
	Monostable MV	14-16
	Astable MV	14-17
14.10	Dynamic Response of Diode and Transistor Switches	14-17
	Response of a Diode Switch	14-17
	Response of a Transistor Switch	14-18

**15. DIGITAL INTEGRATED CIRCUITS**

15.1	Introduction	15-1
15.2	DIC Terms and Parameters	15-1
	Fan In	15-1
	Fan Out	15-3
	Propagation Delay	15-3
	Speed	15-3
	Gate Dissipation	15-3
	Speed-Power Product	15-3
	Noise Margin	15-3
15.3	T <sup>2</sup> L	15-3
	Standard T <sup>2</sup> L	15-3
	Low-Power T <sup>2</sup> L	15-4
	High-Speed T <sup>2</sup> L	15-5
	Schottky-Clamped T <sup>2</sup> L	15-5
15.4	ECL	15-6
15.5	CMOS	15-7
	Inverter	15-7
	NOR Gate	15-7
	NAND Gate	15-8
15.6	Flipflops	15-8
	R-S Flipflop (Latch)	15-8
	Clocked R-S Flipflop	15-9
	J-K Flipflop	15-10
	T Flipflop	15-11
	D Flipflop	15-12
	Clear and Preset	15-12
	Master-Slave Flipflop	15-13
15.7	Counters	15-13
	Other Types of Counters	15-14
	Up counter	15-14
	Down counter	15-14
	Up-down counter	15-14
	Modulo counter	15-14

15.8	Shift Registers	15-15
	Serial register	15-15
	Serial-in, parallel-out register	15-15
	Parallel-in, serial-out register	15-15
	Parallel-in, parallel-out register	15-15
	Circulating register	15-16
15.9	Semiconductor Memories	15-17
	Types of Memories	15-18
	Access and Cycle Times	15-18
	ROM	15-18
	RAM	15-19
15.10	Digital-to-Analog and Analog-to-Digital Converters	15-19
	D/A Converter	15-20
	A/D Converter	15-23
15.11	The Microprocessor	15-23

## **16. POWER SUPPLIES**

16.1	Introduction	16-1
16.2	Rectifier Systems	16-1
	Half-Wave Rectifiers	16-2
	Filtering	16-3
	Full-Wave Rectifiers	16-4
	Tube Rectifiers	16-6
	Bridge Rectifiers	16-7
	Half-Wave Voltage Doublers	16-9
	Full-Wave Voltage Doublers	16-10
	Voltage Triplers and other Voltage Multipliers	16-10
	Load versus Load Resistance	16-12
	Combination Positive and Negative Supplies	16-12
16.3	Regulated Power Supplies	16-13
	Basic Types	16-15
	Series type	16-15
	Shunt type	16-15
	Switching type	16-15
16.4	Power-Supply Regulator Circuits	16-16
16.5	Characteristics of Filtering Circuits for Unregulated Supplies	16-18
16.6	Specifications	16-20
	Regulation	16-20
	Temperature Coefficient	16-20
	Stability	16-20
	Transient Response	16-21
	Ripple	16-22
16.7	Special Design Features	16-23
	Remote Sensing	16-23
	Remote Programming	16-23
	Overvoltage Protection	16-24
	Undervoltage Protection	16-26



**17. BATTERIES**

17.1	Introduction	17-1
	General Considerations	17-2
	Primary Battery	17-2
	Secondary Battery	17-3
	Reserve Batteries	17-3
17.2	Characteristics of Important Commercial Primary Batteries	17-5
	Basic Types	17-5
	Polarization of Dry Cells	17-5
	Performance Data	17-6
	American Standards Association Requirements	17-9
	Shelf Life	17-10
	Alkaline Batteries	17-11
	Mercury Dry Batteries	17-13
	Magnesium Dry Batteries	17-15
17.3	Characteristics of Important Commercial Secondary Types	17-17
	Lead-Acid Battery	17-17
	Nickel-Cadmium Batteries	17-19
	Silver-Zinc Batteries	17-22
17.4	Maintenance	17-24
	Lead-Acid Battery Maintenance	17-24
	Sealed Units	17-25
	Charging Nickel-Cadmium Batteries	17-26
	Charging Silver-Zinc Batteries	17-26
17.5	Special Types	17-27
	Magnesium Batteries	17-28
	Organic Depolarized Batteries	17-28
	Cuprous Chloride-Magnesium Batteries	17-28
	Silver Chloride-Magnesium Batteries	17-29
	Air-Depolarized Batteries	17-29
	Air-Zinc Batteries	17-30
17.6	Fuel Cells	17-31

**18. MICROPROCESSORS AND MICROCOMPUTERS**

18.1	Introduction	18-1
18.2	Transporting Digital Words	18-2
18.3	Introduction to Microprocessor Systems	18-4
	Microcomputers	18-5
18.4	The 8085 Microprocessor	18-6
	Registers	18-6
	Stack Pointers	18-7
	Program Counter	18-7
	Arithmetic Logic Unit	18-8
	Address Latch Incrementer-Decrementer	18-8
	Data or Address Buffer	18-8
	Instruction Register and Decoder	18-8

	<b>Contents</b>	<b>xxiii</b>
Timing and Control		18-8
Interrupt Control		18-8
Serial I/O Control		18-9
Basic System Timing		18-9
Multiplexing		18-10
Types of Addressing		18-11
18.5 The 8085 Instruction Set		18-13
Data Transfer Group		18-13
Arithmetic and Logic Group		18-16
Branch Control Group		18-18
Stack, I/O, and Machine Control Group		18-18
18.6 Software—Writing a Program		18-19
Steps in Writing a Program		18-19
Subroutines		18-21
18.7 Support Devices		18-22
Decoders		18-22
I/O Ports		18-22
Programmable Peripheral Interface (PPI)		18-22
Other Support Devices		18-22
18.8 Microprocessor Survey		18-23
Extended Addressing		18-23
Implied Addressing		18-24
Accumulator Addressing		18-24
Indexed Addressing		18-24
Relative Addressing		18-24
Comparison of Microprocessors		18-24
Intel 8080		18-24
Z80		18-24
6800		18-25
6502		18-25
18.9 Summary		18-26

## **19. LOGIC ANALYZERS, LOGIC PROBES, AND SIGNATURE ANALYSIS**

19.1 Introduction to Logic Analyzers	19-1
19.2 Review of Digital Circuitry	19-1
19.3 Types of Faults in Digital Systems	19-3
Hardware Faults	19-3
No data	19-3
Glitches	19-3
Spikes	19-3
Races	19-4
Timing errors	19-4
Ringing	19-4
Wrong level	19-5
Software Faults	19-5
Wrong instructions	19-5
Latent faults	19-5

Timing faults	19-5
Memory defects	19-5
19.4 Requirements on Logic Analyzer	19-6
19.5 Basic Principles of the Logic Analyzer	19-6
Memory	19-6
Trigger Function	19-7
Data Acquisition	19-7
Display	19-8
19.6 Main Functions of a Logic Analyzer	19-10
Data Acquisition	19-10
The clock	19-10
Data input	19-10
Setup and hold times	19-11
Clock qualifiers	19-12
Start function	19-12
Trigger Function	19-12
Manual triggering	19-13
Internal triggering	19-13
External triggering	19-15
Trigger delay	19-15
Display	19-17
Synchronous and Asynchronous Sampling	19-20
19.7 Applications of the Logic Analyzer	19-21
Exercises in Monitoring Data Transport Via Bus Lines	19-21
19.8 Glossary of Logic Analyzer Terms	19-26
Triggering	19-26
Sampling	19-27
Display	19-27
Memory	19-27
General	19-28
Common Microprocessor Terminology	19-28
19.9 Logic Probe	19-30
19.10 Logic Pulser	19-30
19.11 Signature Analysis for Digital Troubleshooting	19-30
19.12 Basis of Signature Analysis	19-30
19.13 Test Routine in ROMs	19-31
Testing Contents of Several ROMs	19-31
Testing Unknown Boards	19-31
Troubleshooting Techniques	19-32
19.14 The Design of a Signature Analyzer	19-32
Review Questions and Answers About Signature Analysis	19-33

## **20. MICROWAVES**

20.1 Basic Concepts	20-1
Wavelength	20-1
Microwave Region	20-1
Power as a Fundamental Quantity	20-2
Decibels	20-2

	<b>Contents</b>	<b>xxv</b>
20.2	Transmission Lines	20-3
	Characteristic Impedance	20-3
	Coaxial Cable	20-4
	Parallel-Wire Transmission Line	20-5
	Stripline and Microstrip	20-5
	Other Shapes	20-5
	Waveguides	20-5
	Dielectric Transmission Lines	20-13
	Reflection Coefficient	20-13
	Voltage Standing Wave Ratio	20-14
	Smith Chart	20-15
	Power Transfer	20-19
	S Parameters	20-19
	Skin Effect	20-20
20.3	Circuit Components	20-21
	Passive Linear Reciprocal Components	20-22
	Terminations	20-22
	Attenuator	20-22
	Variable attenuator	20-22
	Phase shifter	20-24
	Coupler	20-24
	Hybrids	20-24
	Antennas	20-24
	Filters	20-24
	Passive Linear Nonreciprocal Components	20-25
	Isolator	20-25
	Limiter	20-28
	Active Linear Reciprocal Components	20-29
	Switch	20-29
	Attenuators	20-29
	Active Linear Nonreciprocal Components	20-29
	Amplifiers	20-29
20.4	Antennas	20-33
	Reciprocity	20-33
	Isotropic Radiator	20-33
	Antenna Patterns	20-33
	Polarization	20-34
	Directivity	20-34
	Gain	20-34
	Effective Area	20-34
	Beamwidth	20-35
	Estimating Beamwidth and Directivity	20-35
	Antenna Arrays	20-36
	Pattern Multiplication	20-37
	Microwave Antennas	20-38
20.5	Test Equipment	20-41
	Power Meter	20-41
	SWR Meter	20-42
	Slotted Line	20-42

Frequency Meter	20-42
RF Sources	20-42
Swept Return and Insertion Loss Test Set	20-45
Microwave Network Analyzer	20-47
20.6 Bibliography	20-47

## **21. FIBER-OPTIC SYSTEMS**

21.1 Introduction	21-1
21.2 Optical Fibers and Cables	21-4
Light Guiding	21-4
Attenuation	21-7
Fiber Bandwidth	21-12
Cabled Fibers	21-14
Fiber Connectoring	21-17
Splices	21-17
Connectors	21-18
Couplers	21-19
Connectoring mismatch losses	21-20
21.3 Optical Transmitters and Sources	21-21
Light-Emitting Diodes	21-23
Injection Laser Diodes	21-28
21.4 Optical Detectors and Receivers	21-32
Responsivity	21-34
Noise Equivalent Power	21-36
Sensitivity	21-38
21.5 System Design	21-38
21.6 Selected Bibliography	21-42

## **22. ACTIVE FILTERS**

22.1 Introduction	22-1
22.2 Low-Pass and High-Pass Filters	22-2
First-Order Filters	22-2
Amplifying filters	22-3
Second-Order Filters	22-5
Effect of $Q$	22-5
Circuits	22-6
Design data	22-10
Circuit features	22-12
Third- and Higher-Order Filters	22-12
Single op amp third-order filter	22-12
Cascaded filters	22-13
Attenuation rate	22-14
22.3 Bandpass and Bandstop Filters	22-16
Broadband Filters	22-16
Narrowband Filters	22-17
Bandpass filter	22-17
Bandstop filter	22-20

22.4 State-Variable Filters	22-22
Basic Circuit	22-22
IC filters	22-24
Low- and high-pass functions	22-24
Bandpass function	22-26
Bandstop (notch) function	22-27
Higher-order filters	22-27
Low-frequency operation	22-27
Voltage-tuned filters	22-28
22.5 Other Filters	22-29
Elliptic Filters	22-29
All-Pass Networks	22-29
Digital Filters	22-30
22.6 References and Bibliography	22-31

## **23. DIGITAL MULTIMETERS**

23.1 Basic Building Blocks	23-1
23.2 DC Input Amplifier/Attenuator	23-2
23.3 Internal Reference Voltage	23-3
23.4 AC Conversion	23-4
23.5 Measuring Resistance	23-6
23.6 A/D Conversion Techniques	23-7
23.7 Noise Rejection	23-10
23.8 How To Read DMM Specifications	23-14

## **24. OSCILLOSCOPE MEASUREMENTS**

24.1 Introduction	24-1
24.2 Oscilloscope Controls	24-2
Display System	24-2
Beam finder	24-4
Intensity	24-4
Focus	24-4
Trace rotation	24-4
Vertical System	24-4
Vertical position	24-5
Input coupling	24-5
VOLTS/DIV switch	24-5
Variable volts per division	24-5
Channel 2 inversion	24-5
Vertical operating modes	24-5
Horizontal System	24-6
Horizontal position	24-6
Seconds per division	24-6
Variable seconds per division	24-7
Horizontal magnification	24-7
Horizontal operating mode	24-7

Trigger System	24-7
Trigger level and slope	24-8
Variable trigger holdoff	24-8
Trigger sources	24-9
Trigger operating modes	24-10
Trigger coupling	24-11
24.3 Oscilloscope Measurements	24-11
Safety	24-11
Getting Set Up	24-11
Probes	24-12
Probe compensation	24-12
Probe handling	24-12
Basic Waveforms	24-12
Measurement Techniques	24-13
Direct and derived measurements	24-14
Period measurements	24-16
Frequency measurements	24-16
Rectangular-wave measurements	24-17
Pulse measurements	24-17
Phase measurements	24-18
XY measurements	24-19
Differential measurements	24-20
Z axis measurement	24-20
Delayed-sweep measurements	24-21
24.4 Effects of Instrument Performance	24-24
Instrument Risetime and Measured Risetimes	24-24
Relating Bandwidth and Risetime	24-25
Measurement System Bandwidth	24-27
Circuit Loading	24-27
24.5 Storage Oscilloscopes	24-28
CRT Storage Oscilloscopes	24-28
Bistable CRT storage	24-28
Variable-persistence CRT storage	24-28
Fast-transfer CRT storage	24-29
Stored writing speed	24-29
Digital Storage Oscilloscopes	24-30
How digital storage works	24-30
Comparing digital and CRT storage	24-31
Digital storage oscilloscope specifications	24-32
24.6 Selecting an Oscilloscope	24-33
24.7 Bibliography	24-35

**APPENDIX**

A. The Greek Alphabet	A-1
B. Probable Values of General Physical Constants	A-1
C. Conversion Factors and Prefixes	A-2
D. Decibel Table	A-3
E. Natural Sines and Cosines	A-4

F. Natural Tangents and Cotangents	A-6
G. Common Logarithms of Numbers	A-8
H. Natural, Naperian, or Hyperbolic Logarithms	A-10
I. Degrees and Minutes Expressed in Radians	A-12
J. Radians Expressed in Degrees	A-14
K. Exponentials	A-15
L. Trigonometric Relations	A-17
M. Properties of Hyperbolic Functions	A-18
Figs. 1 and 2: Reactance Charts	

**Index follows the Appendix**