

# CONTENTS

<b>Preface to the First Edition</b>	<b>xv</b>
<b>Preface to the Second Edition</b>	<b>xix</b>
<b>List of Symbols</b>	<b>xxi</b>
<b>Acknowledgments</b>	<b>xxv</b>
<b>1 Introduction to Electronic Measurement Systems</b>	<b>1</b>
1.1 Information	1
1.2 Types of measurement	4
1.3 Why electronic measurement systems?	5
1.4 Future trends	8
Problems	10
Bibliography	10
<b>2 Types of Measuring System</b>	<b>11</b>
2.1 Introduction	11
2.2 Functional structures	12
2.2.1 Measuring structures for an active physical quantity	12
2.2.2 Measuring structures for a passive physical quantity	14
2.3 Signal structures	16
2.3.1 Signals with a unique character	17
2.3.2 Periodic signals	22
2.3.3 Sampled signals	26
2.3.4 Stochastic signals	30
2.4 Spatial structures	32
2.4.1 A multiple-input/output configuration	33
2.4.2 A centralized data-acquisition system	34
2.4.3 A decentralized data-acquisition system with a digital multiplexer	37
2.4.4 A distributed multiplexer data-acquisition system	37
2.4.5 Telemetry	38
2.5 Automated electronic structures	39
2.6 I/O interface	41
2.6.1 IEEE 488	41
2.6.2 The VXI/VME bus	42
2.6.3 Serial and industrial networks, RS-232 (V24)	43
2.6.4 Plug-in data-acquisition (DAQ) boards	44
2.7 Architecture of bus systems	46

<b>Problems</b>	<b>48</b>
<b>Bibliography</b>	<b>49</b>
<b>3 Implementations of Functions</b>	<b>50</b>
3.1 Introduction	50
3.2 Tools	50
3.2.1 Complex calculus and variables	50
3.2.2 Laplace transform of signals	55
3.2.3 Description of linear systems	56
3.3 Analogue functions	67
3.3.1 The operational amplifier	67
3.3.2 Preamplifier with adjustable gain	69
3.3.3 The non-inverting operational amplifier	70
3.3.4 The differential amplifier configuration	70
3.3.5 The comparator	71
3.3.6 The integrator	72
3.3.7 A constant-current source	73
3.3.8 The logarithmic amplifier	73
3.3.9 A current-to-voltage converter	75
3.3.10 An analogue multiplier	75
3.3.11 A peak detector	77
3.4 Filters	77
3.4.1 Types of filter	78
3.4.2 The switched capacitor	78
3.5 Analogue-to-digital and digital-to-analogue conversions	79
3.5.1 Introduction	79
3.5.2 Coding	79
3.6 Digital-to-analogue converters	82
3.6.1 The adder network	82
3.6.2 The ladder network	83
3.7 Analogue-to-digital converters	85
3.7.1 The dual-slope integration ADC	85
3.7.2 The sigma-delta modulator ADC	87
3.7.3 Voltage-to-frequency converter (VFC)	89
3.7.4 Successive approximation ADC	90
3.7.5 Parallel converter	91
3.8 Digital functions	91
3.8.1 A decoder	91
3.8.2 An encoder	92
3.8.3 A multiplexer	92
3.9 User-programmable logic devices	93
3.9.1 Combinational logic	95
3.9.2 Realizations of programmable arrays	96
3.9.3 Sequential logic	101

<b>3.10 Miscellaneous</b>	102
3.10.1 The conventional Wheatstone bridge configuration	103
3.10.2 An integrated Wheatstone bridge	104
3.10.3 The principle of the constant-voltage, constant-current bridge configuration	105
<b>Problems</b>	108
<b>Bibliography</b>	109
<b>4 System Specifications</b>	110
4.1 Introduction	110
4.2 Technical specifications	110
4.2.1 Application area	111
4.2.2 Resolution	113
4.2.3 Accuracy and inaccuracy	113
4.2.4 Sensitivity	116
4.2.5 Linearity	117
4.2.6 Offset and drift	119
4.2.7 Rejection factor	119
4.2.8 Dynamic range	123
4.2.9 Reliability	126
4.2.10 The number of measurements per unit time	126
4.2.11 Environmental conditions	128
4.3 Types of error	128
4.3.1 Systematic errors	128
4.3.2 Conditional errors	129
4.3.3 Stochastic errors	129
4.4 Measures for improving electronic systems	130
4.4.1 The feedback principle	130
4.4.2 Feedforward coupling	133
4.4.3 The influence of feedback on input and output impedance	136
4.5 A microprocessor-based measuring system	139
4.5.1 Microprocessor fundamentals	139
<b>Problems</b>	150
<b>Bibliography</b>	152
<b>5 Reliability</b>	153
5.1 Introduction	153
5.2 Reliability concepts	154
5.2.1 Definitions	154
5.2.2 Stochastic variables, probability distributions, functions and reliability	155
5.2.3 Reliability parameters	158
5.2.4 The mean time between failure	160

5.3	Families of lifetime distributions	161
5.4	Reliability of parts, components, equipment and systems	163
5.4.1	The ISO 9000 system	165
5.5	Availability; repairable and non-repairable systems	166
5.6	Boolean algebra and reliability	169
5.7	The reliability and MTBF of systems in series	172
5.8	The reliability and MTBF of systems in parallel	173
5.8.1	An active on-line standby system	174
5.8.2	A cold on-line standby system	177
5.8.3	A parallel $k$ out of $n$ system	179
5.9	Methods to determine the reliability of systems	180
5.9.1	The network reduction method	180
5.9.2	The path-tracing technique	182
5.9.3	The decomposition technique	182
5.9.4	The minimal-cut-set technique	185
5.9.5	Markov techniques	186
5.10	Design aspects	193
5.11	Causes of failure	199
5.12	Software	201
5.13	Future developments	202
	Problems	202
	Bibliography	204

<b>6</b>	<b>Transducers</b>	<b>205</b>
6.1	Introduction	205
6.2	Classification of transducers	206
6.2.1	Types of energy form	207
6.2.2	Types of energy source	208
6.2.3	Modulating and self-generating transducers	209
6.3	State descriptions	213
6.3.1	The steady-state description	214
6.3.2	The dynamic-state description	216
6.4	Transducer parameters, definitions and terminology	218
6.4.1	Transducer parameters	218
6.4.2	Definitions and terminology	218
6.5	Characteristics of integrated circuits and transducers	221
6.5.1	Silicon technology	224
6.5.2	Size and linewidth	224
6.5.3	Complexity	225
6.5.4	Power consumption	225
6.5.5	Reliability	226
6.5.6	Electrons versus photons as information carrier	227
6.5.7	Available technologies for transducers	227
6.5.8	Price–performance ratio	230
6.5.9	Application areas	231

6.6	Transducer effects in silicon and other compatible materials	231
6.6.1	Transducer effects in silicon	231
6.6.2	Transducer effects in compatible materials	231
6.6.3	Transducer effects in optical semiconductors	232
6.7	The optical energy domain	234
6.7.1	Physics	234
6.7.2	Applied units in the optical domain	235
6.7.3	The interaction of electromagnetic radiation with semiconductors	236
6.7.4	The p-n junction in the optical domain	237
6.7.5	The influence of temperature and radiation on the conductivity	238
6.7.6	Radiant energy in silicon microtransducers	240
6.7.7	Radiant energy in compatible technology	243
6.7.8	Fibre technology	245
6.7.9	Review of known optical effects	248
6.8	The mechanical energy domain	248
6.8.1	Physics	248
6.8.2	Mechanical energy in silicon microtransducers	254
6.8.3	Mechanical energy in compatible technology	256
6.8.4	Review of effects in the mechanical energy domain	257
6.9	The thermal energy domain	257
6.9.1	Physics	257
6.9.2	Thermal effects in semiconductors	260
6.9.3	Thermal energy in silicon microtransducers	261
6.9.4	Thermal energy in compatible technology	263
6.9.5	Review of effects in the thermal energy domain	265
6.10	The magnetic energy domain	265
6.10.1	Physics	266
6.10.2	Hall effect	268
6.10.3	Magnetic energy and silicon microtransducers	271
6.10.4	Magnetic energy in compatible technology	273
6.10.5	Physical effects in the magnetic energy domain	274
6.11	The chemical energy domain	275
6.11.1	'Physics'	275
6.11.2	Chemical energy in silicon microtransducers	278
6.11.3	Review of chemical effects	280
6.12	Future trends in transducers	280
6.12.1	Technological trends	280
	Problems	282
	Bibliography	284
7	Offset and drift	286
7.1	Introduction	286
7.2	Principles of offset voltage and current	287

7.3	Calculation of the offset voltage and current	288
7.3.1	The bipolar transistor	289
7.3.2	The field effect transistor	289
7.4	Offset behaviour of differential amplifier stages	291
7.4.1	The bipolar differential input stage	291
7.4.2	The junction FET differential input stage	293
7.4.3	The MOSFET differential input stage	293
7.5	Offset in transducers	294
7.6	Drift behaviour of offset current and voltage	294
7.6.1	Stochastic variations in electrical conductivity	295
7.6.2	Aging, humidity and vibrations	295
7.6.3	Power supply variations	295
7.7	The influence of temperature	296
7.8	Temperature drift in bipolar transistors	298
7.9	Temperature drift in FETs	300
7.9.1	The junction field effect transistor	300
7.9.2	The MOS field effect transistor	302
7.10	Drift in sensors	303
7.10.1	Drift elimination by modulation	306
7.10.2	The alternating direction method (ADM)	307
	Problems	309
	Bibliography	310
<b>8</b>	<b>Guarding and Shielding</b>	<b>311</b>
8.1	Introduction	311
8.2	The nature and causes of interference	311
8.2.1	Sources of interference	315
8.3	Aspects of guarding	317
8.3.1	Ground and earth	318
8.3.2	A grounded system	319
8.4	Aspects of shielding	321
8.4.1	A shielding cabinet	321
8.4.2	A shielding cabinet as part of an electronic circuit	322
8.4.3	The use of more than one shielding cabinet	323
8.4.4	The connection of a common in a multiple-cabinet configuration	324
8.5	Interference caused by a magnetic field	328
8.6	Types of coupling mechanism	330
8.6.1	Direct coupling	331
8.6.2	Magnetic coupling	333
8.7	Interference caused by power supply transformers	334
8.8	The differential amplifier and guarding	338
8.8.1	The common-mode rejection ratio	341
8.8.2	The CMRR in shielding circumstances	342

8.9 Improvement of the common-mode rejection ratio	344
8.9.1 The application of a floating guard	345
8.9.2 Active guarding or the application of double-shielded cables	348
8.10 Worked examples	349
8.11 Electromagnetic compatibility	354
8.11.1 New Approach, Global Approach and CE mark	354
8.11.2 Generic emission standards	356
Problems	358
Bibliography	360
<b>9 Noise Calculations</b>	<b>361</b>
9.1 Introduction	361
9.2 Noise voltage, noise current and noise figure	362
9.2.1 The noise voltage $e_n$	362
9.2.2 The noise current $i_n$	363
9.2.3 The noise figure NF	363
9.3 The relationship between the noise voltage, noise current and noise figure	364
9.4 Calculating total noise voltage	366
9.5 Calculating the noise figure and the signal-to-noise ratio	370
9.6 The noise figure myth	372
9.6.1 The optimum source resistance	373
9.6.2 The optimum signal-to-noise ratio	375
9.7 Other noise calculating techniques	380
9.7.1 Shifting noise sources	380
9.7.2 Superposition	382
9.7.3 Thevenin and Norton	382
9.7.4 Noise sources in series and in parallel	383
9.7.5 Worked examples	385
Problems	388
Bibliography	389
<b>10 Physics of Noise</b>	<b>390</b>
10.1 Introduction	390
10.2 Thermal noise or Johnson noise in conductors	390
10.3 Shot noise	391
10.4 Flicker noise	392
10.5 Noise in semiconductor components	394
10.5.1 Noise behaviour of the bipolar transistor	394
10.5.2 Noise behaviour of the field effect transistor	396
10.5.3 Noise behaviour of the diode	399
10.6 Noise in sensors	401
Bibliography	403

<b>11 Interfacing to Sensors</b>	<b>404</b>
11.1 Introduction	404
11.2 Sensors in bridge configurations	405
11.2.1 Bridge configuration with one sensor element	405
11.2.2 Bridge configuration with two sensor elements	406
11.2.3 Bridge configuration with four sensor elements	407
11.2.4 A double-bridge configuration	408
11.2.5 Biasing bridge circuits	408
11.3 Bridge amplifier configurations	410
11.3.1 Circuit 1	410
11.3.2 Circuit 2	410
11.3.3 Circuit 3	412
11.3.4 Circuit 4	412
11.3.5 Circuit 5	413
11.3.6 Circuit 6	414
11.3.7 Circuit 7	414
11.4 Telemetry	416
11.5 Hybrid interfacing circuits	417
11.6 Autozeroing	417
11.6.1 Autozeroing in electronics	417
11.6.2 Autozeroing in transducers	418
Problems	418
Bibliography	419
<b>12 Ergonomics or Human Engineering</b>	<b>420</b>
12.1 Introduction	420
12.2 Biological equipment of the human being	421
12.2.1 The auditory window	421
12.2.2 The visual window	421
12.3 Some other aspects of human perception of information	423
12.3.1 Transmission of information	423
12.3.2 Retrieval of information	423
12.3.3 Processing of information	424
12.4 Perception	424
12.5 Trends in the development of measuring systems	425
12.6 The observer–display interaction	427
12.7 Coding of information on displays	429
Problems	433
Bibliography	433
<b>Appendix Table of Frequently Used Physical Constants</b>	<b>434</b>
<b>Index</b>	<b>435</b>